

AN11420

NXP GPS LNA - GPS LNA voltage supply via a coax cable coming from the GPS receiver

Rev. 1 — 4 October 2013

Application note

Document information

Info	Content
Keywords	GPS, GNSS, LNA, AEC-Q100, automotive, voltage supply, coax cable
Abstract	This application note describes how to supply NXP GPS LNA voltage via a coax cable coming from the GPS receiver



Revision history

Rev	Date	Description
1	20131004	First publication

Contact information

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

1. Introduction

GPS LNAs are needed in active antenna applications due to the losses of a long cable between the antenna and the receiver.

This application note gives practical information how to supply an NXP GPS LNA via a coax cable coming from the GPS receiver. This applies to automotive qualified BGU7004 and BGU7008 since they both have the same architecture. They are AEC-Q100 qualified Low Noise Amplifiers (LNAs) for GPS receiver applications in a plastic leadless 6-pin, extremely small SOT886 package. Both of them require only one external matching inductor and one external decoupling capacitor. They adapt itself to the changing environment resulting from co-habitation of different radio systems in modern cellular handsets. During high jamming power levels, resulting for example from a cellular transmit burst, it temporarily increases its bias current to improve sensitivity. Both of them cover full GNSS L1 band, from 1559 MHz to 1610 MHz and work with a supply voltage from 1.5 V to 2.85 V.

The BGU7004 and BGU7008 performance information is available in their datasheets.

2. System features

- AEC-Q100 qualified
- Covers full GNSS L1 band, from 1559 MHz to 1610 MHz
- Noise figure = 0.85 dB for BGU7008 and 0.9 dB for BGU7004
- Gain 18.5 dB for BGU7008 and 16.5 dB for BGU7004
- High 1 dB compression point of -12 dBm for BGU7008 and -11 dBm for BGU7004
- High out of band IP_{3i} of 4 dBm for BGU7008 and 9 dBm for BGU7004
- Supply voltage 1.5 V to 2.85 V, optimized for 1.8 V
- Power down mode current consumption < 1 uA
- Optimized performance at low supply current of 4.8 mA for BGU7008 and 4.5 mA for BGU7004.
- Integrated temperature stabilized bias for easy design
- Requires only one input matching inductor and one supply decoupling capacitor
- Input and output DC decoupled
- ESD protection on all pins (HBM > 2 kV)
- Integrated matching for the output
- Small 6-pin leadless package 1 mm × 1.45 mm × 0.5 mm
- 110 GHz transit frequency - SiGe:C technology

3. Application Information

The application circuit shows how to supply the NXP GPS LNA voltage in an active antenna application via a coax cable coming from the GPS receiver is depicted in Figure 1. Table 1 shows the bill of materials.

3.1 NXP GPS LNA voltage supply in an active antenna application via a coax cable coming from the GPS receiver

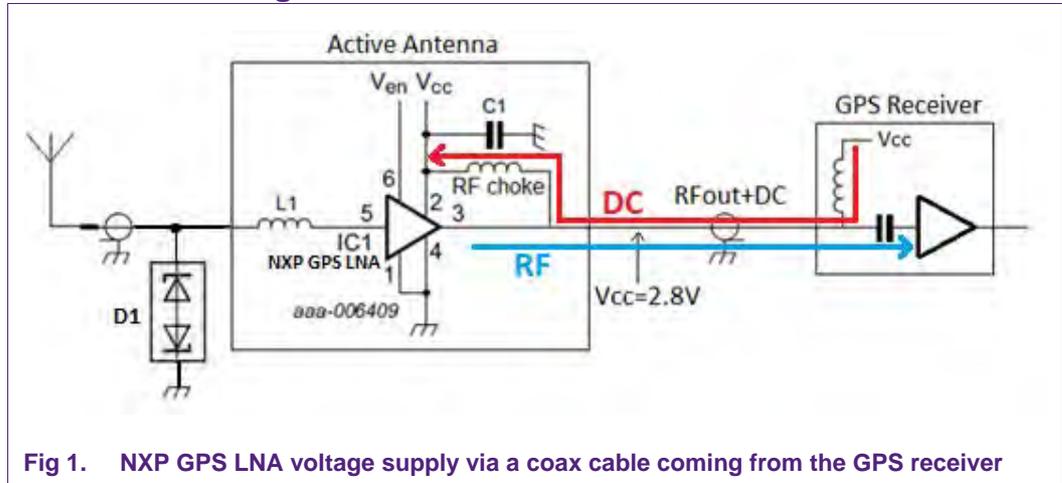


Fig 1. NXP GPS LNA voltage supply via a coax cable coming from the GPS receiver

A GPS signal comes from antenna to the NXP GPS LNA. An optional external ESD protection diode can be used to increase the system's ESD performance from 2kV up to 10kV. At the input of the GPS LNA only one external coil L1 is needed for the matching. At the input there is no external DC blocking capacitor needed since the NXP GPS LNA has an integrated input DC blocking capacitor.

Note that now at the output of the GPS LNA, there are an RF signal and a DC voltage. For the voltage supply of the GPS LNA, since the voltage supply comes from the GPS receiver to the output of the GPS LNA via a coax cable, the voltage supply is tapped from the output of the GPS LNA to the voltage supply Vcc of the GPS LNA via an RF choke, which blocks the RF signal and passes the DC supply voltage.

Close to the Vcc pin (pin 2) of the GPS LNA, an external decoupling capacitor C1 is needed to decouple and to give an extra filtering of the RF signal in the DC supply line.

At the output of the GPS LNA, there is no external DC blocking capacitor needed either because the NXP GPS LNA has an integrated output DC blocking capacitor as well, which blocks the DC supply voltage and passes the RF signal.

The enable (pin 6 of the GPS LNA) voltage can be connected to Vcc for "always on" or supplied separately. Pin 1 and 4 of the GPS LNA are grounded. The BGU7004 and BGU7008 pinning information is available in their datasheets.

Figure 2 until Figure 5 show the comparison for BGU7008 at 2.85V between the default application and the one using supply voltage via a coax cable in term of NF, Gain, Input Return Loss, and Output Return Loss respectively. The figures show that there are no significant differences in term of performance between the default application and the one using supply voltage via a coax cable.

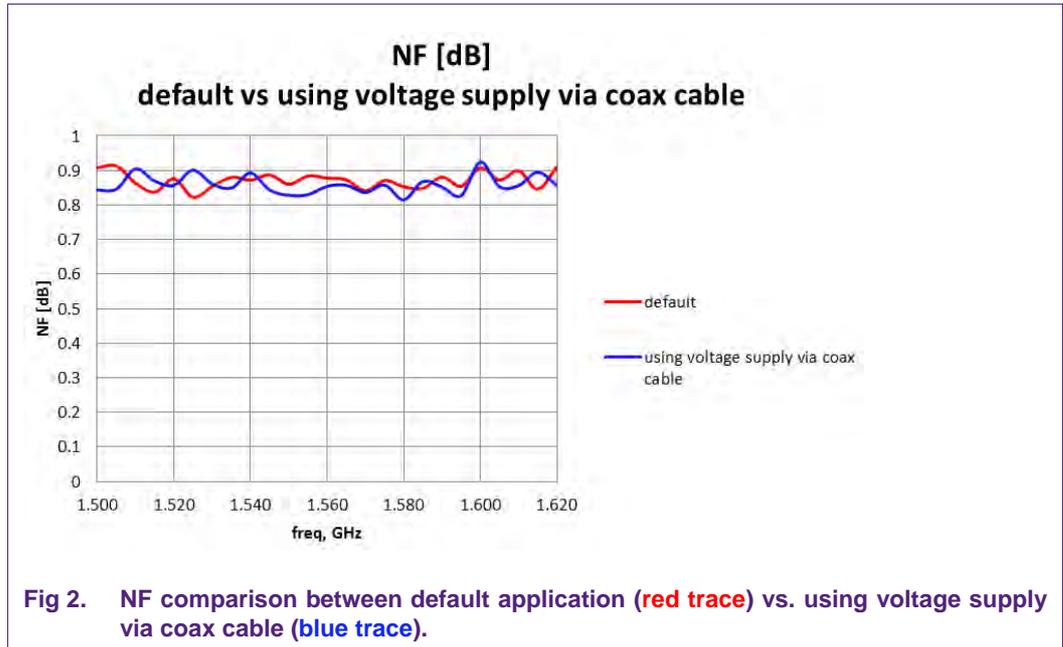


Fig 2. NF comparison between default application (red trace) vs. using voltage supply via coax cable (blue trace).


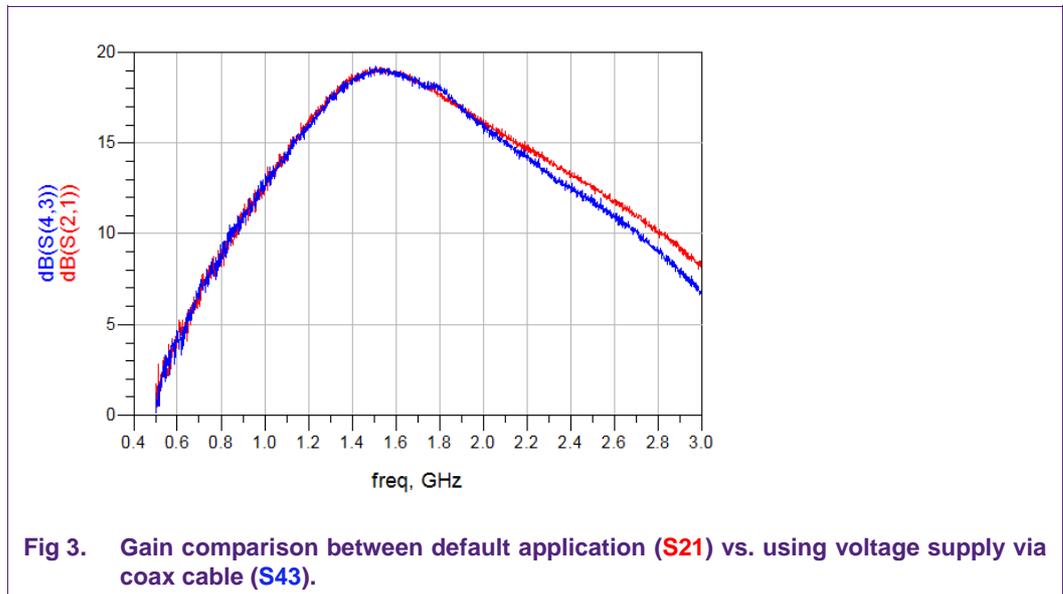
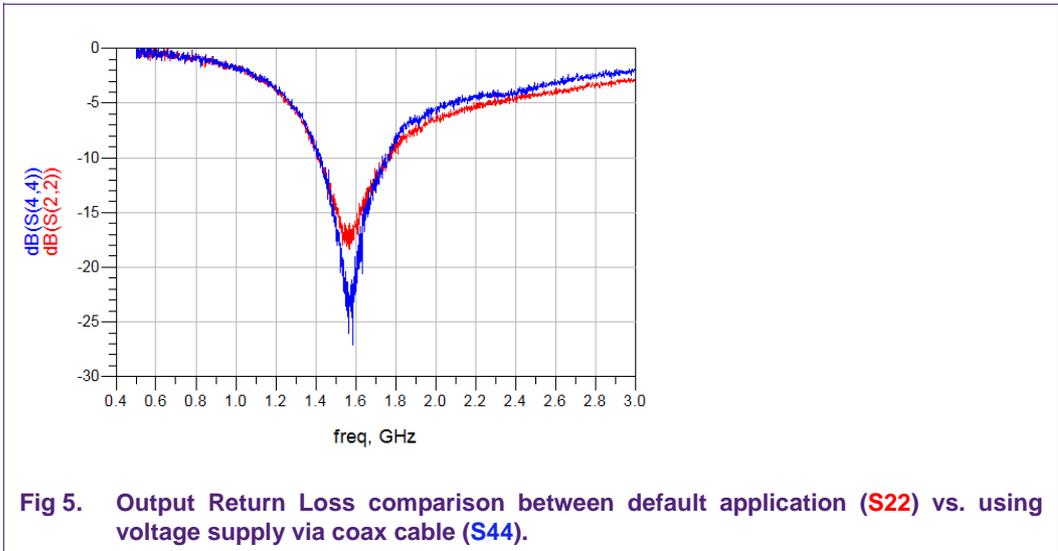


Fig 3. Gain comparison between default application (S21) vs. using voltage supply via coax cable (S43).

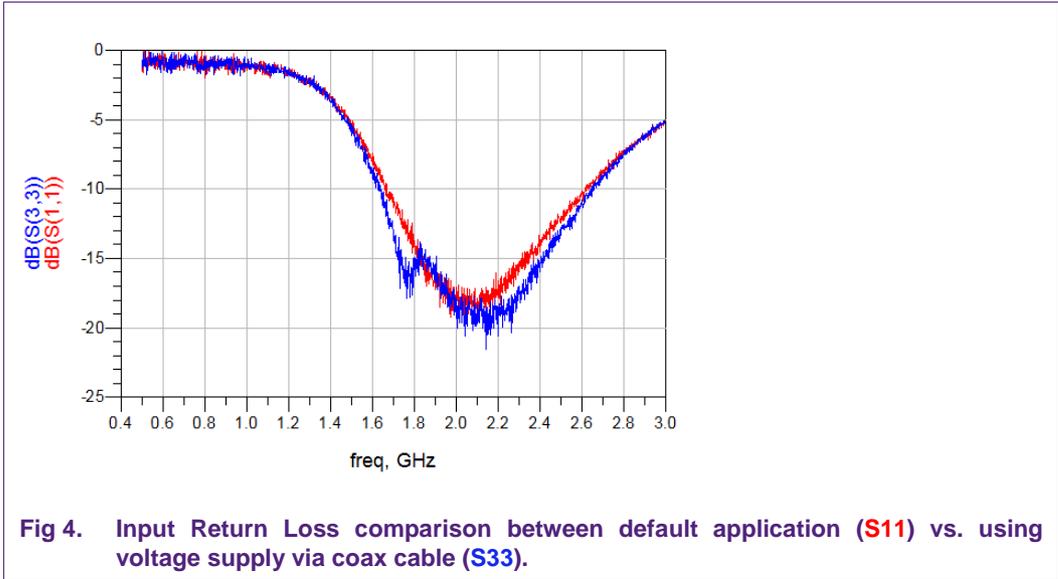

3.2 Bill of materials

Table 1. Evaluation board BOM

Component	Description	Value	Supplier
C1	Decoupling capacitor	1 nF	various
IC1	BGU7004 or BGU7008 GPS LNA	-	NXP
L1	High quality matching inductor	5.6 nH	Murata LQW15A
RF choke	RF choke	100 nH	Murata LQG15HS
D1	ESD Diode (optional)	PESD5V0F1BL	NXP

4. Abbreviations

Table 2. Abbreviations

Acronym	Description
DC	Direct Current
RF	Radio Frequency
GPS	Global Positioning System
LNA	Low Noise Amplifier
GNSS	Global Navigation Satellite System
ESD	Electro Static Discharge
HBM	Human Body Model
SiGe:C	Silicon Germanium Carbon

5. Legal information

5.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

5.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP

Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from national authorities.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

5.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are property of their respective owners.

6. List of figures

Fig 1.	NXP GPS LNA voltage supply via a coax cable coming from the GPS receiver	4
Fig 2.	NF comparison between default application (red trace) vs. using voltage supply via coax cable (blue trace).....	5
Fig 3.	Gain comparison between default application (S21) vs. using voltage supply via coax cable (S43).....	5
Fig 4.	Input Return Loss comparison between default application (S11) vs. using voltage supply via coax cable (S33).....	6
Fig 5.	Output Return Loss comparison between default application (S22) vs. using voltage supply via coax cable (S44).....	6

7. List of tables

Table 1. Evaluation board BOM.....6
Table 2. Abbreviations7

8. Contents

1.	Introduction	3
2.	System features.....	3
3.	Application Information	3
3.1	NXP GPS LNA voltage supply in an active antenna application via a coax cable coming from the GPS receiver.....	4
3.2	Bill of materials.....	6
4.	Abbreviations	7
5.	Legal information	8
5.1	Definitions	8
5.2	Disclaimers.....	8
5.3	Trademarks	8
6.	List of figures.....	9
7.	List of tables	10
8.	Contents.....	11

Please be aware that important notices concerning this document and the product(s) described herein, have been included in the section 'Legal information'.

© NXP B.V. 2013.

All rights reserved.

For more information, visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: 4 October 2013

Document identifier: AN11420