

# AN11787

## Low-Cost External Remote Keyless Entry (RKE) Low Noise Amplifier for 315 / 433 / 868 MHz Automotive Applications using the BFU520W RF Transistor

Rev. 1 — 22 March 2016

Application Note

### Document information

| Info            | Content  |
|-----------------|--|
| <b>Keywords</b> | BFU520W, Remote Keyless Entry, RKE, Automotive, LNA  |
| <b>Abstract</b> | This document provides circuit schematic, layout, BOM and typical evaluation board performance for a low-cost, wideband LNA covering 315, 433 & 868 MHz bands . Two LNA variants are presented; “Type 1” is set up to run from a fixed 5 volt supply (in-vehicle application) whereas the “Type 2” is modified so as to run from a single-cell battery as in a Keyfob. |



**Revision history**

| <b>Rev</b> | <b>Date</b> | <b>Description</b> |
|------------|-------------|--------------------|
| 1          | 20160322    | First publication  |

**Contact information**

For additional information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: [salesaddresses@nxp.com](mailto:salesaddresses@nxp.com)

## 1. Introduction

The **BFU520W** is an Automotive-Qualified (AEC-Q101) silicon RF Transistor for high-frequency, low-noise applications. BFU520W is one of 20 different types of RF transistor in NXP’s new BFU5xxx family. Fabricated in a modern 8-inch process, these devices show exceptional device-to-device consistency and very high production yields. BFU5xxx devices are suitable for small signal to medium power RF applications up to 2 GHz, have a collector-emitter breakdown voltage  $V_{CE0}$  of 12 volts, and are available in a wide variety of industry-standard surface-mount packages. All members of this transistor family are Automotive-Qualified per AEC-Q101. **Figure 1** below gives an overview of this family of devices, with the “I<sub>cc</sub>” row showing typical (not maximum permitted) operating currents for each type.

| Package         | Transistor Types |          |          |         |         |
|-----------------|------------------|----------|----------|---------|---------|
| I <sub>cc</sub> | 5 mA             | 10 mA    | 20 mA    | 30 mA   | 150 mA  |
| SOT323          | BFU520W          | BFU530W  | BFU550W  |         |         |
| SOT23           | BFU520A          | BFU530A  | BFU550A  |         |         |
| SOT143          | BFU520           | BFU530   | BFU550   |         |         |
| SOT143X         | BFU520X          | BFU530X  | BFU550X  |         |         |
| SOT143XR        | BFU520XR         | BFU530XR | BFU550XR |         |         |
| SOT89           |                  |          |          | BFU580Q | BFU590Q |
| SOT223          |                  |          |          | BFU580G | BFU590G |
| SOT363          | BFU520Y          |          |          |         |         |

**Fig 1. Overview of BFU5xxx family of RF Transistors**

### Key Benefits of BFU5xxx family:

- **Automotive-Qualified per AEC-Q101**
- High Gain, Low Noise Figure; suitable for applications up to 2 GHz
- Low cost / high performance-to-price ratio
- Five (5) different RF transistor chip types – covering low current, low-noise to higher current, medium power ‘driver’ applications
- Eight (8) different industry-standard package types with externally visible connections to facilitate visual inspection of solder joints
- Compliant to Directive 2002/95/EC, regarding Restriction of Hazardous Substances (RoHS) following NXP’s RHF-2006 indicator D (dark green)

### Key Benefits of BFU520W External RKE LNA described in this Applications Note:

- 3 – 5 dB improvement in RKE Receiver Sensitivity
- High Gain & Low Noise Figure with only ~ 3.5 mA current consumption
- Broad Bandwidth => same design used for 315, 433 & 868 MHz with no changes
- Very Low-cost implementation; no chip inductors (only resistors & capacitors)
- Unconditional Stability
- Easy-to-use, forgiving design, using only “E12” series component values
- Flexible – Gain, Linearity, etc. can be adjusted by changing values of externals


## 2. Automotive RKE application constraints, the ‘range problem’ and BFU520W LNA Design

**Figure 2** shows frequency bands in use for Remote Keyless Entry applications, along with car & light truck production volumes for different regions as of 2015. RKE systems presently in use operate at 315, 433 or 868 MHz. Note, a half-wavelength at 315 MHz would be ~ 47.5 cm, & about 34.5 cm at 434 MHz. If we use a half-wave dipole as a starting point or reference for an RKE system antenna, one can imagine how large this antenna would be, especially for use in keyfobs. Bear in mind, antenna efficiency tends to degrade dramatically as we reduce antenna size below this half-wavelength value.

| Region        | Estimated Vehicle Production Volume (Millions), CY2015 | RKE Frequency ( ‘1-way’ RKE ) | Comments                                   |
|---------------|--|-------------------------------|--|
| EU            | 21   | 433 MHz                       | Limited 2-way RKE applications @ 868 MHz * |
| China         | 24   | 315 MHz                       | Limited 2-way RKE applications @ 868 MHz * |
| Japan         | 13   | 315 MHz                       | Very low permitted keyfob Tx output power  |
| NAFTA         | 19   | 315 MHz                       | Limited 2-way RKE applications @ 868 MHz * |
| South America | 3  | 315 MHz                       | Limited 2-way RKE applications @ 868 MHz * |

**Fig 2. World-wide frequency bands in use for RKE applications.**

In automotive systems, the RKE receiver antenna is often placed in a non-ideal location for radio signal propagation - in the vehicle’s dashboard or other position dictated by cost and practical considerations. Such non-ideal locations increase path loss & reduce RKE system range. Furthermore, the antennas used are typically printed on a PC board, or constructed with wire or stamped metal, with lowest possible cost and poor efficiency. Lastly, these antennas are often ‘electrically short’ or smaller than a half-wavelength, in addition to being bent and folded into strange shapes, due to size constraints. All of these compromises further degrade antenna efficiency. See **Figure 3** for an example.

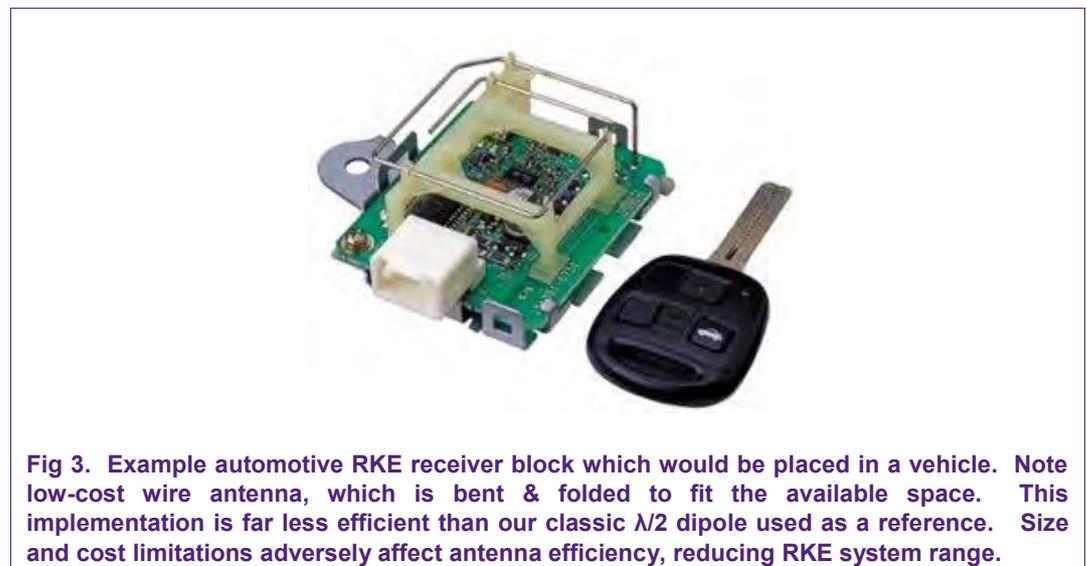

*It must be emphasized, that the above described compromises made to RKE antenna placement and implementation all tend to reduce the radio link margin or range of the RKE system.* In newer, emerging 2-Way RKE systems, the small ‘keyfob’ held by the vehicle operator also must have an RKE receiver / transceiver installed, and keyfob antennas are even smaller and less efficient, being only a small fraction of a wavelength in size. **Meanwhile, automotive manufacturers & their customers demand ever increasing range (and thus better radio link margin), with the RKE system being expected to work at ranges of 30 to 100 meters or more.**

Despite improvements in Noise Figure (and receiver sensitivity) of CMOS RKE integrated circuits themselves, the range of the RKE system is often less than desired, given all the aforementioned compromises made for the sake of cost-reduction & practicality. The Automotive RKE system designer is faced with a challenge, of how to increase RKE system range in a cost-effective way. **Figure 4** gives a list of the most common options available to increase RKE radio link margin, along with limitations of each. **The last option – addition of an external Low Noise Amplifier (LNA) stage – is usually the best option, and this application note will describe such an external LNA made with NXP’s Automotive-Qualified BFU520W RF Transistor.**

| Option   | Comment   |
|--|---|
| Improve antenna efficiency   | Limited by space & cost   |
| Increase transmitter output power                                    | Limited or constrained by battery life & government regulations         |
| Improve RKE receiver IC noise figure / sensitivity                   | Limited by CMOS process   |
| Add an external Low Noise Amplifier (LNA) between antenna and RKE IC | Most cost-effective option with minimal increase in current consumption |

**Fig 4. Options and constraints for increasing RKE system range**

Friis’ formula in **Figure 5**, describes how overall receiver noise figure of a multi-stage system is calculated. Reducing overall or ‘cascaded receiver noise figure’ will increase the range of the radio link. Per Friis’ formula, placing a low noise gain stage with Noise Factor  $F_1$  and Gain  $G_1$  in front of the RKE receiver block will reduce the noise figure contribution of subsequent stages by the reciprocal of the first stage’s gain value. If the Noise Figure of the external LNA in front of the receiver chain is sufficiently low, and LNA gain sufficiently high, a significant improvement in overall receiver sensitivity and range can be achieved. The trade-off, or price paid for using this option, is some reduction in the ability of the receiver chain to handle large signals or ‘jammers’ due to the additional gain added, as well as some increase in power consumption due to the addition of the external LNA stage. The general rule-of-thumb for receiver design is, for the first LNA stage, use as low of a noise figure LNA as reasonably possible, with just enough gain such that this first stage ‘dominates’ or ‘sets’ the overall receiver noise figure. Avoiding use of excessive gain will minimize the adverse impact on large signal handling ability for

the receiver. There are various software tools available for making these calculations and trade-offs, ranging from simple spreadsheets to more sophisticated system simulation software tools.

$$F_{total} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \frac{F_4 - 1}{G_1 G_2 G_3} + \dots + \frac{F_n - 1}{G_1 G_2 \dots G_{n-1}}$$

Fig 5. Friis' formula for calculation of overall or 'cascaded' noise figure of a receiver.

In testing with Automotive RKE Receiver and Transceiver IC's, it has been shown that overall receiver sensitivity can be improved by 3 to 5 dB by using the BFU520W external LNA described in this Applications Note.

## 2.1 BFU520W External Automotive RKE LNA Design Targets

The 'ideal' LNA should have some or all of the following characteristics:

- i) The active device should be AEC-Q101 qualified
- ii) Gain 13 - 15 dB with Noise Figure < 2 dB
- iii) Ability to adjust / increase or decrease Gain
- iv) Low-cost
- v) Operate at 5 volts (in-vehicle) or over 1.9 – 3.6 volts (from keyfob battery)
- vi) Low current consumption
- vii) Adjustable operating current to optimize linearity, Gain, etc.
- viii) Unconditional Stability ("K" > 1 and B<sub>1</sub> > 0; or μ<sub>1</sub> > 1.0 )
- ix) Wide Bandwidth to cover 315, 434 & 868 MHz bands with same design; broadband matching will also make LNA serve as a good termination for adjacent circuit blocks (filters, switches, antennas, etc.)
- x) Simple, flexible forgiving design insensitive to PC board layout variation

Using the BFU520W RF Transistor in a resistive-feedback configuration achieves the above listed goals. The LNA Gain may be increased or decreased somewhat by varying the amount of negative feedback used – simply by changing the value of the RF feedback resistor. Gain and Linearity may also be increased by increasing LNA operating current via changing the value of the bias resistor(s). This process is described in a later section of this document. Note, **no chip inductors are used** to further reduce cost – only resistors and capacitors are required.

Two variants of this basic LNA design are described in subsequent sections. Please refer to **Figure 6**. The "Type 1" refers to the in-vehicle external LNA, which runs from a 5 volt regulated power supply; the "Type 2" has its bias resistor values changed to be able to operate off of a keyfob battery – i.e. 3.6 V when the keyfob's battery is fully charged, down to 1.9 V when the battery is near the end of its life.

The schematic diagram and Bill Of Material (BOM) for each of the two LNA variants are shown in later sections.

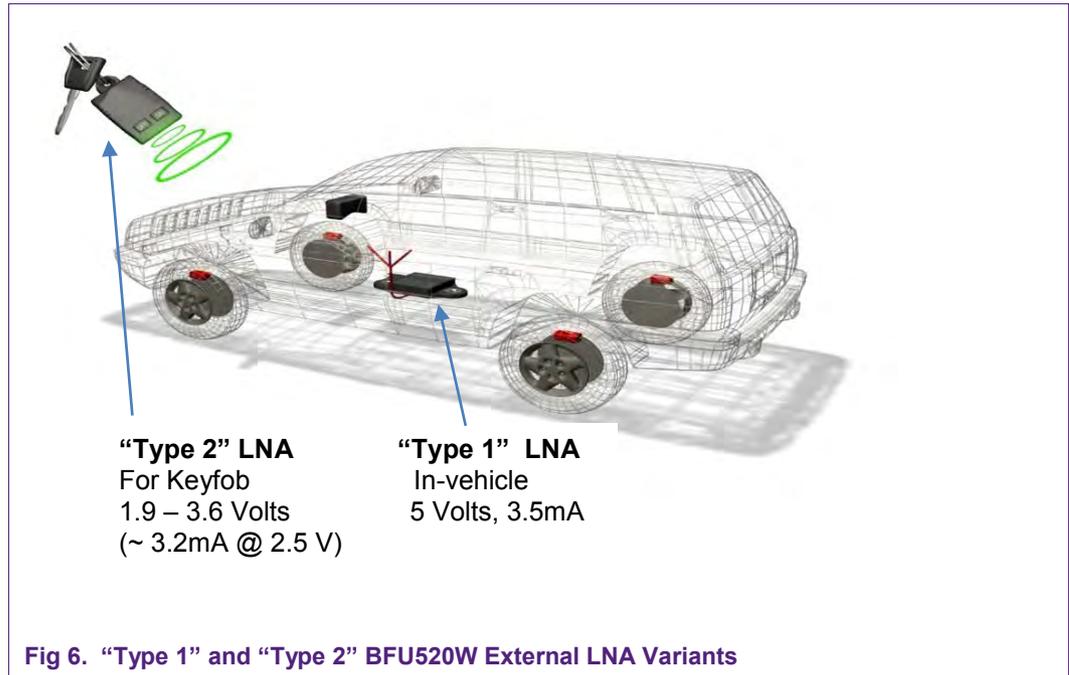


Fig 6. "Type 1" and "Type 2" BFU520W External LNA Variants

## 2.2 PC Board Details, both LNA Types

The same printed circuit board is used for both Type 1 and Type 2 LNA's. **Figure 7** gives a cross-sectional diagram of the circuit board, and **Figures 8** and **9** provide photos of the assembled board. Standard, low-cost FR4 PC board material is used along with '0402' case size passives. Note, for the circuits shown in this Applications Note, only 'E12' series component values are used. 50 ohm microstrip traces are used for the input and output transmission lines. Via holes are 0.2 mm / 0.008 inch diameter drill size, before metal plating of through-holes. The total board thickness of ~ 0.060 inch / 1.65 mm makes the circuit board stiff enough to reduce flexing or bending, helping to prevent damage or cracking to components mounted to the PCB.

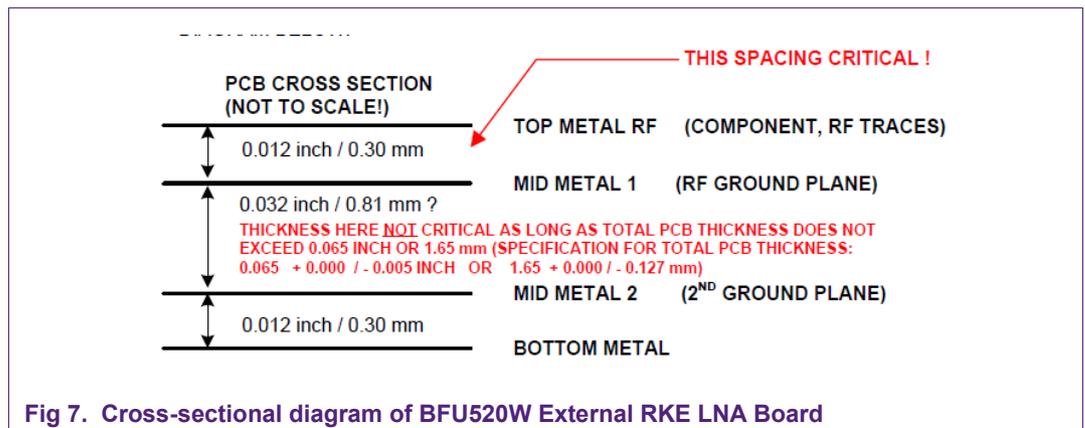


Fig 7. Cross-sectional diagram of BFU520W External RKE LNA Board

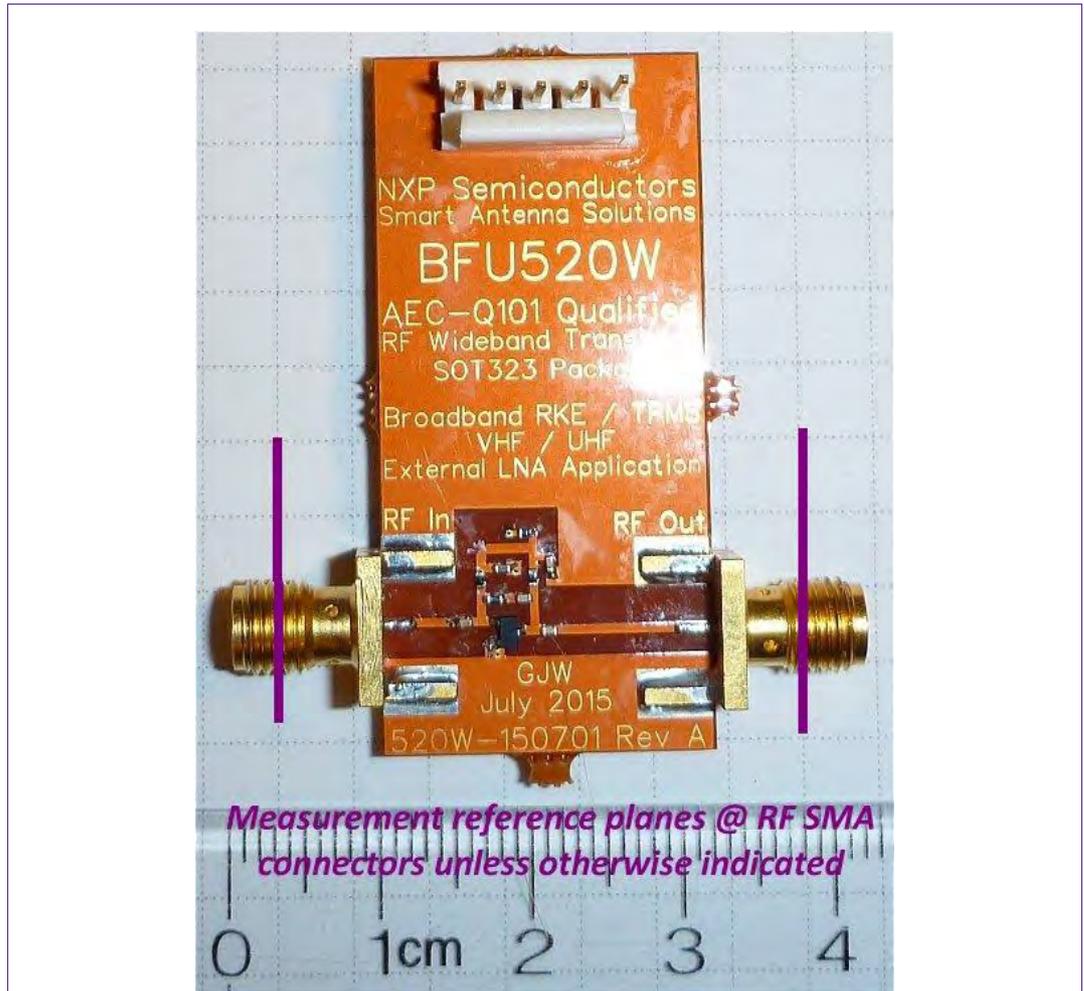


Fig 8. Photo of assembled BFU520W LNA PC board. Measurement reference planes for data shown in this document are as shown at RF connectors unless otherwise indicated.

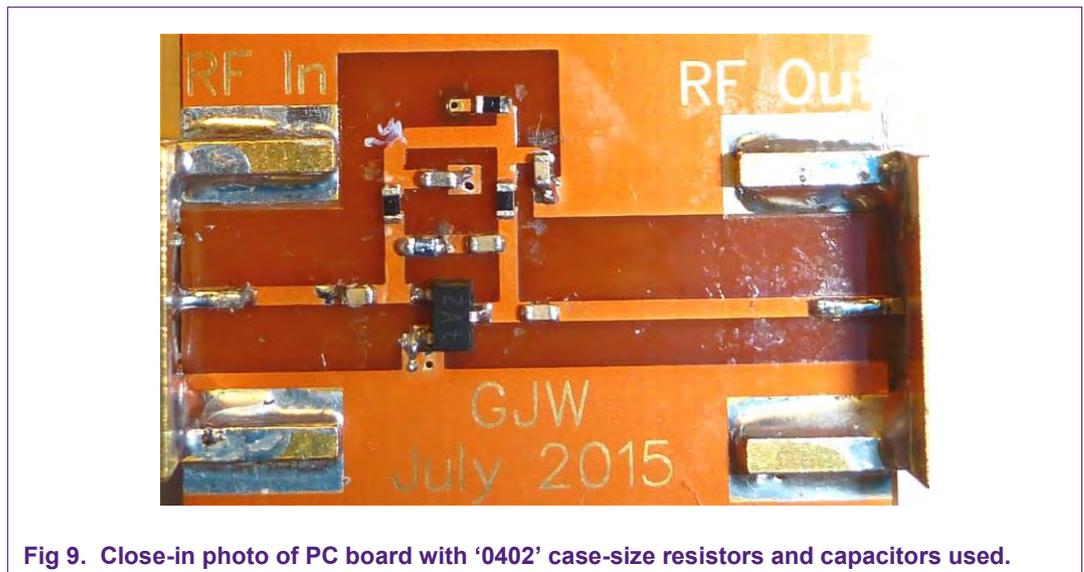


Fig 9. Close-in photo of PC board with '0402' case-size resistors and capacitors used.

### 3. Typical Application Board Test Results, “Type 1” LNA (5 Volts, 3.5mA)

This section presents results of a typical “Type 1” BFU520W LNA, designed for placement in a vehicle and running from a fixed 5 volt power supply. Measurement results are summarized in **Figure 10**. The Schematic Diagram and Bill of Material (BOM) are given in **Figures 11** and **12**, respectively. Parts placement is shown in **Figure 13**.


(T=25 °C, network analyzer source power ≈ -30 dBm, V<sub>CC</sub> = 5.0 V, V<sub>CE</sub> = 3.2 V, I<sub>c</sub>=3.5 mA, Z<sub>s</sub>=Z<sub>L</sub>=50 Ω )

| Frequency MHz | dB[s11] <sup>2</sup> | dB[s21] <sup>2</sup> | dB[s12] <sup>2</sup> | dB[s22] <sup>2</sup> | * NF dB | IIP <sub>3</sub> dBm | OIP <sub>3</sub> dBm | IP <sub>1dB</sub> dBm | OP <sub>1dB</sub> dBm |
|---------------|----------------------|----------------------|----------------------|----------------------|---------|----------------------|----------------------|-----------------------|-----------------------|
| 315           | -10.2                | 15.2                 | -21.5                | -11.5                | 1.5     | -13.2                | +2.0                 | -21.9                 | -6.7                  |
| 434           | -10.5                | 14.6                 | -21.3                | -11.4                | 1.5     | -13.4                | +1.2                 | -21.7                 | -7.1                  |
| 868           | -11.7                | 11.9                 | -20.1                | -10.3                | 1.5     | ---                  | ---                  | ---                   | ---                   |
| 915           | -11.8                | 11.6                 | -19.9                | -10.2                | 1.4     | ---                  | ---                  | ---                   | ---                   |

\* does not extract PCB loss

If PCB and RF connector loss (at input) were extracted, noise figure would be ~ 0.1 dB lower

Fig 10. Summary of measurement data for “Type 1” BFU520W LNA.

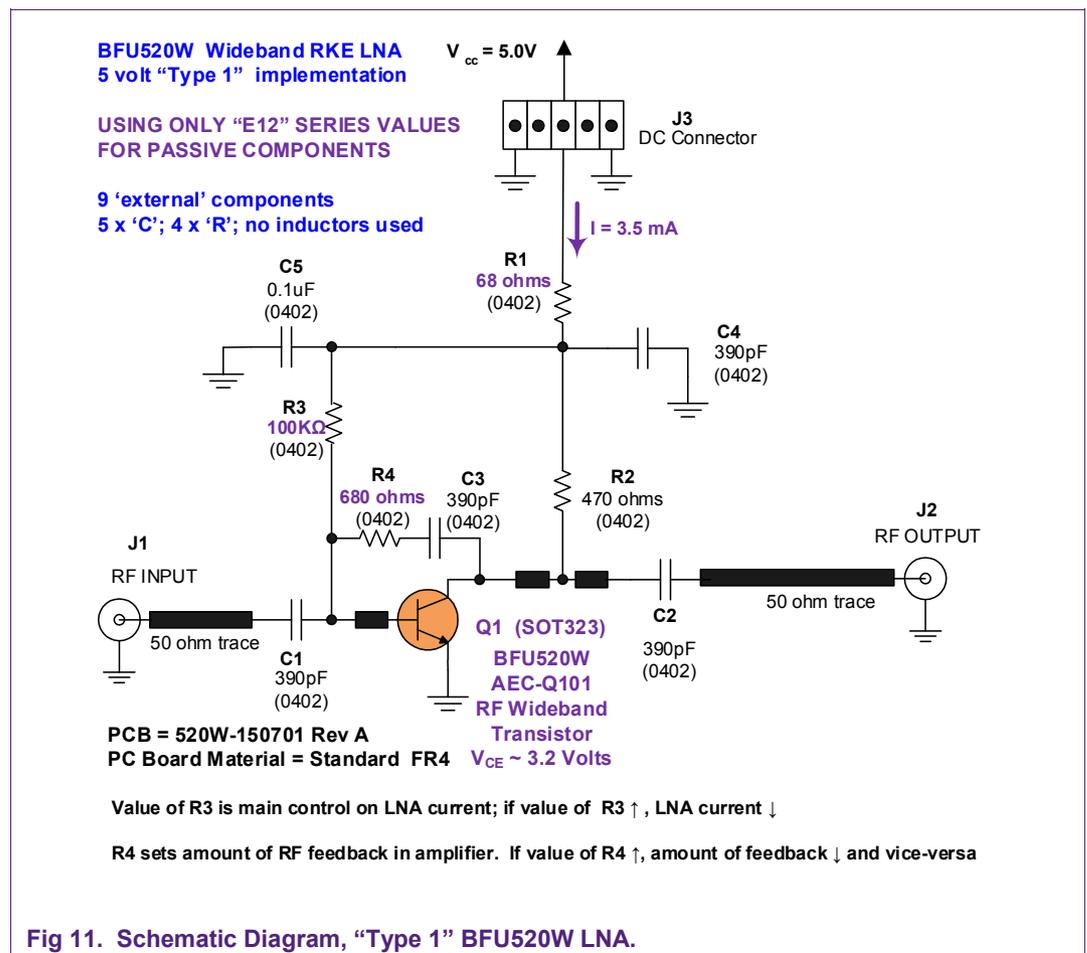

| Reference | Value          | Function / Description   |
|-----------|----------------|--|
| Q1        | -              | Active Device NXP BFU520W RF wideband Transistor, AEC-Q101 Qualified, SOT323 package   |
| C1, C2    | 390 pF         | Input & Output DC blocks   |
| C3        | 390 pF         | DC block for RF feedback path (collector-to-base)  |
| C4        | 390 pF         | Power supply decoupling, collector   |
| C5        | 0.1 $\mu$ F    | Low-frequency decoupling   |
| R1        | 68 $\Omega$    | DC bias resistor; provides some DC negative feedback to DC operating point to compensate for changes in Q1's $h_{FE}$ over temperature, etc.   |
| R2        | 470 $\Omega$   | "RF Choke" for collector (RF output) of Q1; lower cost than an inductor Trade-off: 'softer' Gain Compression curve, some loss of linearity   |
| R3        | 100 k $\Omega$ | DC bias feed to base of Q1; primary resistor for setting Q1 collector current; adjust $I_C$ by varying this value  |
| R4        | 680 $\Omega$   | RF negative feedback to amp; when value of R4 $\downarrow$ , amount of feedback is increased & vice-versa. Can decrease LNA gain by making value of R4 $\downarrow$ . But, more feedback makes Noise Figure $\uparrow$ |

**Fig 12. Bill Of Material (BOM, for Type 1 BFU520W RKE LNA (5 volt, 3.2mA variant)).**



3.1 S-Parameters, Stability Factor and Noise Figure, “Type 1” LNA

Figures 14 – 17 show broadband (25 MHz – 6 GHz) S-parameters for “Type 1” (5 volt, 3.5mA) BFU520W RKE LNA, taken at T=25°C. Figure 18 shows Stability Factor  $\mu_1$ , which verifies Unconditional Stability over 25 MHz – 6 GHz. Lastly, LNA Noise Figure is given in Figure 19.

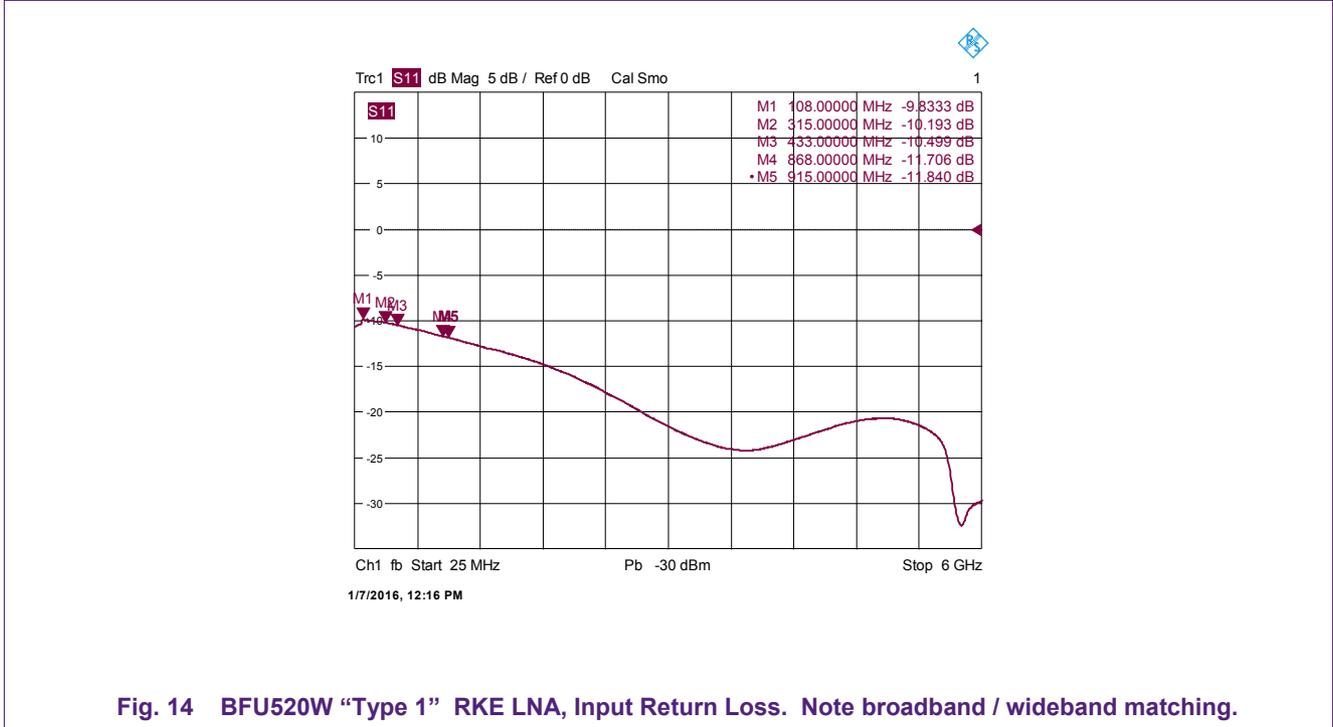


Fig. 14 BFU520W “Type 1” RKE LNA, Input Return Loss. Note broadband / wideband matching.

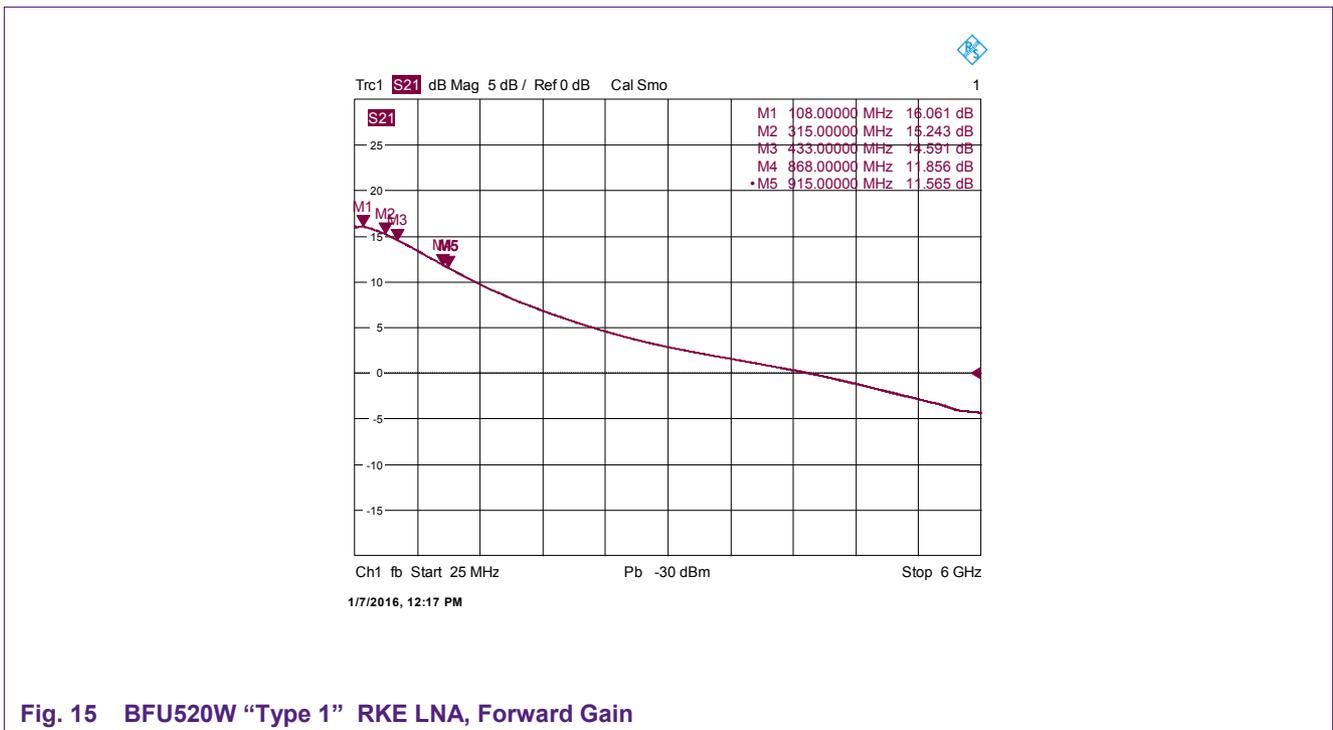


Fig. 15 BFU520W “Type 1” RKE LNA, Forward Gain

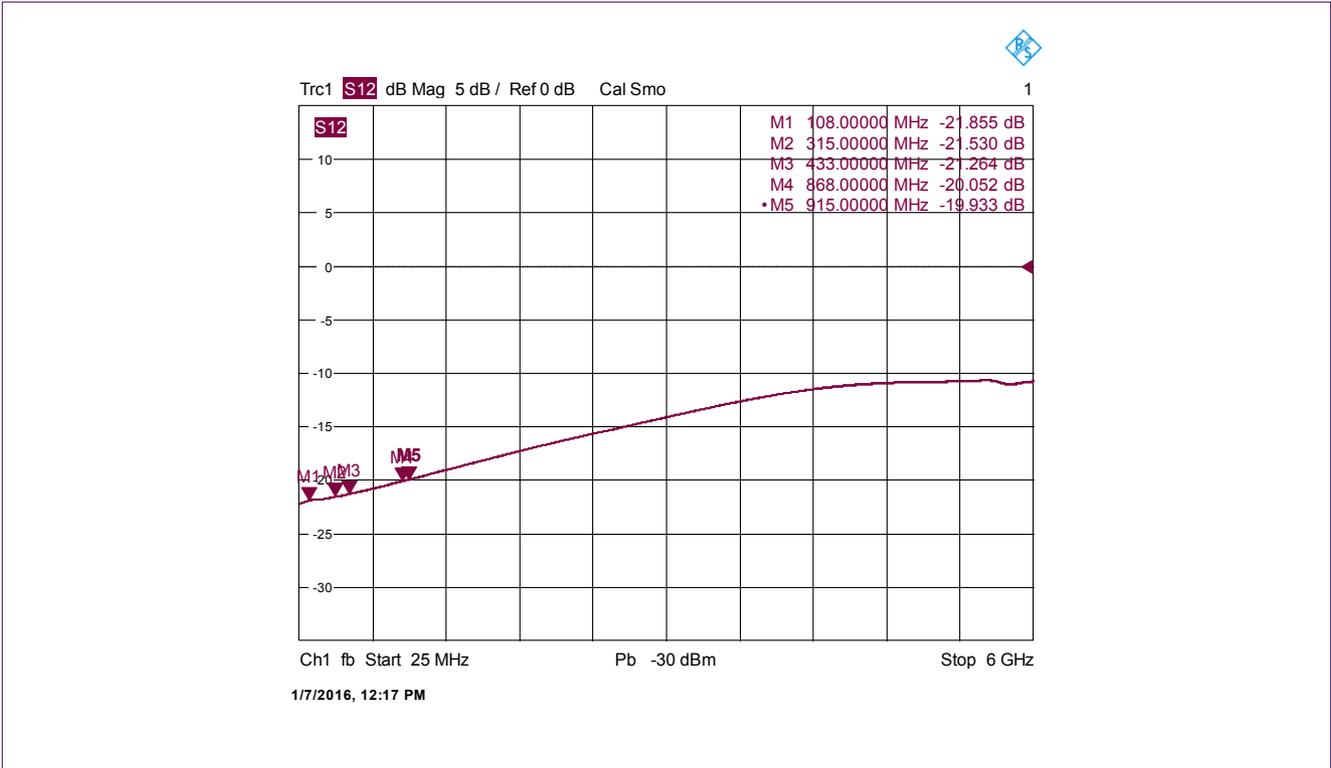


Fig 16. BFU520W “Type 1” RKE LNA, Reverse Isolation

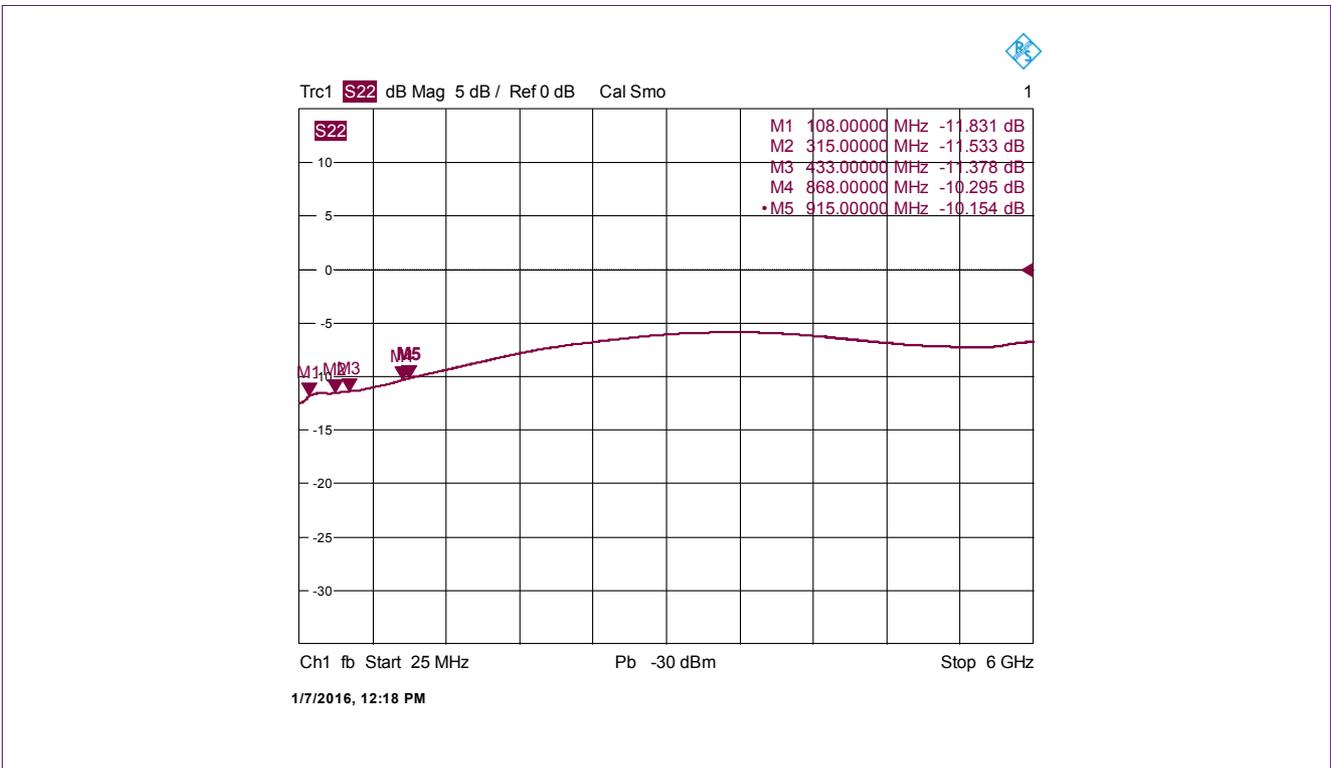


Fig 17. BFU520W “Type 1” RKE LNA, Output Return Loss. Note broadband / wideband matching.

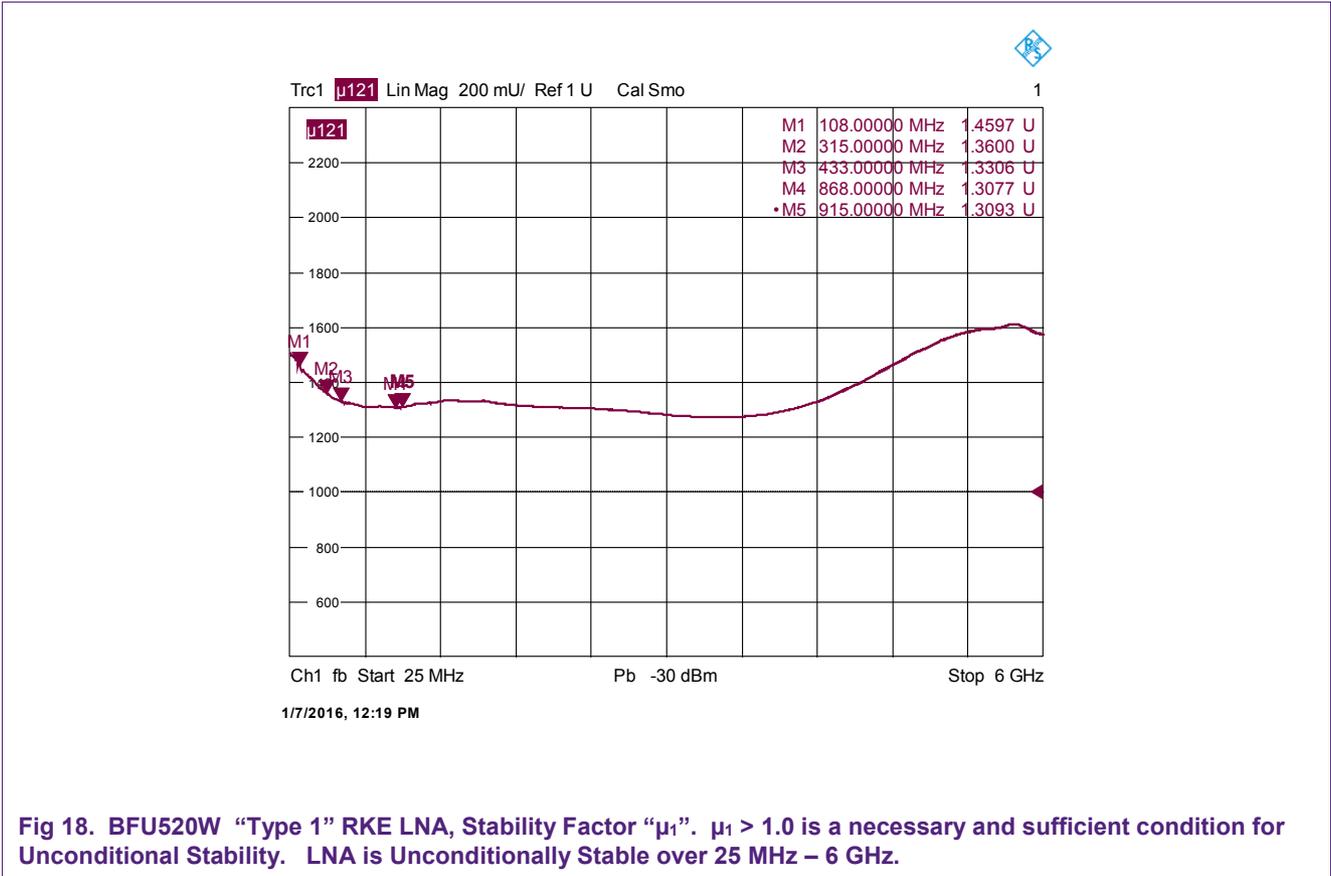


Fig 18. BFU520W “Type 1” RKE LNA, Stability Factor “ $\mu_1$ ”.  $\mu_1 > 1.0$  is a necessary and sufficient condition for Unconditional Stability. LNA is Unconditionally Stable over 25 MHz – 6 GHz.

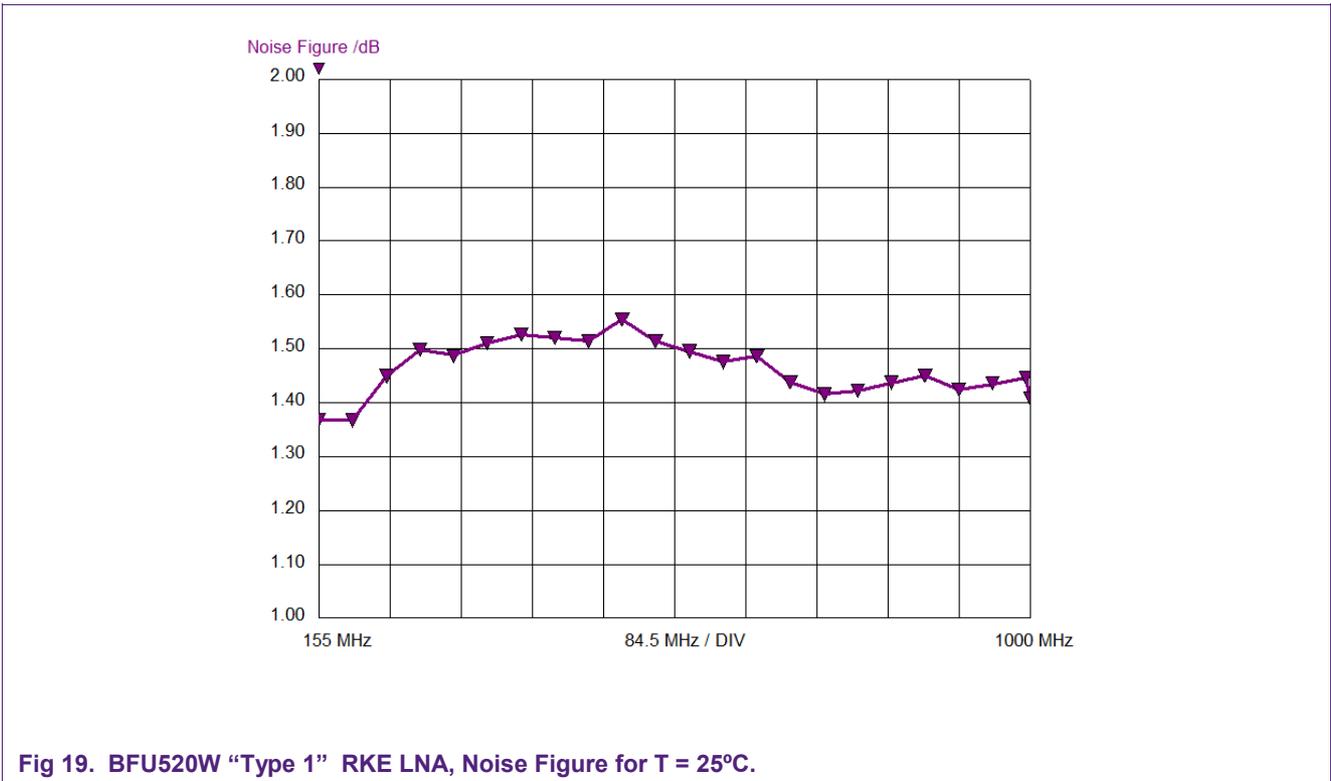


Fig 19. BFU520W “Type 1” RKE LNA, Noise Figure for T = 25°C.

### 4. Typical Application Board Results, “Type 2” LNA for Keyfob Applications (1.9 – 3.6 Volts, 3.2 mA @ 2.5 V)

This section shows results of a typical “Type 2” BFU520W RKE LNA, used for placement in a Keyfob, running from a coin cell battery. Intended voltage range is ~ 3.6 volts when battery is fully charged, down to ~ 1.9 volts at end of battery life. Data for T=25°C, for both 315 & 433 MHz is summarized at 1.9, 2.5, 3.0 and 3.6 volts in Figure 20. Schematic Diagram & BOM are given in Figures 21 & 22. Note, only resistor value changes are needed moving from Type 1 => Type 2 configuration.

| Frequency (MHz) | Supply Voltage V <sub>CC</sub> (Volts) | LNA Current (mA) | LNA V <sub>CE</sub> (Volts) | dB[s11] <sup>2</sup> | dB[s21] <sup>2</sup> | dB[s22] <sup>2</sup> | Noise Figure (dB) † | Input P <sub>1dB</sub> (dBm) | Output P <sub>1dB</sub> (dBm) | Comments                                       |
|-----------------|--|------------------|-----------------------------|----------------------|----------------------|----------------------|---------------------|------------------------------|-------------------------------|--|
| 315             | 1.9                                    | 2.09             | 1.24                        | -6.5                 | 11.7                 | -9.6                 | 1.8                 | --                           | ---                           | Gain, NF significantly degraded @ 1.9V / 2.1mA |
|                 | 2.5                                    | 3.21             | 1.49                        | -9.4                 | 14.2                 | -12.7                | 1.6                 | --                           | ---                           | “Nominal” operation point                      |
|                 | 3.0                                    | 4.14             | 1.70                        | -11.8                | 15.4                 | -15.0                | 1.5                 | --                           | ---                           |  |
|                 | 3.6                                    | 5.25             | 1.94                        | -14.8                | 16.5                 | -18.4                | 1.5                 | --                           | ---                           | Good Gain if battery charged                   |
| 433             | 1.9                                    | 2.09             | 1.24                        | -6.7                 | 11.2                 | -9.8                 | 1.8                 | -22.8                        | -12.6                         | Gain, NF significantly degraded @ 1.9V / 2.1mA |
|                 | 2.5                                    | 3.21             | 1.49                        | -9.7                 | 13.5                 | -12.6                | 1.6                 | -21.5                        | -9.0                          | “Nominal” operation point                      |
|                 | 3.0                                    | 4.14             | 1.70                        | -11.9                | 14.7                 | -15.1                | 1.5                 | -20.4                        | -6.7                          |  |
|                 | 3.6                                    | 5.25             | 1.94                        | -14.5                | 15.6                 | -17.9                | 1.5                 | -19.2                        | -4.6                          | Good Gain if battery charged                   |

Fig 20. Summary of data for “Type 2” BFU520W RKE LNA, for T=25°C, at 1.9, 2.5, 3.0 & 3.6 Volts.

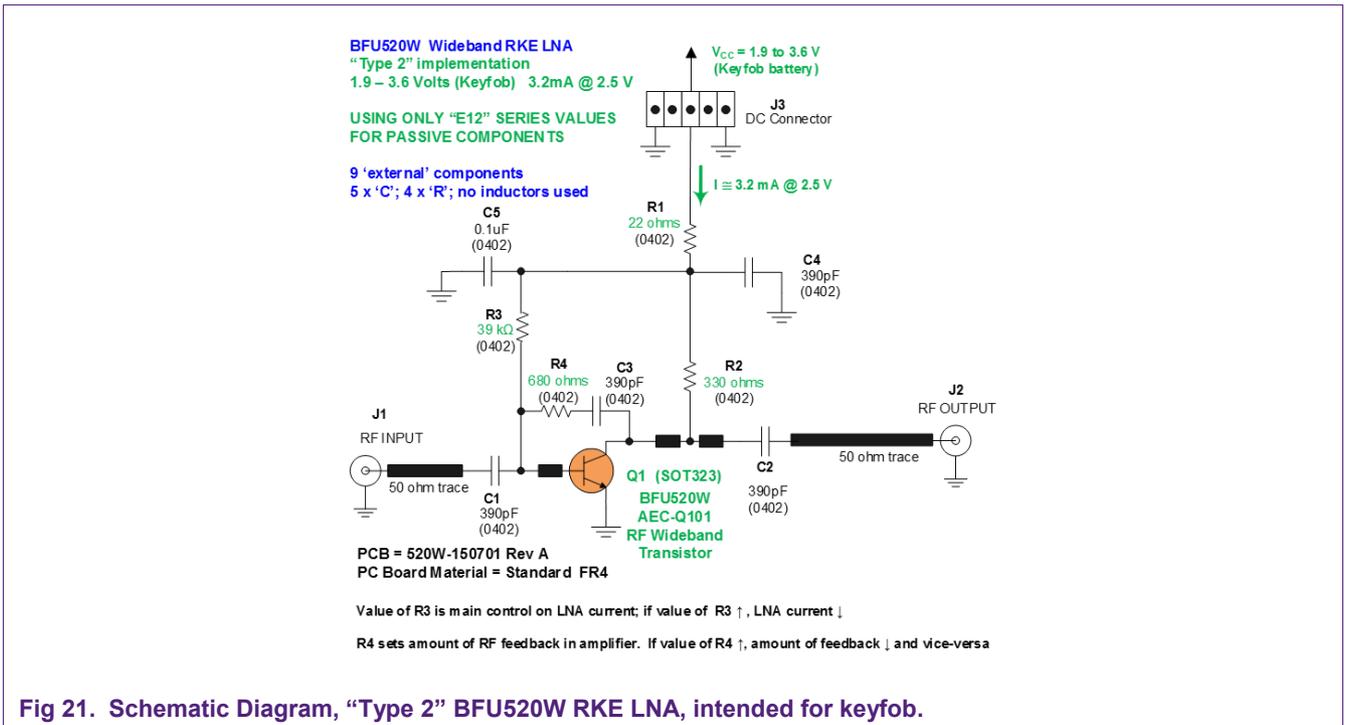


Fig 21. Schematic Diagram, “Type 2” BFU520W RKE LNA, intended for keyfob.

| Reference      | Value  | Description / Function   |
|----------------|--------|--|
| Q1             | -      | Active Device NXP BFU520W RF wideband Transistor, AEC-Q101 Qualified, SOT323 package   |
| C1, C2, C3, C4 | 390 pF | Input & Output DC blocks (C1, C2); DC Block for RF Feedback path (C3); power supply decoupling (C4)  |
| C5             | 0.1 μF | Low-frequency decoupling   |
| R1             | 22 Ω   | DC bias resistor; provides some DC negative feedback to DC operating point to compensate for changes in Q1's $h_{FE}$ over temperature, etc.   |
| R2             | 330 Ω  | "RF Choke" for collector (RF output) of Q1; lower cost than an inductor Trade-off: 'softer' Gain Compression curve, some loss of linearity   |
| R3             | 39kΩ   | DC bias feed to base of Q1; primary resistor for setting Q1 collector current; adjust $I_C$ by varying this value  |
| R4             | 680 Ω  | RF negative feedback to amp; when value of R4 ↓, amount of feedback is increased & vice-versa. Can decrease LNA gain by making value of R4↓. But, more feedback makes Noise Figure ↑ |

Fig 22. Bill Of Material (BOM) for "Type 2" BFU520W RKE LNA intended for Keyfob.

#### 4.1 Supply current, S-Parameters, Stability Factor and Noise Figure over battery voltage (~ 3.6 volts down to ~ 1.9 volts) "Type 2" LNA

Data for the "Type 2" Keyfob-type BFU520W RKE LNA is presented in this section, showing how the LNA operating current and RF parameters vary over battery voltage at T=25°C. The main conclusions are as follows:

- 1) **LNA current** varies from ~ 2.1 – 5.3mA over 1.9 – 3.6 volt battery voltage range
- 2) **Gain** stays between 14 – 17 dB at 315 / 433 MHz for 2.5 – 3.6 volts; Gain drops to 11 – 12 dB at 1.9 volts
- 3) **Noise Figure** remains fairly constant between 2.5 – 3.6 volts, with ~ 0.3 dB degradation at 1.9 volts
- 4) **Unconditional Stability** is maintained across entire 1.9 – 3.6 volt range
- 5) **Impedance Match** degrades as supply voltage (and thus LNA current) decreases, with the most severe change occurring from 2.5 => 1.9 volts

**Figure 23** shows LNA current variation over battery voltage range. **Figure 24** shows LNA Input Return Loss vs voltage, and **Figure 25, 26 & 27** show Gain, Reverse Isolation, and Output Return Loss vs. voltage, respectively. The stability factor  $\mu_1$  of the amplifier at each of the four voltages tested is shown in **Figures 28 – 31**. Noise Figure at each test voltage is shown in **Figures 32 – 35**.

| Supply Voltage $V_{CC}$ (Volts) | LNA Current (mA) | BFU520W $V_{CE}$ (Volts) | Comment              |
|---------------------------------|------------------|--------------------------|----------------------|
| 1.9                             | 2.09             | 1.24                     |                      |
| 2.5                             | 3.21             | 1.49                     | Nominal, 'set point' |
| 3.0                             | 4.14             | 1.70                     |                      |
| 3.6                             | 5.25             | 1.94                     |                      |

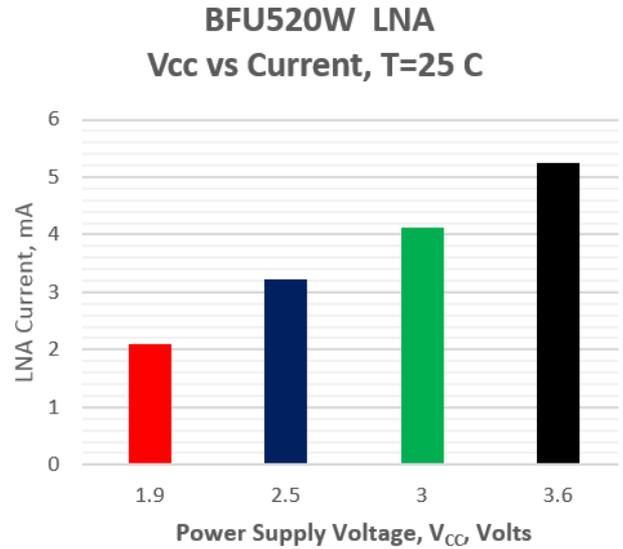


Fig 23. Variation in LNA current & collector-emitter voltage vs. battery voltage for a “Type 2” BFU520W RKE Keyfob LNA.

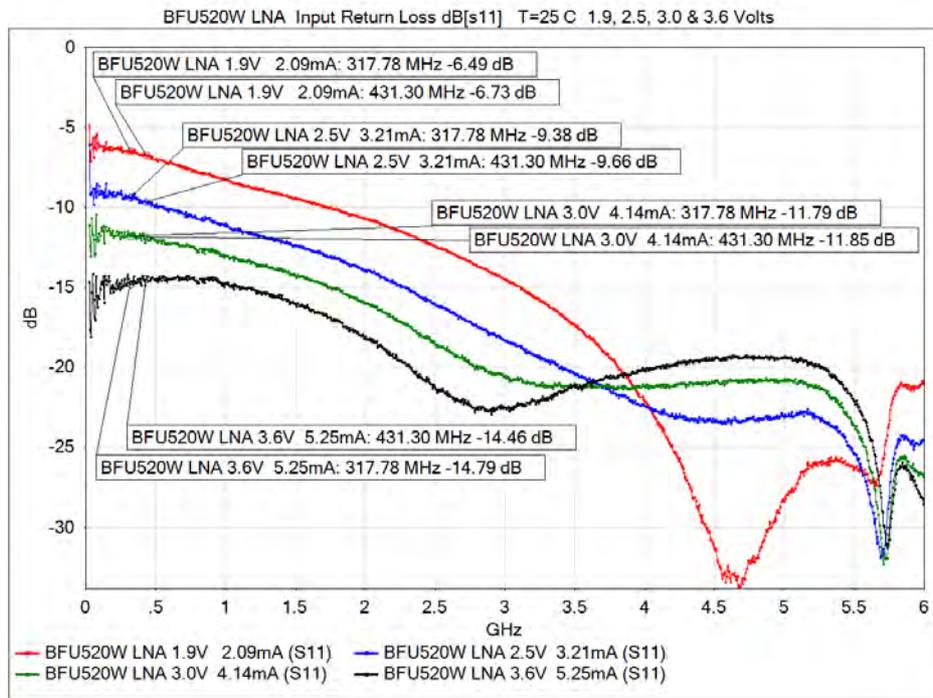


Fig 24. Input Return Loss vs Battery Voltage for a “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz. Note, input match degrades as voltage decreases.

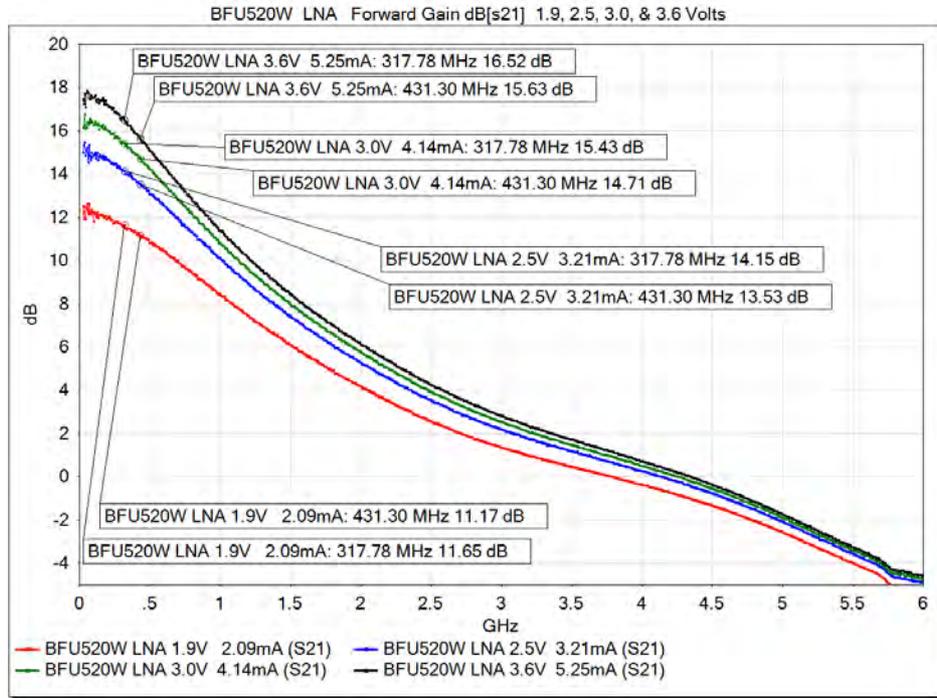


Fig 25. Gain vs Battery Voltage for a “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz. We see a total gain variation of ~ -4.5 dB at 315 or 433 MHz as voltage decreases from 3.6 V down to 1.9V.

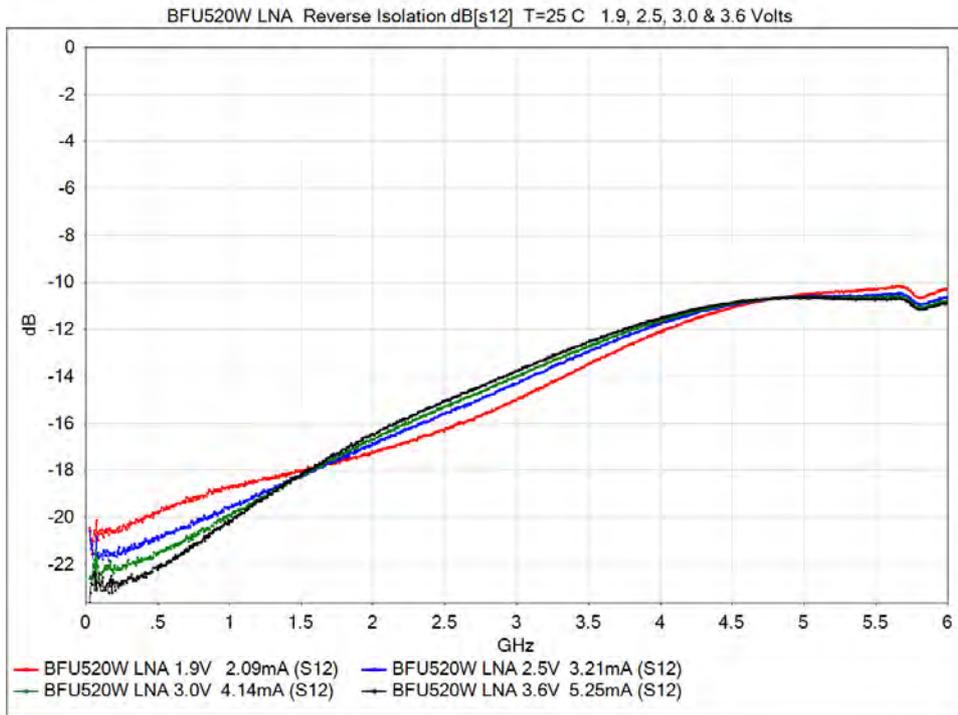


Fig 26. Reverse Isolation vs Battery Voltage for a “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.

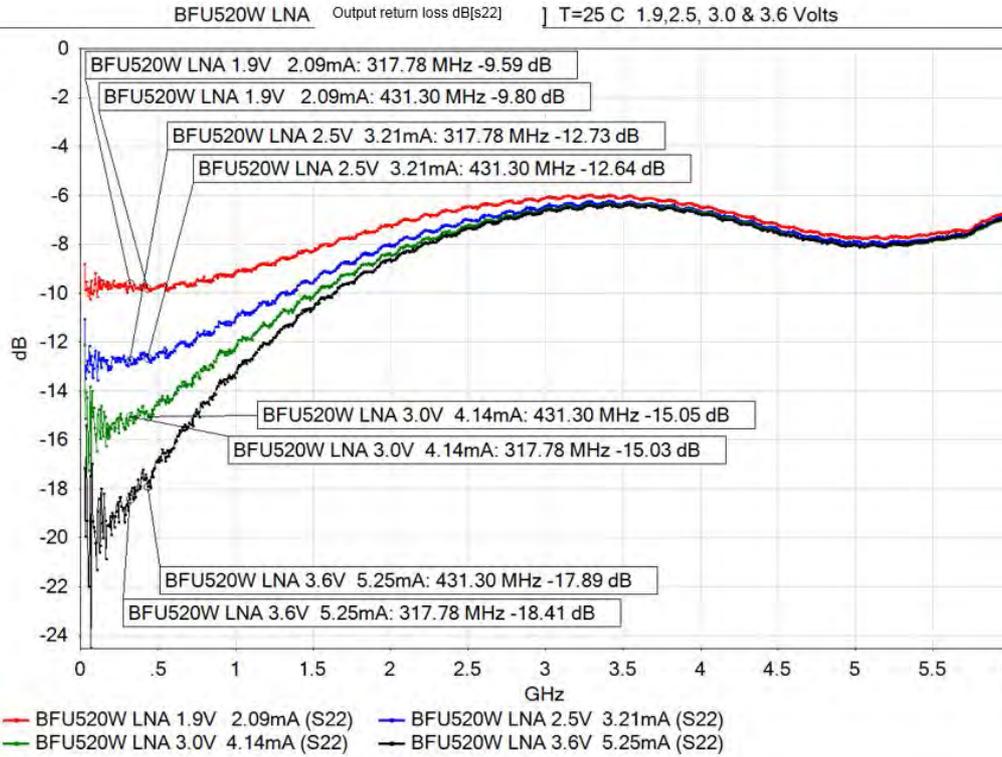


Fig 27. Output Return Loss vs Battery Voltage for a “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.

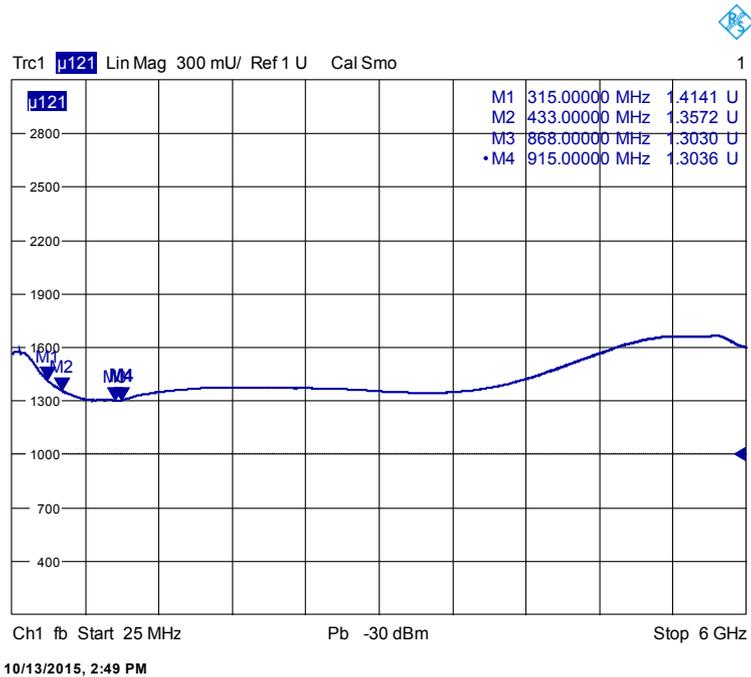


Fig 28. Stability factor  $\mu_1$  at 1.9 volts, “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.

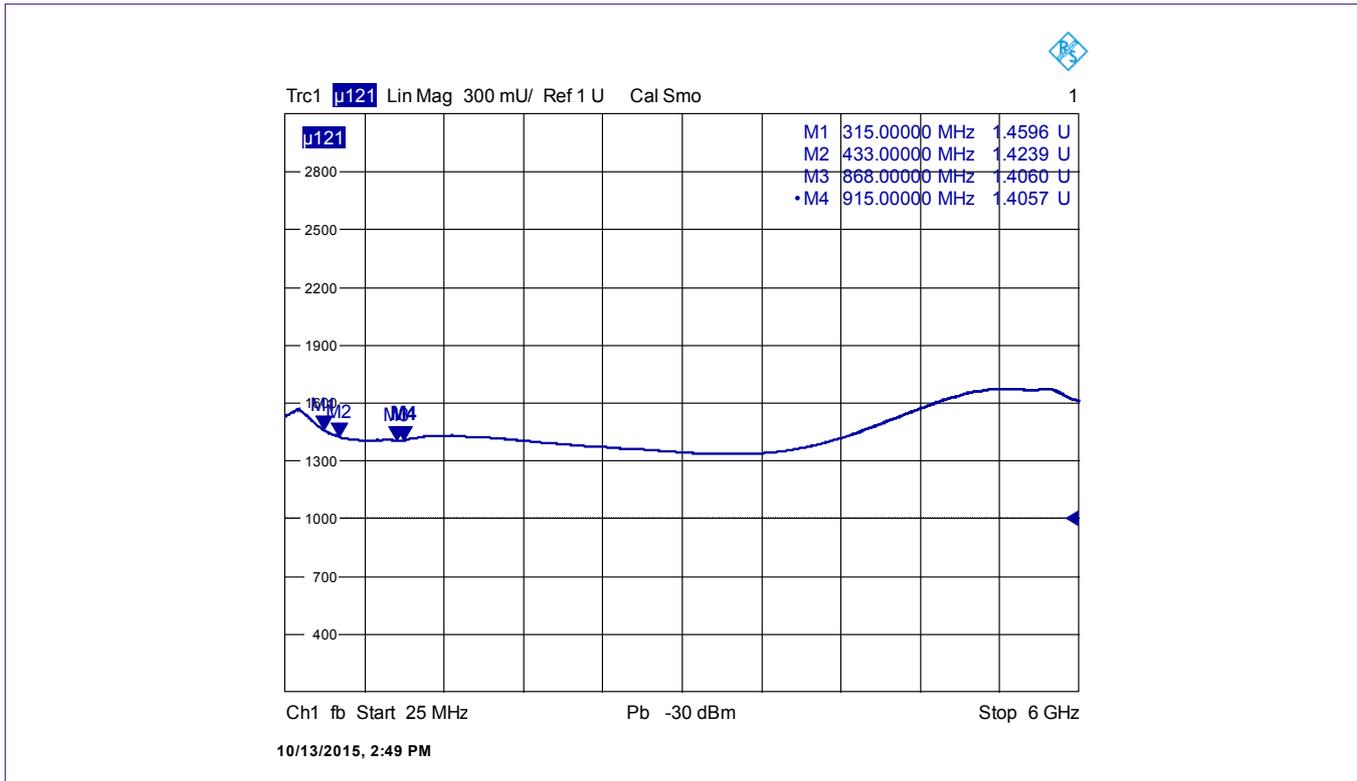


Fig 29. Stability factor  $\mu_1$  at 2.5 volts, “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.

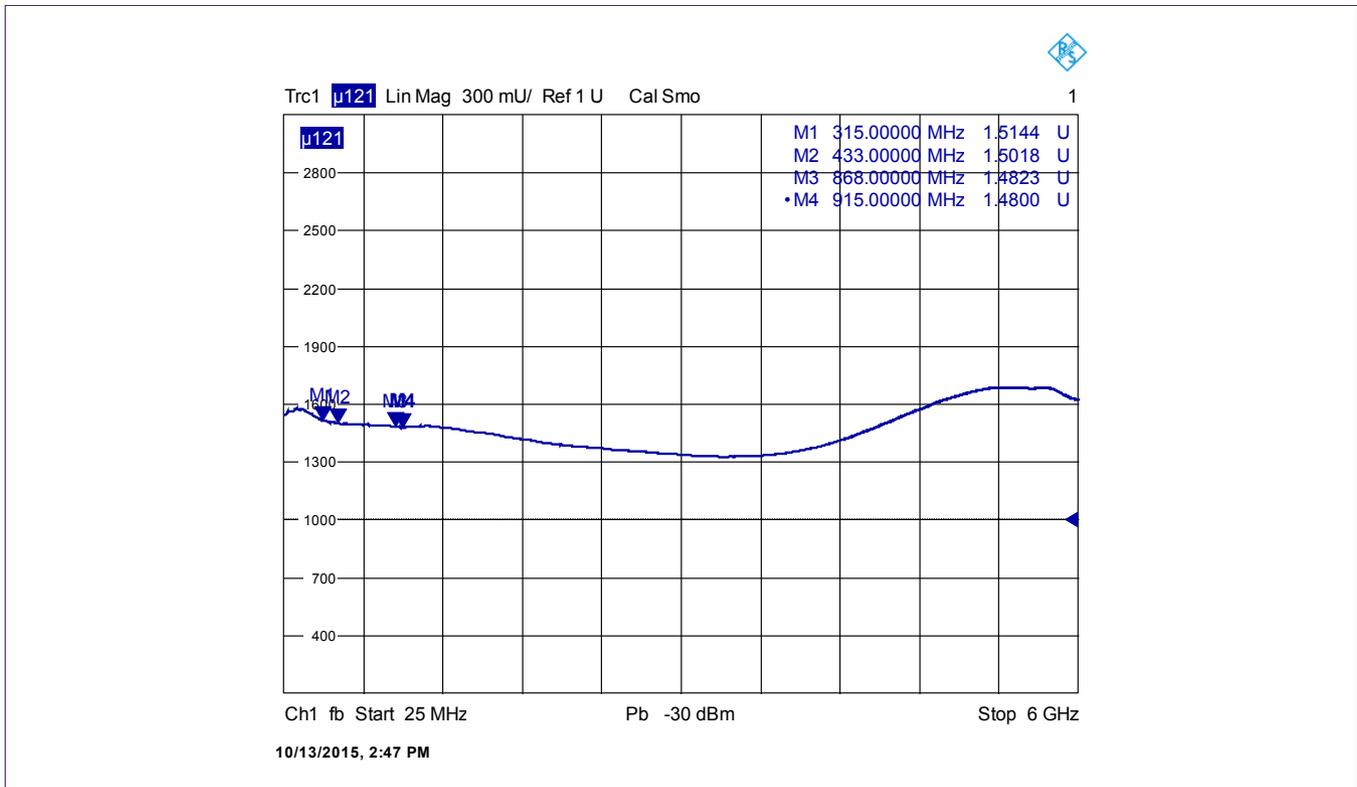


Fig 30. Stability factor  $\mu_1$  at 3.0 volts, “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.

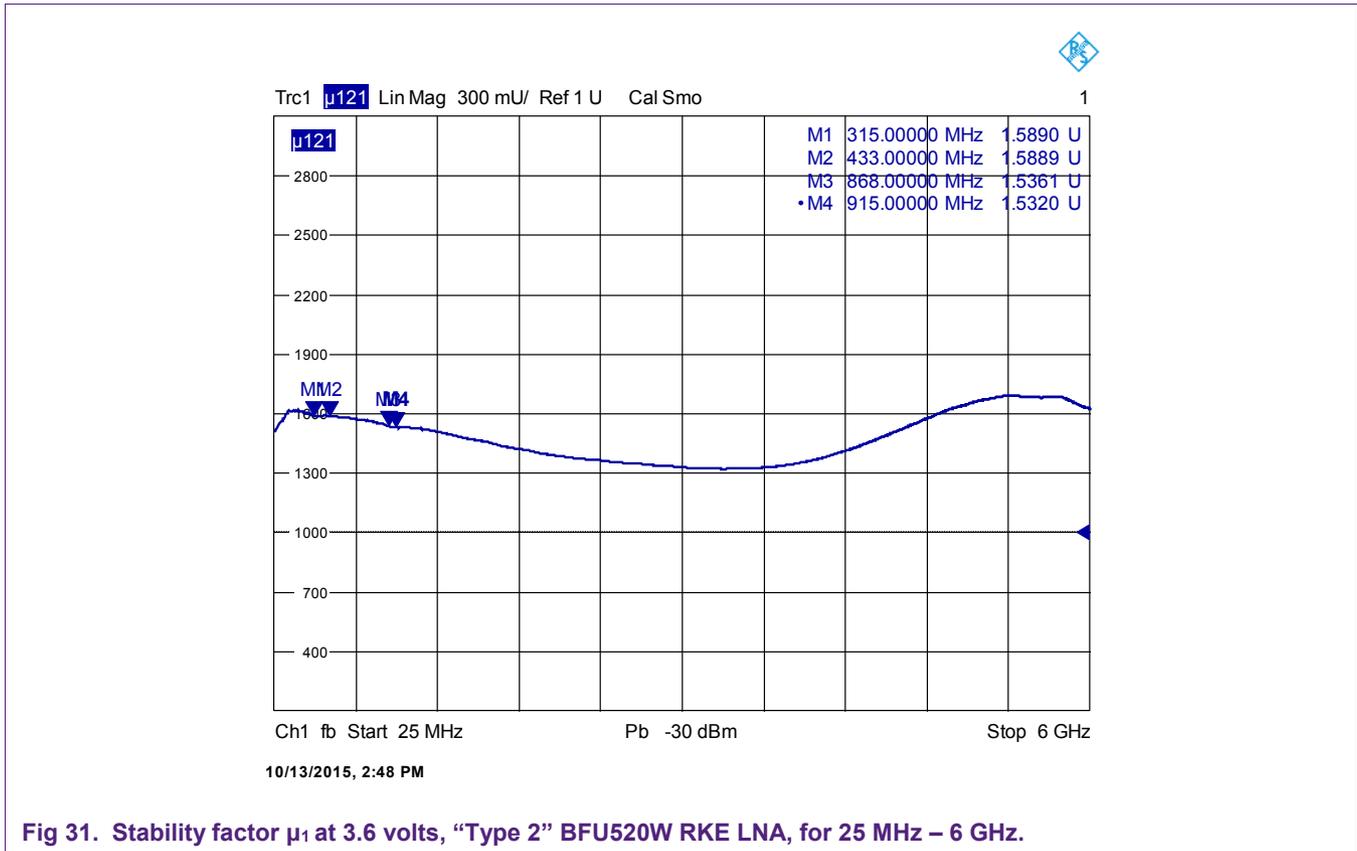


Fig 31. Stability factor  $\mu_1$  at 3.6 volts, “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.

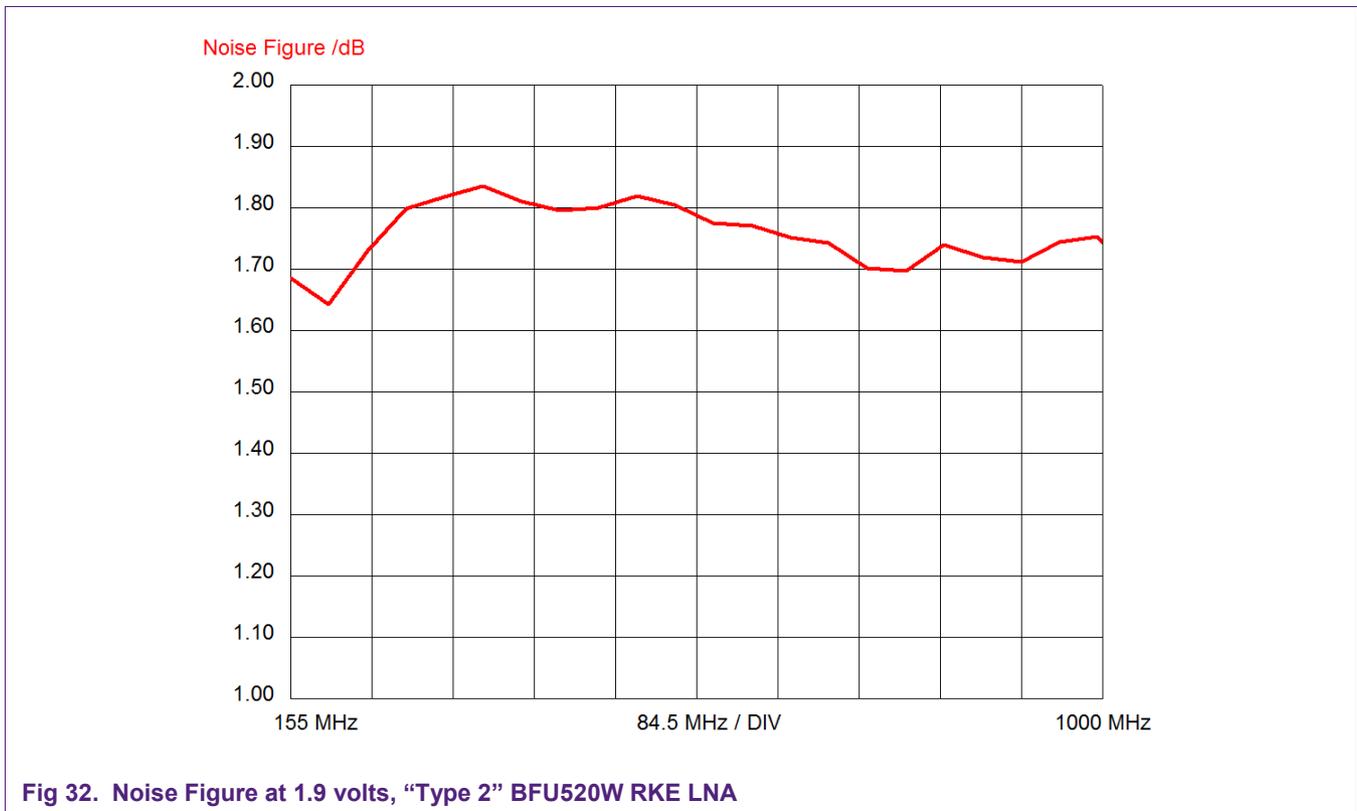


Fig 32. Noise Figure at 1.9 volts, “Type 2” BFU520W RKE LNA

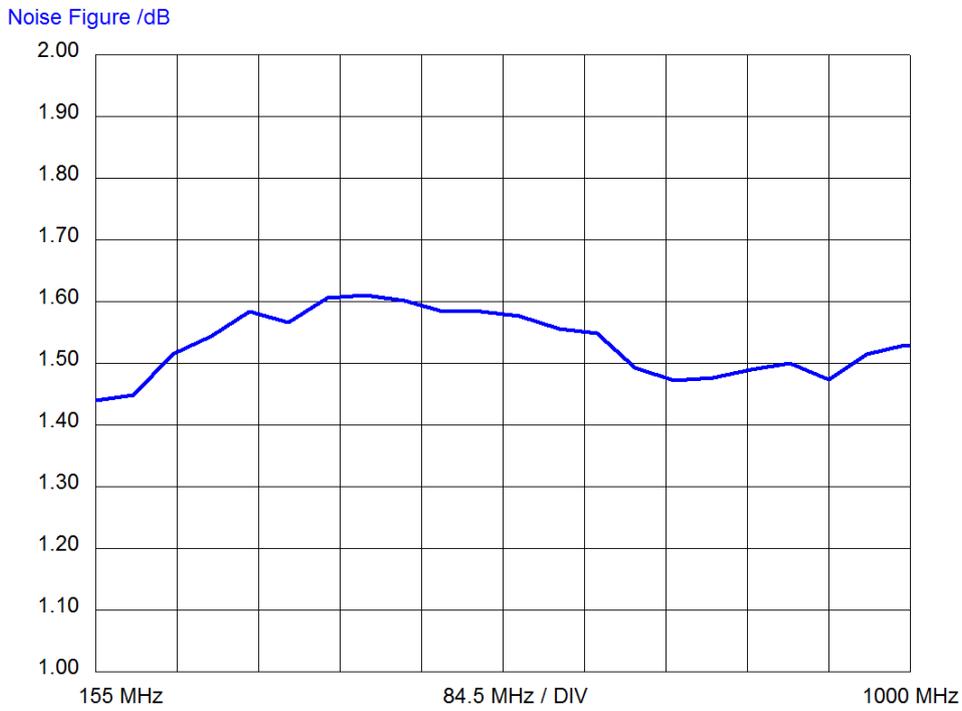


Fig 33. Noise Figure at 2.5 volts, “Type 2” BFU520W RKE LNA

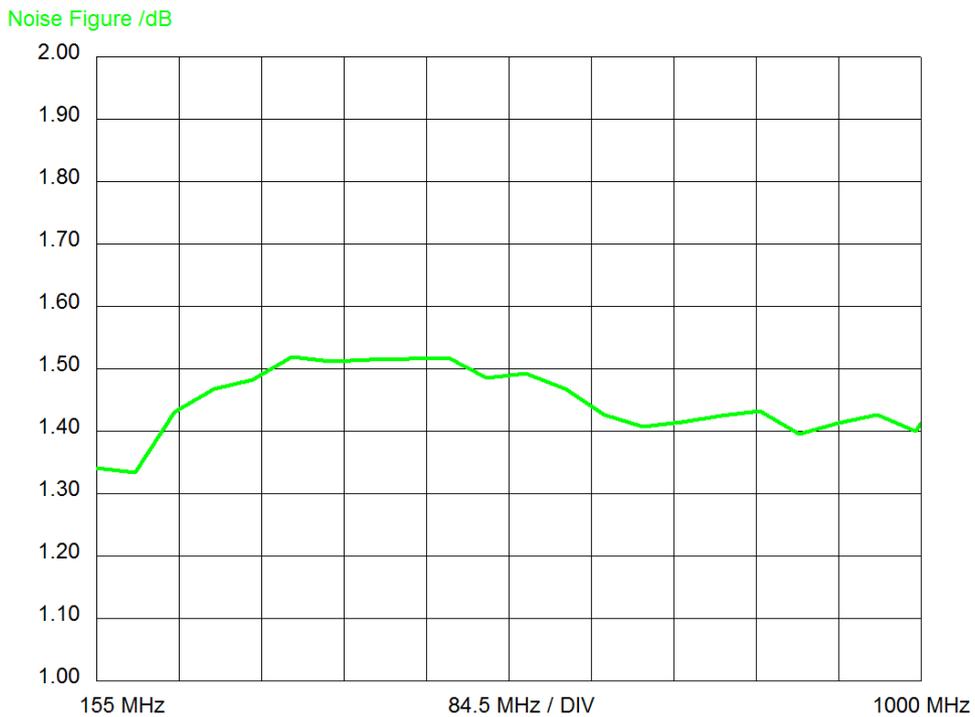


Fig 34. Noise Figure at 3.0 volts, “Type 2” BFU520W RKE LNA

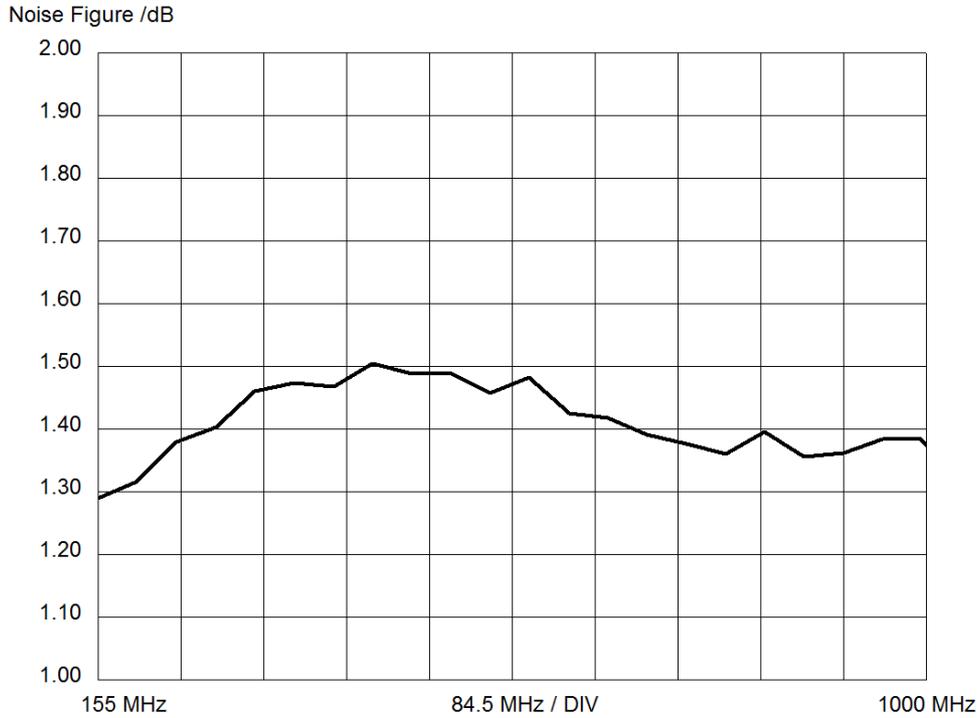


Fig 35. Noise Figure at 3.6 volts, “Type 2” BFU520W RKE LNA

## 5. Information on BFU520W RKE LNA Customer Evaluation Kits

There are two (2) types of fully populated and tested BFU520W RKE LNA Customer Evaluation Kits available, one for each of the “Type 1” and “Type 2” demos described in this applications note. Each kit has a PC board and some extra BFU520W device samples in it. Please reference the information below when placing an order for a Customer Evaluation Kit through your NXP Sales Representative.

| Name                | Description  | Artf   | OM-            | 12NC              |
|---------------------|--|--------|----------------|-------------------|
| <b>BFU520W-RKE1</b> | <b>Type 1</b><br>In-vehicle<br>(5 volt, 3.5mA)                         | 157556 | <b>OM17022</b> | 12NC 934070272598 |
| <b>BFU520W-RKE2</b> | <b>Type 2</b><br>For Keyfob<br>(1.9 – 3.6 volts,<br>3.2mA @ 2.5 Volts) | 162023 | <b>OM17023</b> | 12NC 934070273598 |

## 6. Legal information

### 6.1 Definitions

**Draft** — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

### 6.2 Disclaimers

**Limited warranty and liability** — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

**Right to make changes** — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

**Suitability for use** — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from national authorities.

**Evaluation products** — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

### 6.3 Licenses

#### Purchase of NXP <xxx> components

<License statement text>

### 6.4 Patents

Notice is herewith given that the subject device uses one or more of the following patents and that each of these patents may have corresponding patents in other jurisdictions.

<Patent ID> — owned by <Company name>

### 6.5 Trademarks

Notice: All referenced brands, product names, service names and trademarks are property of their respective owners.

<Name> — is a trademark of NXP B.V.

## 7. List of figures

|  |    |  |    |
|--|----|--|----|
| Fig 1. Overview of BFU5xxx family of RF Transistors.   | 3  | Fig 24. Input Return Loss vs Battery Voltage for a “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz. Note, input match degrades as voltage decreases.  | 16 |
| Fig 2. World-wide frequency bands in use for RKE applications.   | 4  | Fig 25. Gain vs Battery Voltage for a “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz. We see a total gain variation of ~ -4.5 dB at 315 or 433 MHz as voltage decreases from 3.6 V down to 1.9V. | 17 |
| Fig 3. Example automotive RKE receiver block which would be placed in a vehicle. Note low-cost wire antenna, which is bent & folded to fit the available space. This implementation is far less efficient than our classic $\lambda/2$ dipole used as a reference. Size and cost limitations adversely affect antenna efficiency, reducing RKE system range. | 4  | Fig 26. Reverse Isolation vs Battery Voltage for a “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.   | 17 |
| Fig 4. Options and constraints for increasing RKE system range.  | 5  | Fig 27. Output Return Loss vs Battery Voltage for a “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.  | 18 |
| Fig 5. Friis’ formula for calculation of overall or ‘cascaded’ noise figure of a receiver.   | 6  | Fig 28. Stability factor $\mu_1$ at 1.9 volts, “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.   | 18 |
| Fig 6. “Type 1” and “Type 2” BFU520W External LNA Variants.  | 7  | Fig 29. Stability factor $\mu_1$ at 2.5 volts, “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.   | 19 |
| Fig 7. Cross-sectional diagram of BFU520W External RKE LNA Board   | 7  | Fig 30. Stability factor $\mu_1$ at 3.0 volts, “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.   | 19 |
| Fig 8. Photo of assembled BFU520W LNA PC board. Measurement reference planes for data shown in this document are as shown at RF connectors unless otherwise indicated.   | 8  | Fig 31. Stability factor $\mu_1$ at 3.6 volts, “Type 2” BFU520W RKE LNA, for 25 MHz – 6 GHz.   | 20 |
| Fig 9. Close-in photo of PC board with ‘0402’ case-size resistors and capacitors used.   | 8  | Fig 32. Noise Figure at 1.9 volts, “Type 2” BFU520W RKE LNA  | 20 |
| Fig 10. Summary of measurement data for “Type 1” BFU520W LNA.  | 9  | Fig 33. Noise Figure at 2.5 volts, “Type 2” BFU520W RKE LNA  | 21 |
| Fig 11. Schematic Diagram, “Type 1” BFU520W LNA.   | 9  | Fig 34. Noise Figure at 3.0 volts, “Type 2” BFU520W RKE LNA  | 21 |
| Fig 12. Bill Of Material (BOM, for Type 1 BFU520W RKE LNA (5 volt, 3.2mA variant).   | 10 | Fig 35. Noise Figure at 3.6 volts, “Type 2” BFU520W RKE LNA  | 22 |
| Fig 13. Parts placement on PC Board for both “Type 1” and “Type 2” BFU520W LNAs.   | 10 |  |    |
| Fig 14. BFU520W “Type 1” RKE LNA, Input Return Loss. Note broadband / wideband matching.   | 11 |  |    |
| Fig 15. BFU520W “Type 1” RKE LNA, Forward Gain   | 11 |  |    |
| Fig 16. BFU520W “Type 1” RKE LNA, Reverse Isolation  | 12 |  |    |
| Fig 17. BFU520W “Type 1” RKE LNA, Output Return Loss. Note broadband / wideband matching.  | 12 |  |    |
| Fig 18. BFU520W “Type 1” RKE LNA, Stability Factor “ $\mu_1$ ”. $\mu_1 > 1.0$ is a necessary and sufficient condition for Unconditional Stability. LNA is Unconditionally Stable over 25 MHz – 6 GHz.  | 13 |  |    |
| Fig 19. BFU520W “Type 1” RKE LNA, Noise Figure for T = 25°C.   | 13 |  |    |
| Fig 21. Schematic Diagram, “Type 2” BFU520W RKE LNA, intended for keyfob.  | 14 |  |    |
| Fig 22. Bill Of Material (BOM) for “Type 2” BFU520W RKE LNA intended for Keyfob.   | 15 |  |    |

## 8. Contents

---

|     |   |           |
|-----|---|-----------|
| 1.  | <b>Introduction .....</b>   | <b>3</b>  |
| 2.  | <b>Automotive RKE application constraints, the ‘range problem’ and BFU520W LNA Design .....</b>   | <b>4</b>  |
| 2.1 | BFU520W External Automotive RKE LNA Design Targets .....  | 6         |
| 2.2 | PC Board Details, both LNA Types .....  | 7         |
| 3.  | <b>Typical Application Board Test Results, “Type 1” LNA (5 Volts, 3.5mA) .....</b>  | <b>9</b>  |
| 3.1 | S-Parameters, Stability Factor and Noise Figure, “Type 1” LNA .....   | 11        |
| 4.  | <b>Typical Application Board Results, “Type 2” LNA for Keyfob Applications (1.9 – 3.6 Volts, 3.2 mA @ 2.5 V) .....</b>                    | <b>14</b> |
| 4.1 | Supply current, S-Parameters, Stability Factor and Noise Figure over battery voltage (~ 3.6 volts down to ~ 1.9 volts) “Type 2” LNA ..... | 15        |
| 5.  | <b>Information on BFU520W RKE LNA Customer Evaluation Kits .....</b>  | <b>22</b> |
| 6.  | <b>Legal information .....</b>  | <b>23</b> |
| 6.1 | Definitions .....   | 23        |
| 6.2 | Disclaimers .....   | 23        |
| 6.3 | Licenses .....  | 23        |
| 6.4 | Patents .....   | 23        |
| 6.5 | Trademarks .....  | 23        |
| 7.  | <b>List of figures .....</b>  | <b>24</b> |
| 8.  | <b>Contents .....</b>   | <b>25</b> |

---

Please be aware that important notices concerning this document and the product(s) described herein, have been included in the section 'Legal information'.

---