

AN13732

PCA9482UK 6 A 2:1, 1:2, and 1:1 mode switched capacitor direct charger

Rev. 1.2 — 3 August 2023

Application note

Document information

Information	Content
Keywords	6 A 2:1/1:2/1:1 mode switched capacitor; PCA9482UK
Abstract	Many mobile phones have adopted features requiring high system performance, such as 5G, multiple cameras, and high resolution LCDs with multi-processors, increasing the demand for higher battery capacity. These power-hungry features have created the need for users to charge their mobile phone batteries frequently and quickly. Legacy inductor-based chargers are still widely used in mobile applications, but the high heat from induction charging limits higher charging power for the battery. These chargers are unable to satisfy users who require fast charging. Switched-capacitor (SC) direct charging has been recognized as a good replacement for inductor-based charging, because of its higher efficiency and lower heat dissipation.



Revision history

Revision history

Rev	Date	Description
1.2	20230803	Section 3.4 : Added comment on min/max AVDD voltage
1.1	20230227	Section 3.2 : Added "nINT pin can be floating or open if not used."
1	20220927	Initial release.

1 Introduction

Many mobile phones have adopted features requiring high system performance, such as 5G, multiple cameras, and high resolution LCDs with multi-processors, increasing the demand for higher battery capacity. These power-hungry features have created the need for users to charge their mobile phone batteries frequently and quickly.

Legacy inductor-based chargers are still widely used in mobile applications, but the high heat from induction charging limits higher charging power for the battery. These chargers are unable to satisfy users who require fast charging.

Switched-capacitor (SC) direct charging has been recognized as a good replacement for inductor-based charging, because of its higher efficiency and lower heat dissipation. Fast direct chargers have become mandatory in many mobile phones, including low-tier models.

PCA9482UK achieves best-in-class SC direct charging in terms of efficiency, with lower BOMs.

This application note provides details for possible customer applications, including external components.

2 PCA9482UK Charging application

2.1 30 W charging application

The input current at VBUS can reach 3 A, which is half of the maximum output current. A single PCA9482UK can support 30 W charging without an additional SC converter.

An example of the charging block is shown in [Figure 1](#).

 


Figure 1. PCA9482UK charging application with single SC converter

2.2 Guidance for monitoring status and interrupt for IVIN and IBAT regulation

PCA9482UK has input and charging current (IVIN and IBAT) regulation features. Both regulation features are used to limit input and battery charging current, in order to not exceed allowable input and charging current that are programmed at each register.

Input current is monitored at current sense circuit at OVPFET, and charging current is sensed at an external series sense resistor located at one of battery terminals. Sensed current is converted to voltage for gate control of OVPFET, and input current and charging current are regulated to the programmed limits when they exceed programmed current.

Corresponding status and interrupt bits indicate when current regulation happens. There is a fixed offset between real regulation and the threshold of the status and interrupt settings, so that real regulation happens after an interrupt is triggered and its status bit changes. The status bit, though, is repeatedly toggled around the threshold of status for input and charging current regulation, due to current ripple through OVPFET and the external sense resistor.

In an application, the system recognizes any set of interrupt and corresponding status for current regulation, and adjusts input current and voltage to exit the regulation condition. If the moment when the current regulation status bit is toggling should be ignored, though, then a repetition of reading the status register value three to five times is required. This would detect when the status bit stops toggling and settles on a particular status.

2.3 Guidance for IVIN ADC in reverse 1:1 and 1:2 mode

PCA9482UK supports an input current monitoring feature in forward 2:1 and 1:1 switching operations, using an ADC function.

When an IVIN ADC function in reverse 1:1 and 1:2 mode is needed for certain applications, PCA9482UK can also support that, using the following register settings and calculations.

1. Register settings
 - a. Set ADC_EN bit in address 0x2Ah to 1b to enable ADC function.
 - b. Set ADC_READ_VIN_CURRENT_EN bit in address 0x2Bh to 1b to enable IVIN ADC feature.
 - c. Read address 0x3Bh and 0x3Ch sequentially. ADC read should be low-byte (bit 7:0) first and then high byte (bit 11:8).
2. Calculation to convert from ADC readout to IVIN current (A):

IVIN Current (A) in reverse 1:2 and 1:1 mode = DEC[11 :0] x 0.00212

Note: [7:0] bits in address 0x3B are [7:0] of the 12 bit ADC read value and [3:0] bits in address 0x3C are [11:8] of the 12 bit ADC read value.

3 PCA9482UK reference schematic

3.1 Reference schematic with OVP IC

 


Figure 2. PCA9482UK reference schematic with OVP IC

3.2 I²C and other digital pins

PCA9482UK provides two options for the I²C address, determined by the ADDRESS pin setting, as shown in [Table 1](#).

Table 1. I²C addresses

ADDRESS	Address (write) in hex	Address (read) In hex
LOW	BA	BB
FLOAT	B8	B9

The I²C interface supports clock speeds up to 1 MHz. SDA and SCL should have a 2.2 kΩ pullup resistor.

The EN pin is the digital pin used to enable the device. The polarity of the EN pin can be selected using EN_CFG in register 0x18.

nINT is the open drain output, requiring a 220 kΩ pullup resistor. It goes low when any unmasked interrupt bit is asserted.

nINT pin can be floating or open if not used.

3.3 NTC

The NTC input with AVDD pull-up voltage is connected to an external negative temperature coefficient (NTC) thermistor to monitor system temperature, or to NTC on the battery package to monitor battery temperature. To utilize the NTC function, set NTC_EN bit to 1b. There are two registers that can be used to set a different temperature threshold, such as hot/warm and cold/cool. If one of two programmed thresholds is monitored, the device issues a corresponding interrupt signal.

3.4 AVDD

AVDD is the internal LDO output, requiring a 1 μF/6.3 V bypass capacitor. Typical AVDD is 1.536 V. Minimum and maximum AVDD are 1.53 V and 1.54 V, respectively.

3.5 Input capacitor selection

In switched capacitor converter application, large AC currents flow through the input/output capacitors. The input capacitor helps to keep the input voltage stable during a switching operation.

Low equivalent series resistance (ESR) ceramic capacitors are highly recommended for this application. Larger size X7R MLCC capacitors are normally recommended. Capacitance derating needs to be considered at a DC bias voltage.

3.6 Flying capacitor selection

Large AC currents flow through the flying capacitors. Low ESR ceramic capacitors are highly recommended for this application. The flying capacitor must be selected to accommodate the maximum load current. Larger size X7R MLCC capacitors are normally recommended. Capacitance derating needs to be considered at a DC bias voltage.

In general, a recommended voltage ripple at C_{FLY} is about 2% of output voltage. If the maximum output voltage is 5V, the ripple at C_{FLY} is 100 mV. The value of C_{FLY} can be obtained from the formula below in dual phase.

$$C_{FLY} (\mu F) = \frac{I_{OUT} (max)}{2 \times frequency \times \Delta V_{CFLY} (Voltage\ ripple)}$$

Where:

I_{OUT} (max): A maximum output current

ΔV_{CFLY}: voltage ripple on fly cap

Frequency: SC's operating frequency

2 x 22 μF is fully verified in application, and can support 30 W charging in a smartphone form factor without additional thermal dissipation measures..

3.7 Output capacitor selection

Large AC current flows through the flying capacitors and input/output capacitors. The average output current is given by the formula below.

$$I_{OUT} = 2 \times \text{Frequency} \times C_{FLY} \times \Delta V_{CFLY}$$

The total output voltage ripple is:

$$\Delta V_{OUT} = \frac{I_{OUT}}{2 \times \text{frequency} \times (C_{FLY} + C_{SC_OUT})}$$

A voltage ripple at C_{VOUT} should be determined using system requirements.

3.8 Bill of material (BOM)

[Table 2](#) shows all the components for the device.

Table 2. Bill of material

Name	Value	Size	Part Name / Maker	Note
C _{VIN}	4.7 μF/16 V	1608	Murata, GRM188C71C475ME21	C _{EFF} =1.4 μF at 10 V
	1 nF/25 V	0603	Murata, GRM033R61E102KA01	Optional for high frequency filter
C _{OVP_OUT}	10 μF/16 V	1608	Murata, GRM188R61C106KAAL	Two capacitors. C _{EFF} =1.7 μF for one capacitor at 10 V
C _{FLY}	22 μF/16 V	1608	SEMCO, CL10A226MO7JZNC	Two capacitors. C _{EFF} =6.9 μF at 5 V
C _{BST}	100 nF/16 V	0603	Murata, GRM033R61C104KE14	
C _{VOUT}	22 μF/10 V	1608	SEMCO, CL10A226MP8NUNE	Two capacitors. C _{EFF} =5 μF at 4.5 V
C _{AVDD}	1 uF/6.3 V	0603	Murata, GRM033D70J105ME01	C _{EFF} =0.88 μF at 1.5 V
R _{SENSE}	1/2/5 mΩ			for battery current
R _{I2C}	2.2 kΩ	0603		SCL and SDA
R _{nINT}	220 kΩ	0603		
NTC	β=4250 or β=3380	0603	NCP03WF104F05RL or NCP03XH103F05RL	Place it if needed

4 Layout Guides

4.1 PCB layout guidelines

The device has a dual phase converter with two flying capacitors on each phase. Here is a PCB layout priority list for proper layout.

It is essential that PCB layout is performed in this order.

1. Utilize 8-layer board for optimal layout, and assign one layer as solid ground plane near the device to minimize high-current path.

PCA9482UK 6 A 2:1, 1:2, and 1:1 mode switched capacitor direct charger

2. Place flying capacitors as close to CP1A, CP1B, CP1A_BOT and CP1B_BOT bumps as possible. The trace shall be wide enough to carry the charging and discharging current and short to minimize trace resistance which affects efficiency directly.
3. Place output capacitor as close as possible to VOUT bumps. Use as wide as possible on the 2nd layer to short VOUT from each phase.
4. Place input capacitors as close as possible to VIN and input power trace should be routed to center of VIN pins.
5. Place two OVP_OUT capacitors close to edge of bumps symmetrically.
6. Decoupling capacitors shall be placed next to the device and make trace connection as short as possible.
7. Ensure that there are sufficient thermal vias directly under bumps of the power FETs, power ground, connecting to copper on other layers.

 


Figure 3. PCA9482UK recommended PCB layout

5 Legal information

5.1 Definitions

Draft — A draft status on a document indicates that the content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included in a draft version of a document and shall have no liability for the consequences of use of such information.

5.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Terms and conditions of commercial sale — NXP Semiconductors products are sold subject to the general terms and conditions of commercial sale, as published at <http://www.nxp.com/profile/terms>, unless otherwise agreed in a valid written individual agreement. In case an individual agreement is concluded only the terms and conditions of the respective agreement shall apply. NXP Semiconductors hereby expressly objects to applying the customer's general terms and conditions with regard to the purchase of NXP Semiconductors products by customer.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Suitability for use in non-automotive qualified products — Unless this document expressly states that this specific NXP Semiconductors product is automotive qualified, the product is not suitable for automotive use. It is neither qualified nor tested in accordance with automotive testing or application requirements. NXP Semiconductors accepts no liability for inclusion and/or use of non-automotive qualified products in automotive equipment or applications.

In the event that customer uses the product for design-in and use in automotive applications to automotive specifications and standards, customer (a) shall use the product without NXP Semiconductors' warranty of the product for such automotive applications, use and specifications, and (b) whenever customer uses the product for automotive applications beyond NXP Semiconductors' specifications such use shall be solely at customer's own risk, and (c) customer fully indemnifies NXP Semiconductors for any liability, damages or failed product claims resulting from customer design and use of the product for automotive applications beyond NXP Semiconductors' standard warranty and NXP Semiconductors' product specifications.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

Translations — A non-English (translated) version of a document, including the legal information in that document, is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

Security — Customer understands that all NXP products may be subject to unidentified vulnerabilities or may support established security standards or specifications with known limitations. Customer is responsible for the design and operation of its applications and products throughout their lifecycles to reduce the effect of these vulnerabilities on customer's applications and products. Customer's responsibility also extends to other open and/or proprietary technologies supported by NXP products for use in customer's applications. NXP accepts no liability for any vulnerability. Customer should regularly check security updates from NXP and follow up appropriately.

Customer shall select products with security features that best meet rules, regulations, and standards of the intended application and make the ultimate design decisions regarding its products and is solely responsible for compliance with all legal, regulatory, and security related requirements concerning its products, regardless of any information or support that may be provided by NXP.

NXP has a Product Security Incident Response Team (PSIRT) (reachable at PSIRT@nxp.com) that manages the investigation, reporting, and solution release to security vulnerabilities of NXP products.

5.3 Trademarks

Notice: All referenced brands, product names, service names, and trademarks are the property of their respective owners.

NXP — wordmark and logo are trademarks of NXP B.V.

Tables

Tab. 1. I2C addresses 5 Tab. 2. Bill of material 7

Figures

Fig. 1. PCA9482UK charging application with single SC converter 3 Fig. 2. PCA9482UK reference schematic with OVP IC 5
Fig. 3. PCA9482UK recommended PCB layout 8

Contents

1	Introduction	3
2	PCA9482UK Charging application	3
2.1	30 W charging application	3
2.2	Guidance for monitoring status and interrupt for IVIN and IBAT regulation	4
2.3	Guidance for IVIN ADC in reverse 1:1 and 1:2 mode	4
3	PCA9482UK reference schematic	5
3.1	Reference schematic with OVP IC	5
3.2	I2C and other digital pins	5
3.3	NTC	6
3.4	AVDD	6
3.5	Input capacitor selection	6
3.6	Flying capacitor selection	6
3.7	Output capacitor selection	7
3.8	Bill of material (BOM)	7
4	Layout Guides	7
4.1	PCB layout guidelines	7
5	Legal information	9

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.
