

AN10841

MIFARE Plus Card Coil Design

Rev. 1.1 — 4 April 2017
172711

Application note
COMPANY PUBLIC

Document information

Info	Content
Keywords	Contactless, MIFARE Plus, ISO/IEC 1443, Resonance, Coil, Inlay
Abstract	This document provides guidance for engineers designing magnetic loop antenna coils for the MIFARE Plus S, X and SE.



Revision history

Rev	Date	Description
1.1	20170404	Updated for 70 pF version
01	20090626	Initial version

Contact information

For more information, please visit: <http://www.nxp.com>

1. Introduction

MIFARE Plus is a passive device (without battery) powered by a magnetic field generated by the PCD. To get the magnetic flux cut by the PICC, it requires a loop antenna.

This document describes some notes to the design of such loop antennas for MIFARE Plus. The detail design is explained in [1]. Although such antennas are relatively straightforward in principle and look very similar when comparing various contactless smartcards, experience proves that their parameters do have a noticeable impact on performance.

In this document, some examples are attached for your reference but please adapt and verify them before you go for production.

1.1 How to use this document

In this document, only the hints and notes specific to MIFARE Plus are explained. All the basics and common design details are explained in the base document [1]. Use the base document and apply wherever required the notes mentioned here.

1.2 Abbreviations and terms

Table 1 lists the abbreviations as used in this document.

Table 1. Table of abbreviations

Abbreviations	
PICC	Proximity Integrated Circuit Card (ISO/IEC14443), tag
PCD	Proximity Coupling Device (ISO14443), reader
f_{RT}	Threshold resonance frequency
Q	Quality factor

2. Card Coil Design notes for MIFARE Plus

There are different classes of antenna widely used in contactless application for MIFARE Plus PICC. For different antenna classes the design of PICC coils are different. Even different application requirements also lead to different antenna design. Basically, three parameters are important for card coil design: coil area, resonance frequency and quality factor.

2.1 Different classes of antenna according to ISO/IEC 14443-1

In the following figure Fig 1, different antenna sizes according ISO/IEC 14443-1 are shown.

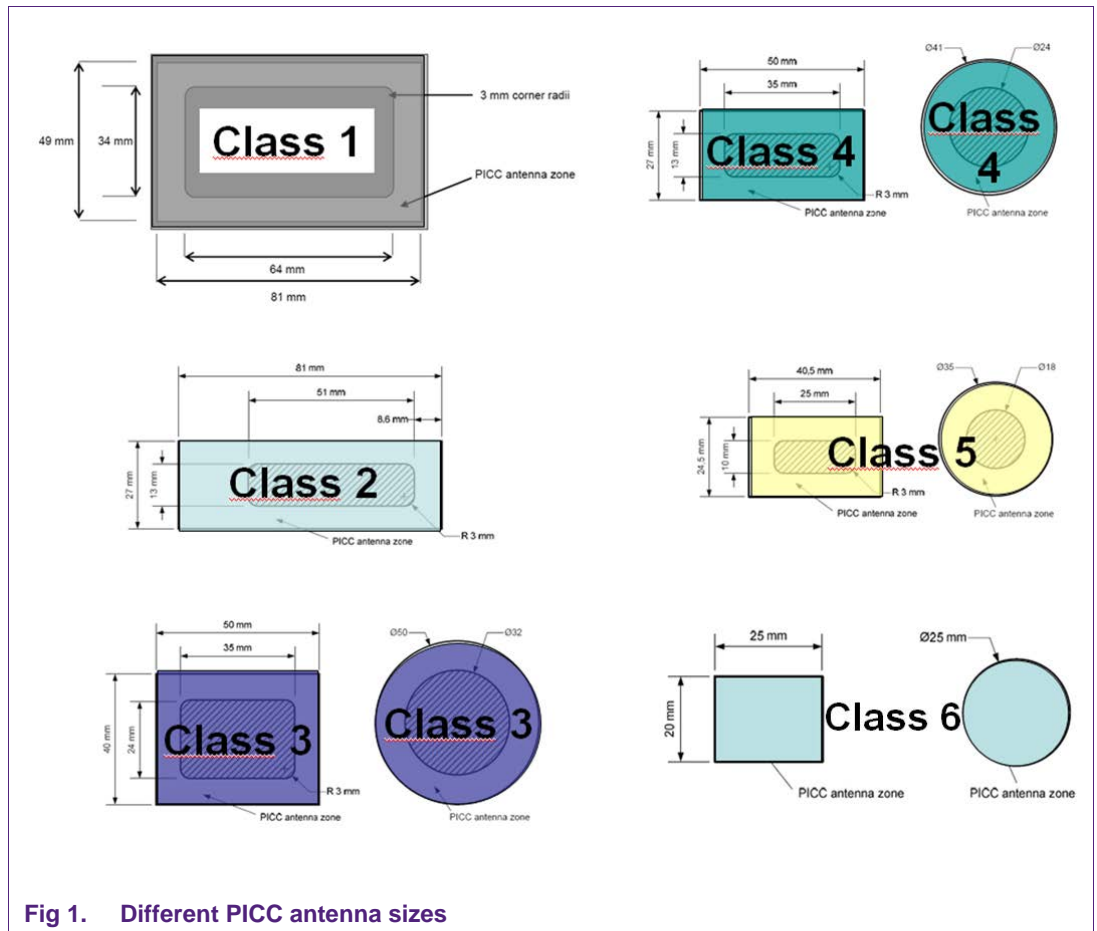


Fig 1. Different PICC antenna sizes

2.2 Average card coil area

Make a card coil area as big as possible. The bending corners are better than sharp corners.

2.3 Unloaded threshold resonance frequency

The appropriate resonance frequency of the antenna coil depends on the card ICs and applications. To cover manufacturing tolerances and optimum performance, for MIFARE Plus, the recommended threshold resonance frequency is given in Table 2.

2.3.1 Measurement of threshold resonance frequency

There are different ways to measure the resonance frequency, and may end up with different results. Follow the way described in the Card Coil Design Guide.

2.4 Unloaded Q of the coil

The quality factor of the antenna coil is very important for longer distance and stable communication. The appropriate Q of an antenna coil depends on the card ICs and applications. To cover manufacturing tolerances and optimum performance, for MIFARE Plus, the recommended Q is given in Table 2.

2.4.1 Measurement of unloaded Q of the coil

There are different ways to measure the Q, and may end up with different results. Follow the way described in the Card Coil Design Guide [1].

2.5 NXP recommendation for PICC coil design

Table 2 summarizes recommendations on MIFARE Plus chip capacitance, inlay threshold resonance frequency as well as on quality factor of the coil for different classes (sizes).

Table 2. PICC coil design recommendation

Antenna class	Recommended chip of MIFARE Plus	Recommended threshold resonance frequency (f_{RT})	Recommended unloaded Q	Comments
Class 1	17pF	13.56 MHz < f_{RT} < 16.00 MHz	>30	For the single card application, a lower frequency is better and for multi-card (or stacked cards) applications, a higher frequency is better.
Class 2	70pF	12.70 MHz < f_{RT} < 14.50 MHz	>40	For 106 kbps and single card application. The optimum resonance frequency is 13.56 MHz.
Class 3	70pF	12.70 MHz < f_{RT} < 14.50 MHz	>40	For 106 kbps and single card application. The optimum resonance frequency is 13.56 MHz.
Class 4	70pF	12.70 MHz < f_{RT} < 14.50 MHz	>40	For 106 kbps and single card application. The optimum resonance frequency is 13.56 MHz.
Class 5	70pF	12.70 MHz < f_{RT} < 14.50 MHz	>40	For 106 kbps and single card application. The optimum resonance frequency is 13.56 MHz.
Class 6	70pF	13.00 MHz < f_{RT} < 14.00 MHz	>40	For 106 kbps and single card application. The optimum resonance frequency is 13.56 MHz.

NOTE: Increasing the communication bit rates may reduce the communication distance specially for the small classes of antenna (other than class 1).

2.6 Practical design hints and recommendations

2.6.1 ID1-sized antennas

Within the confines of the application and the card manufacturing processes used, try to maximize the antenna size. The outermost turn of the antenna coil should be placed as close as possible to the edge of the card (represented by an 81 x 49 mm rectangle, Fig 2).

Note: international standards and industry specifications may restrict the choice.

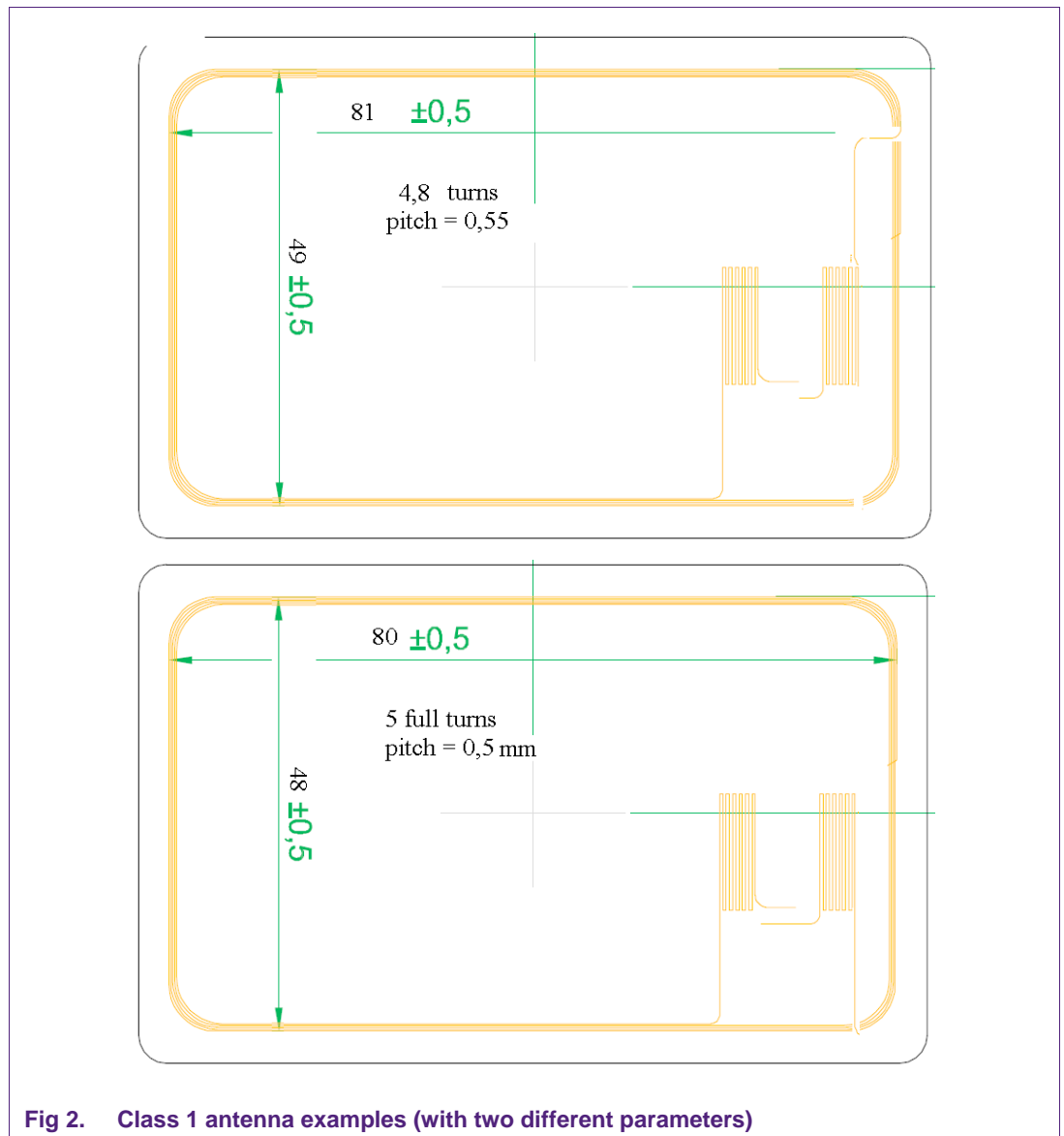


Fig 2. Class 1 antenna examples (with two different parameters)

For 17pF chip the ID1 size (class 1) antenna is recommended. For other classes use the 70pF version of MIFARE Plus chip.

Fig 3 shows further examples of typical parameters for different ID1-sized antenna designs. Besides geometrical coil parameters (orange colored area), also measured (blue colored area) and calculated (green colored area) electrical parameters are listed in comparison.

Embedded Wire rectangular Antennas								
Dimensions	outline	mm	72.6 x 42	80.2 x 48	80 x 47.5	80 x 48	80.5 x 48	
	wire diam.	mm	0.112	0.112	0.112	0.112	0.112 ?	
	wire pitch	mm	0.14	0.45	0.45	0.45	0.3	
	turns		5	5	4.9	5	5	
measured	Ls @ 1MHz	µH	4.83	4.89	4.69	4.90	5.23	
	Rs Q 1 MHz	Ohm	2.05	2.29	2.22	2.24	2.37	
	fres	MHz	36.84	38.45	42.58	39.46	39.19	
	Rp @ fres	kOhm	55.00	69.00	90.00	90.00	55.00	
Calculated	Q @ fres		63.00	66.00	72.00	70.00		
	Cp	pF	3.87	3.51	2.98	3.32	3.16	
	Rs	Ohm	3.92	3.78	3.22	3.38	4.49	
	Q		105.03	110.11	124.00	123.70	99.16	


Fig 3. Typical parameters of different class 1 card antennas

2.7 Practical design hints and recommendations for 70pF IC

For class 2 and up to class 6 antennas, it is recommended to use 70pF chip version.

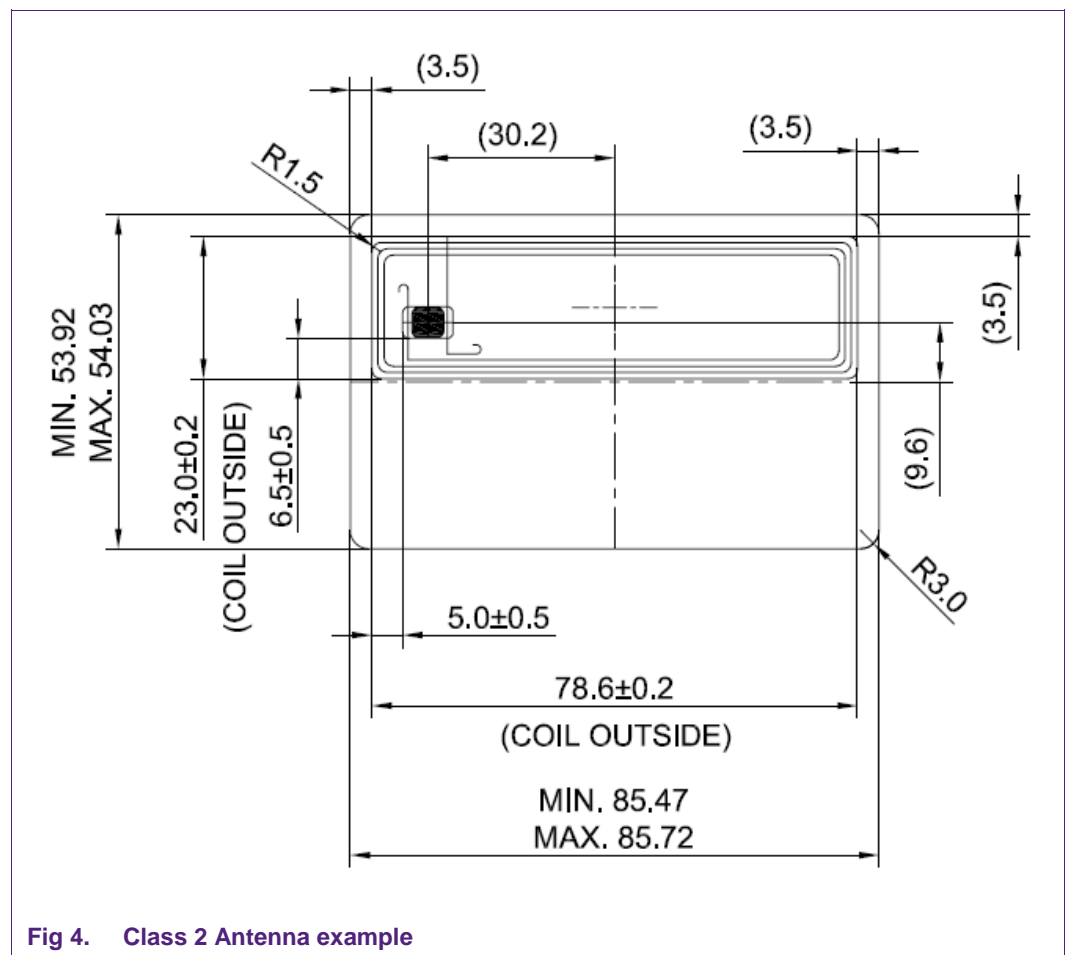2.7.1 ID ½ sized (class 2) antenna

Geometrical parameters of one possible class 2 size antenna design, as well as its location within the ID1 card area is shown in Fig 4.



3. Reference

- [1] AN011732 "MIFARE Card Coil Design Guide"

4. Legal information

4.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

4.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Translations — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

4.3 Licenses

ICs with DPA Countermeasures functionality



NXP ICs containing functionality implementing countermeasures to Differential Power Analysis and Simple Power Analysis are produced and sold under applicable license from Cryptography Research, Inc.

4.4 Trademarks

Notice: All referenced brands, product names, service names and trademarks are property of their respective owners.

MIFARE — is a trademark of NXP B.V.

MIFARE Plus — is a trademark of NXP B.V.

5. List of figures

Fig 1. Different PICC antenna sizes.....4
Fig 2. Class 1 antenna examples (with two different parameters).....6
Fig 3. Typical parameters of different class 1 card antennas7
Fig 4. Class 2 Antenna example8

6. List of tables

Table 1. Table of abbreviations.....3
Table 2. PICC coil design recommendation.....5

7. Contents

1.	Introduction	3
1.1	How to use this document.....	3
1.2	Abbreviations and terms	3
2.	Card Coil Design notes for MIFARE Plus	4
2.1	Different classes of antenna according to ISO/IEC 14443-1	4
2.2	Average card coil area	4
2.3	Unloaded threshold resonance frequency.....	5
2.3.1	Measurement of threshold resonance frequency.....	5
2.4	Unloaded Q of the coil.....	5
2.4.1	Measurement of unloaded Q of the coil	5
2.5	NXP recommendation for PICC coil design.....	5
2.6	Practical design hints and recommendations	6
2.6.1	ID1-sized antennas	6
2.7	Practical design hints and recommendations for 70pF IC	8
2.7.1	ID ½ sized (class 2) antenna.....	8
3.	Reference.....	8
4.	Legal information	9
4.1	Definitions	9
4.2	Disclaimers.....	9
4.3	Licenses.....	9
4.4	Trademarks.....	9
5.	List of figures.....	10
6.	List of tables	11
7.	Contents.....	12

Please be aware that important notices concerning this document and the product(s) described herein, have been included in the section 'Legal information'.
