

AN12325

Using the DCDC feature

Rev. 0 — February 2019

Application Note

by: NXP Semiconductors

1 Introduction

This application note provides a hardware design guide for the DCDC converter on the LPC55xx devices and explains how to properly choose external components for the DCDC converter. The main part of the document focuses on the critical parameters of external components and their implication of incorrect selection, including a PCB design example of the external component.

2 Theory and uses of DCDC converters

DCDC converters are used in portable electronic devices, such as cellular phones and laptop computers, which are supplied primarily from batteries. Such electronic devices often contain several sub-circuits, each with its own voltage level requirement different from the level supplied by the battery or an external supply (sometimes higher or lower than the supply voltage). Additionally, the battery voltage lowers because its stored energy is drained. Switched DCDC converters offer a method to increase the voltage from a partially lowered battery voltage and save space (instead of using multiple batteries to achieve the same goal).

Most DCDC converter circuits also regulate the output voltage. Exceptions include high-efficiency LED power sources (which are DCDC converters that regulate the current flowing through the LEDs) and simple charge pumps (which double or triple the output voltage).

Switching converters (such as buck converters in LPC5500) provide much higher power efficiency than DCDC converters and linear regulators (simpler circuits that lower the voltage by dissipating the excess power as heat), but do not step up the output current.

3 Hardware design guide

This chapter summarizes the hardware requirements for external components used for a proper functionality of the DCDC internal converter. It contains the recommendation of appropriate component selection and the PCB drawing.

The LPC55xx family consists of six internal regulators (including the DCDC converter) which are supplied by the main external supply domain (VBAT 1.8 V – 3.6 V). The connection of all the external components and the MCU needed for a proper DCDC functionality is shown in [Figure 1](#), on page 2.

Contents

1 Introduction.....	1
2 Theory and uses of DCDC converters.....	1
3 Hardware design guide.....	1
4 Conclusion.....	4



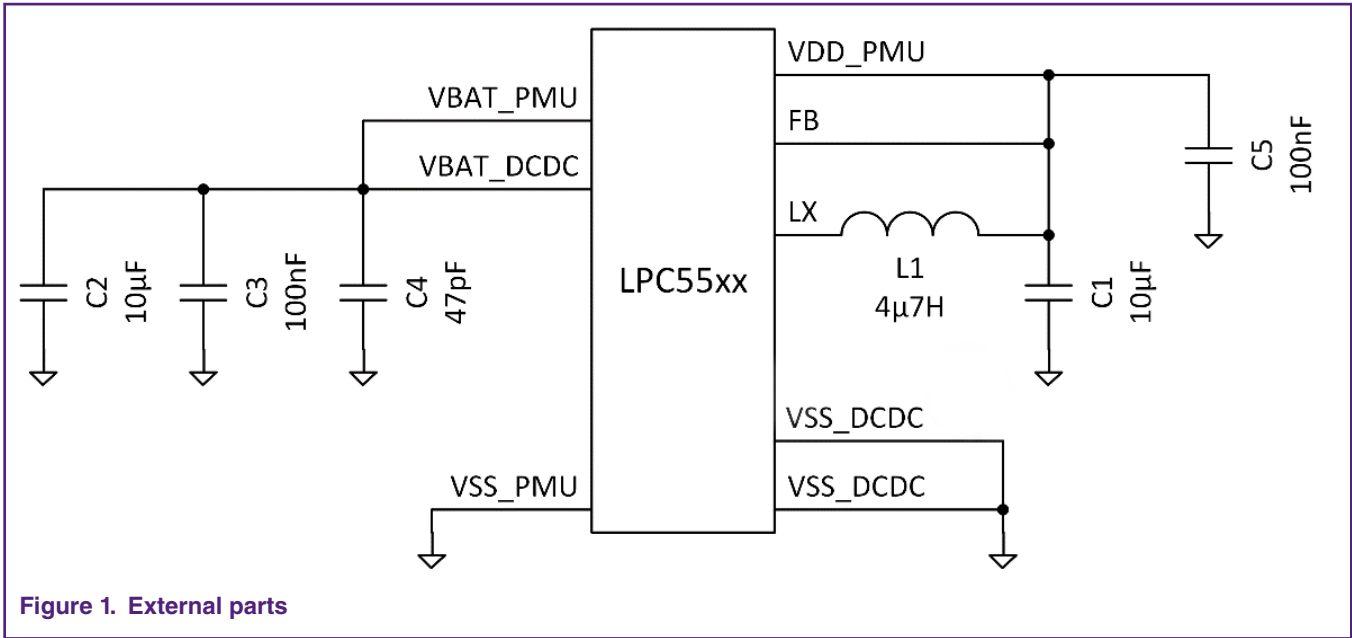


Figure 1. External parts

Table 1. List of pin names and numbers for internal DC-DC converter on page 2 summarizes pin names and numbers for all packages.

Table 1. List of pin names and numbers for internal DC-DC converter

Pin Name	Pin number	
	HLQFP100	VBGA100
VBAT_DCDC	49	45
VBAT_DCDC_CORE	50	45
VBAT_PMU	51	46
VSS_DCDC	47	43
VSS_DCDC_CORE	46	42
VSS_PMU	-	47
LX	48	44
FB_VDD_PMU	45	41

Table 2. External parts on page 2 summarizes typical values and limitations for the external components of the DCDC internal converter.

Table 2. External parts

Part	Min	Typ	Max	Unit
C1	10	22 (X5R or X7R)	47	µF
C2	10	22 (X5R or X7R)	47	µF
C3	80	100 (X5R or X7R)	120	nF
C4	38.7	47 (COG)	56.2	pF

Table continues on the next page...

Table 2. External parts (continued)

C5	80	100 (X5R or X7R)	120	nF
L1	3.87	4.7	10	μ H

3.1 Input decoupling capacitors

The 100-nF and 47-pF ceramic capacitors are the input decoupling capacitors for the DCDC converter. The 10- m F (or 20- m F) input ceramic capacitor is used to decouple and power the internal DCDC converter. All the decoupling capacitors must be placed close to the pin. For the capacitors, there is no ESR value restriction.

3.2 Output filter capacitor

This capacitor sets the voltage ripple value. A minimum value of the output capacitor is 10 μ F and it is necessary for the correct functionality of the DCDC converter. This capacitor also sets the voltage ripple value, which is very important for the USB power supply requirements.

If the value of the output capacitor is below the 10 μ F, the voltage ripple is higher and it does not meet the requirements of the internal LDO. Values higher than 22 μ F increase the possible noise current.

3.3 Power inductor

The typical inductor value for the most application ranges from 3.7 μ H to 5.6 μ H. These values are chosen according to the desired ripple current.

At the expense of a higher output-voltage ripple, small-value inductors result in a higher output current slew rate, improving the load transient response of the converter. Larger values of inductors lower the ripple current and reduce the core magnetic hysteresis losses.

[Table 3. Power inductor](#) on page 3 summarizes the typical values and limitations of the power inductor.

Table 3. Power inductor

Parameter	Min	Typ	Max	Unit
Inductance value	3.7	4.7	5.6	μ H
Saturation current	350	500	-	mA

3.3.1 Saturation current limitation

The minimum value of the saturation current is 350 mA. The recommended saturation current is 500 mA (or higher).

3.4 PCB guide line

To reduce the series resistance from the DCDC inductor, keep the traces as thick and as short as possible. The ground between the inputs of capacitors C2, C3, C4, the DCDC ground pads, and the output capacitor C1 must be on the same plane. It is not possible to use a via or a strap connection. Figure 2 shows a proper DCDC ground connection.

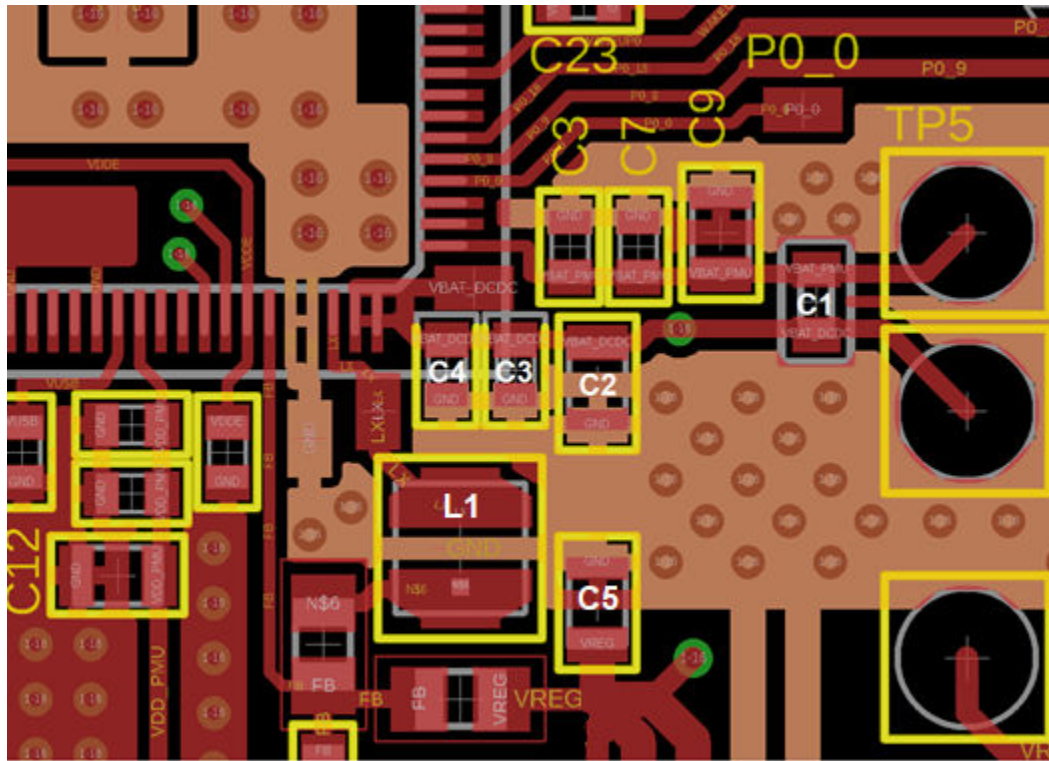


Figure 2. Ground connection

4 Conclusion

This application note summarizes all external components and PCB recommendations of the internal DCDC converter used in LPC55xx. For a proper functionality, follow all of these recommendations in your designs with LPC55xx. Efficiency is often the main purpose to use a DCDC converter. The use of DCDC converters increases the efficiency of the conversion from battery voltage to a low supply voltage. A linear regulator can be used but it cannot achieve the same efficiency as switching regulators.

How To Reach Us

Home Page:

nxp.com

Web Support:

nxp.com/support

Information in this document is provided solely to enable system and software implementers to use NXP products. There are no express or implied copyright licenses granted hereunder to design or fabricate any integrated circuits based on the information in this document. NXP reserves the right to make changes without further notice to any products herein.

NXP makes no warranty, representation, or guarantee regarding the suitability of its products for any particular purpose, nor does NXP assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters that may be provided in NXP data sheets and/or specifications can and do vary in different applications, and actual performance may vary over time. All operating parameters, including "typicals," must be validated for each customer application by customer's technical experts. NXP does not convey any license under its patent rights nor the rights of others. NXP sells products pursuant to standard terms and conditions of sale, which can be found at the following address: nxp.com/SalesTermsandConditions.

While NXP has implemented advanced security features, all products may be subject to unidentified vulnerabilities. Customers are responsible for the design and operation of their applications and products to reduce the effect of these vulnerabilities on customer's applications and products, and NXP accepts no liability for any vulnerability that is discovered. Customers should implement appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP, the NXP logo, NXP SECURE CONNECTIONS FOR A SMARTER WORLD, COOLFLUX, EMBRACE, GREENCHIP, HITAG, I2C BUS, ICODE, JCOP, LIFE VIBES, MIFARE, MIFARE CLASSIC, MIFARE DESFire, MIFARE PLUS, MIFARE FLEX, MANTIS, MIFARE ULTRALIGHT, MIFARE4MOBILE, MIGLO, NTAG, ROADLINK, SMARTLX, SMARTMX, STARPLUG, TOPFET, TRENCHMOS, UCODE, Freescale, the Freescale logo, Altivec, C-5, CodeTEST, CodeWarrior, ColdFire, ColdFire+, C-Ware, the Energy Efficient Solutions logo, Kinetis, Layerscape, MagniV, mobileGT, PEG, PowerQUICC, Processor Expert, QorIQ, QorIQ Qonverge, Ready Play, SafeAssure, the SafeAssure logo, StarCore, Symphony, VortiQa, Vybrid, Airfast, BeeKit, BeeStack, CoreNet, Flexis, MXC, Platform in a Package, QUICC Engine, SMARTMOS, Tower, TurboLink, and UMEMS are trademarks of NXP B.V. All other product or service names are the property of their respective owners. AMBA, Arm, Arm7, Arm7TDMI, Arm9, Arm11, Artisan, big.LITTLE, Cordio, CoreLink, CoreSight, Cortex, DesignStart, DynamIQ, Jazelle, Keil, Mali, Mbed, Mbed Enabled, NEON, POP, RealView, SecurCore, Socrates, Thumb, TrustZone, ULINK, ULINK2, ULINK-ME, ULINK-PLUS, ULINKpro, μ Vision, Versatile are trademarks or registered trademarks of Arm Limited (or its subsidiaries) in the US and/or elsewhere. The related technology may be protected by any or all of patents, copyrights, designs and trade secrets. All rights reserved. Oracle and Java are registered trademarks of Oracle and/or its affiliates. The Power Architecture and Power.org word marks and the Power and Power.org logos and related marks are trademarks and service marks licensed by Power.org.

© NXP B.V. 2019.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: February 2019

Document identifier: AN12325

