

THERMAL DISTORTION IN VIDEO AMPLIFIERS

Prepared by: **Curtis Gong**
Motorola RF Products Division
Torrance, CA

ABSTRACT

Thermal distortion is a problem in many high resolution video amplifiers. Thermal distortion occurs when there are instantaneous power changes in the transistor stages. If the problem goes uncompensated, it leads to a visual effect known as smearing. This Application Note will discuss what smearing is, what causes thermal distortion, how to measure it and how to compensate the problem.

WHAT IS SMEARING?

Smearing is best explained by using an example. Smearing, or ghosting, is most noticeable when a black block is displayed on an all white background. Referring to Figure 1, both Sections a. and b. should be the same brightness. When there is a smearing problem, Section b. will be brighter than Section a. This problem is related to the droop of the video signal, and can be explained using Figure 2. Notice after the transition from black to white (from high voltage to low voltage), the video signal is below the specified white level. This signal shows up on the display as a section "brighter" than white. The signal does eventually settle to the white level; but until it does, the display will appear brighter than it should be.

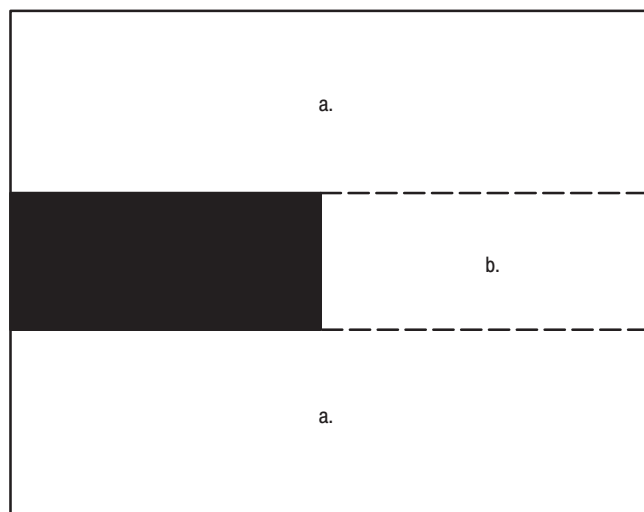


Figure 1.

WHAT CAUSES THERMAL DISTORTION?

The transistors of a video amplifier are often subject to large instantaneous power changes because of the large voltage swings, particularly on transitions from black to white. These power changes cause changes in the transistor's junction temperature. Due to the transistor's thermal time constant, which is the amount of time it takes something to heat up or cool down, the transistor can't change temperature fast enough. It is this thermal time constant and the fact that V_{BE} of a transistor changes with temperature, $-2 \text{ mV}/^\circ\text{C}$, that causes thermal distortion.

Figure 3 shows a simple example that can be used to explain the thermal distortion concept. In the ideal case, where V_{BE} does not change with temperature, there is a power swing of 107 mW across the transistor. Using the 107 mW and a thermal resistance of $30^\circ\text{C}/\text{W}$, we can see how this power swing affects the output in the real case. (A change in power of 107 mW would create about the normal junction temperature T_E a change of $\pm 1.6^\circ\text{C}$.) Notice on the plot of T_J , that the junction temperature does not change instantaneously. This is a result of the thermal time constant. Using $-2 \text{ mV}/^\circ\text{C}$, we can calculate V_{BE} ; from there we can calculate V_E , I_E , and V_O . This example clearly shows the distortion of the square wave.

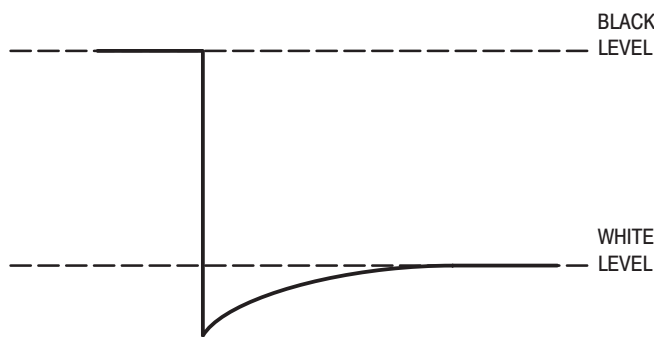


Figure 2.

Freescale Semiconductor, Inc.
ARCHIVE INFORMATION

ARCHIVE INFORMATION

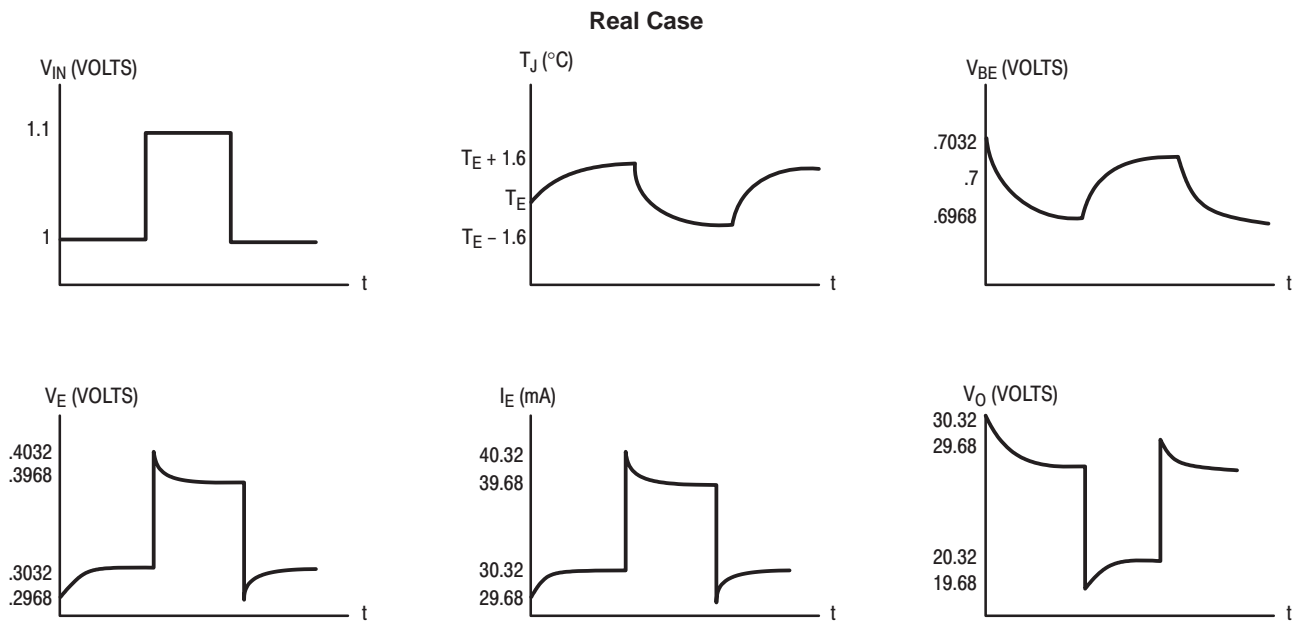
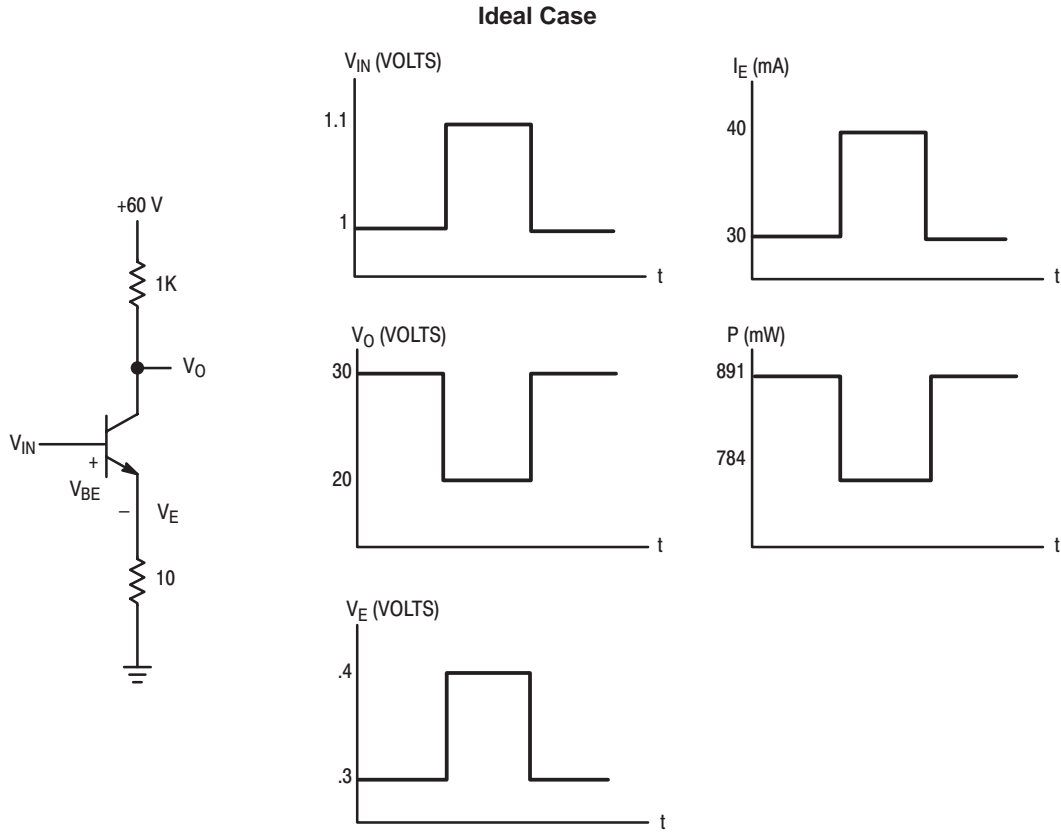


Figure 3.

MEASURING THE DISTORTION

Making an accurate measurement of the distortion can be difficult. The oscilloscope must have enough vertical offset to enable the edge to be viewed with a reasonable scale. Often, flatness measurements in the 100 mV to 200 mV range must be measured on a 1 Volt/div scale. In this case, the accuracy is not good. Another issue that must be considered is scope performance at maximum offsets. When a scope is operating at a maximum offset, it may introduce some of its own distortion. Check with the manufacturer.

HOW TO COMPENSATE THE PROBLEM

There is no real standard on how small the distortion must be. Several years ago a 1% flatness was acceptable (400 mV for a 40 V swing). On today's high resolution displays, this is clearly unacceptable. A flatness of 200 mV for a 40 V swing will cause noticeable smearing problems. Some designers believe a 50 mV flatness is required, but anything less than 100 mV is generally acceptable. Flatness of 50 mV – 100 mV for a 40 V swing is very difficult to measure.

The effect of thermal distortion can be compensated. The Motorola CR2424 is used as an example to show some of the compensation techniques that can be utilized. The output waveform, when there is a distortion problem, appears as a signal with excessive mid and high frequency gain. The signal would be flat if this excessive gain were eliminated. One way of doing this is to use a series RC network as feedback from the output to the input. The CR2424 has an internal compensation network which noticeably improves the flatness. Unfortunately, this is only a first order compensation network and doesn't eliminate all problems. The flatness can be further improved by adding an external compensation network consisting of a 150 pF capacitor and a 200 kΩ resistor. Figure 4 shows the flatness of the CR2424 without the internal compensation network while Figure 5

shows the flatness with the internal network. Note the considerable improvement in the flatness of the output waveform when the complete CR2424, including its internal compensation network, is used.

Figure 6 shows the effect of an external compensation network. The improvement may seem small, but it can be seen on the CRT. Additional external compensation networks may be added to further improve the flatness. In oscilloscopes, where flatness is very important, as many as ten networks are used.

There is another flatness issue. The first 0.5 μs of the pulse is not flat. This can be seen in Figures 5 and 6. On the display, this problem shows up as a gray area right after the transition from black to white. This is a frequency response issue and can be corrected by adding an additional input peaking network. Figure 7 shows the circuit and a photo of the actual waveform.

When using the external compensation network techniques as previously described, there are several precautions that must be taken. The first precaution is that thermal distortion is dependent on signal swing. The distortion improves with smaller signal swings because the power changes are less. The 200 kΩ and 150 pF RC compensation network was optimized for a 40 V signal swing. For smaller signal swings, the compensation network tends to overcompensate causing the flatness to slope in the opposite direction, i.e., the smearing would appear darker than white instead of brighter than white. In this case, the CRT designer may want to adjust the compensation network (by changing the capacitor) to optimize the flatness at a different contrast level (voltage swing) on the display.

Another area of precaution is the 215 Ω input peaking resistor. Since the CR2424 is a feedback amplifier, the gain is determined by the input peaking resistor and the feedback network. The previously mentioned compensation networks were optimized for a 215 Ω input resistor. If the resistor was changed, the CR2424 would have a different gain and the compensation networks would no longer be optimized.

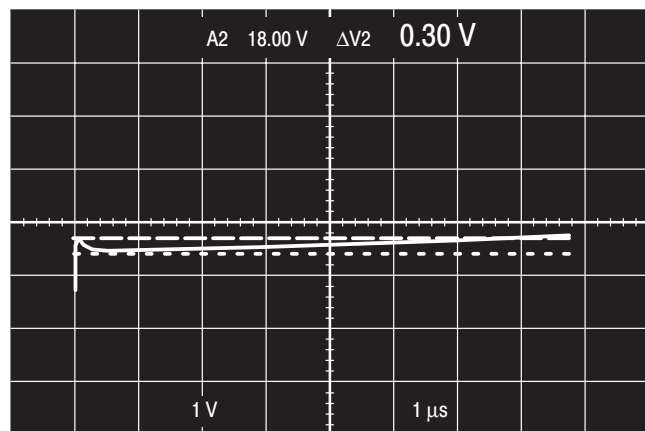


Figure 4. CR2424 Without Compensation

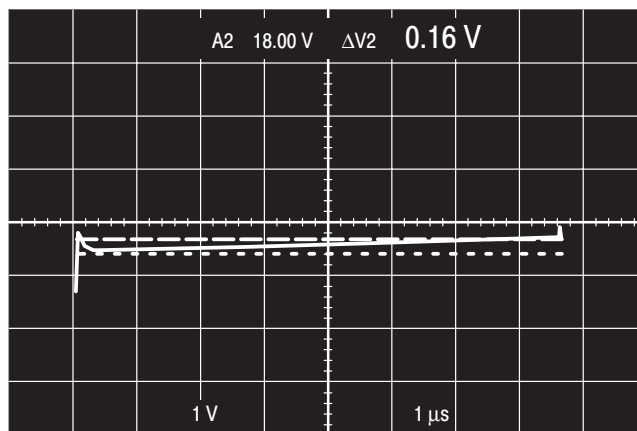


Figure 5. CR2424 With Internal Compensation

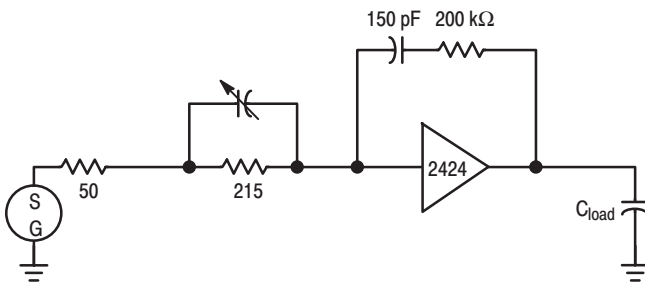
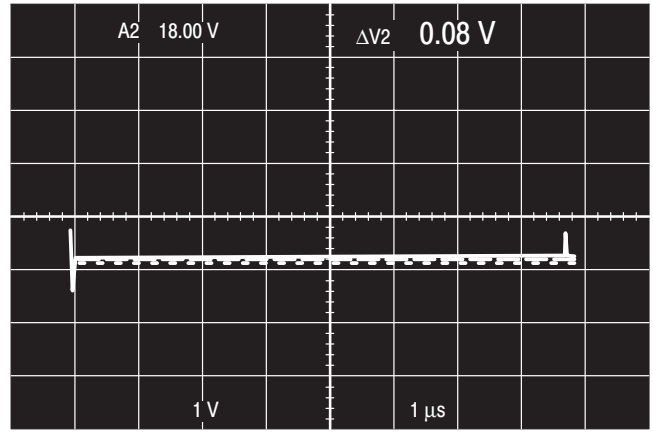
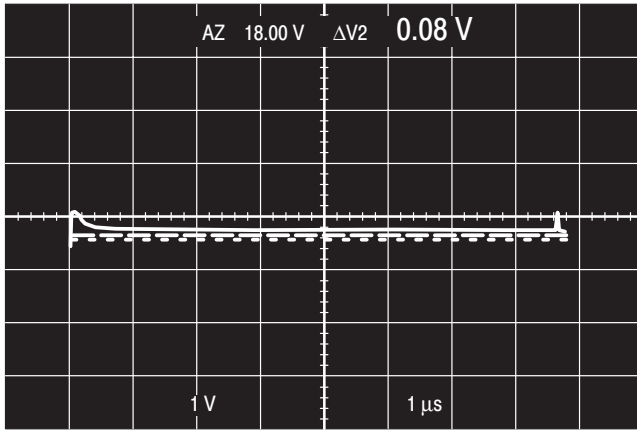


Figure 6. CR2424 With External Compensation

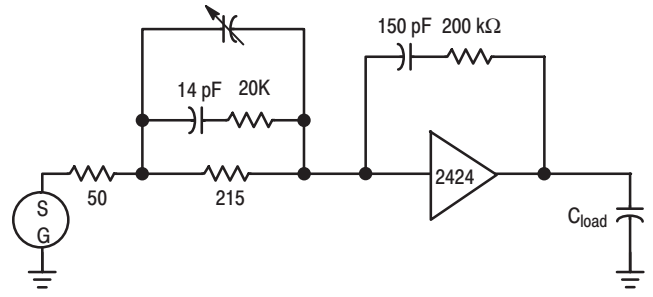



Figure 7. CR2424 With Modified Input Network

Freescale Semiconductor, Inc.
 ARCHIVE INFORMATION

ARCHIVE INFORMATION



Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters can and do vary in different applications. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Motorola does not convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

Literature Distribution Centers:

USA: Motorola Literature Distribution; P.O. Box 20912; Phoenix, Arizona 85036.

EUROPE: Motorola Ltd.; European Literature Centre; 88 Tanners Drive, Blakelands, Milton Keynes, MK14 5BP, England.

JAPAN: Nippon Motorola Ltd.; 4-32-1, Nishi-Gotanda, Shinagawa-ku, Tokyo 141, Japan.

ASIA PACIFIC: Motorola Semiconductors H.K. Ltd.; Silicon Harbour Center, No. 2 Dai King Street, Tai Po Industrial Estate, Tai Po, N.T., Hong Kong.



MOTOROLA

**For More Information On This Product,
Go to: www.freescale.com**