

Designing with I²C-Bus Devices

Emmanuel T. Nana

Technical Marketing Manager Secure Interfaces & Power

June 2019 | Session #AMF-IND-T3704









SECURE CONNECTIONS FOR A SMARTER WORLD

NXP Secure Interfaces & Power Solutions

Signal Integrity & Routing Solutions

- Signal Switches & Re-drivers
- USB 3.1, USB Type-C
- Thunderbolt
- PCIe, SATA, SAS
- DP. HDMI. VGA
- Audio, Data
- Memory Interface

Industry leader in high-speed switching. Lowest-power consumption re-drivers

Security & Authentication

· Anti-Counterfeit Solution

Industry's smallest package with lowest power.

Load Switches

- Over Voltage Protection
- Over Current Protection
- · Reverse Current Protection
- Under voltage Lockout
- Thermal Shutdown
- Low R_{ON}
- Low Quiescent Current

HV Load switching with 100V surge protection.

Power Solutions

- USB Power Delivery
- AC-DC Controllers
- DC-DC Boost Converters
- Direct Charging (Rapid Battery Charging)
- Wireless Charging (Qi/A4WP)
- Micro-PMIC
- Powerline Communication Modem

High efficiency power conversion.

Support of multi-charging protocols (Direct, USB-PD, QC, BC1.2, and proprietary).

Interface Solutions

- DisplayPort Bridges
- UARTS
- Comparators
- I²C Bus Buffers
- I²C Bus Controllers
- I²C Muxes & Switches
- Voltage Level Translators

Industry's largest I²C Portfolio for Mobile, Computing and Industrial.

Bus Peripherals

- Real Time Clocks
- GPIO Expanders
- Temperature Sensors
- LCD Drivers
- LED Controllers
- Capacitive Sensors
- Stepper Motor Controllers
- EEPROM
- Watch IC
- Data ConverterDIP Switches
- Ultra low-power RTC's.

Widest portfolio of GPIO Expanders.

Wireless Connectivity & Smart Sensor Solutions

- NTAG Smart Sensors
- NFMI Radio
- Audio over BLE
- RF & IF Discretes
- Transceivers
- LNA's
- Mixers
- Switches

Integrated temperature logging solutions.

Ultra low-power single-chip solution, providing robust wireless audio streaming.

Smart Audio Solutions

- Class AB Amplifiers
- Class D Amplifiers
- Smart Amplifiers (/w integrated DSP)
- Software
- Speaker Protection
- Audio DAC & ADC

Best-in class speaker protection hardware and software Class D Amplifier solutions.



Agenda

- Introduction to I²C
- I²C-Bus Communication Protocol
- I²C-Bus Pull-up Resistor Calculation
- I²C Interface Signals
- I²C-Bus Tools










What is I^2C ?

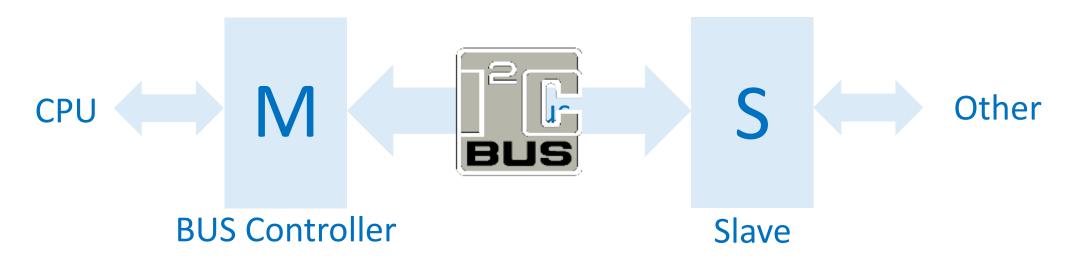
- A communication bus for slow speed digital data
- I²C = *Inter Integrated Circuit* (Philips invented in the 1980s)
- Original purpose to link a CPU to other circuits in television sets
- Links one or more SLAVE devices
- To a MASTER (one or more BUS CONTROLLERS)





What is I²C?

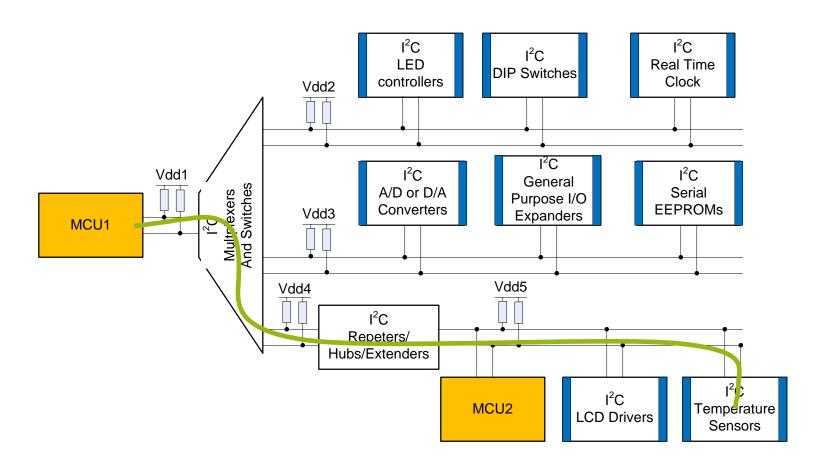- I²C BUS can have:
 - Multiple masters
 - Multiple slaves
- Only one master talks to one slave at a time
- All the slaves on the same bus must have different address
- Slow speed device cannot understand higher speed transfer






I²C-Bus Physical Layer

Physical Layer = Electrical Connections

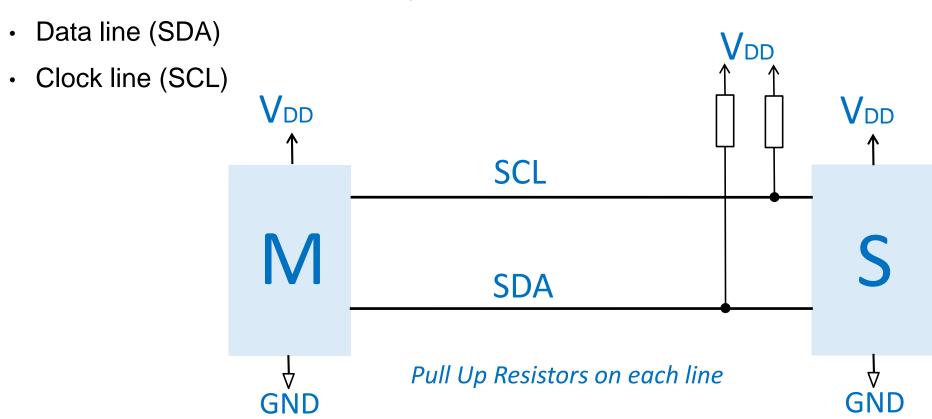Two Wires: Data and Clock (plus ground and supply)










What is the I²C Protocol Layer?

Protocol Layer = Data Format, Traffic, Collision Arbitration

An I²C Bus must have:

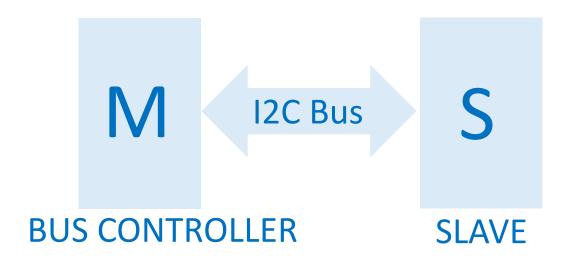Two node types (Master and Slave)
Minimum of ONE Slave and ONE Bus Master





I²C Interface Protocol

I²C BUS constructs off 9 bit block

START condition: When SCL is HIGH then SDA goes from HIGH to LOW

Address bit 7 bit after START condition

Read or Write bit
After 7 bit address, the 8th bit is Read or Write bit
1 = Read cycle or 0 = Write cycle

ACK


Synchronization bit between master and slave 0 = ACK and 1 = NACK

Data Byte

8-bit after address byte is data byte from master or slave

STOP condition:

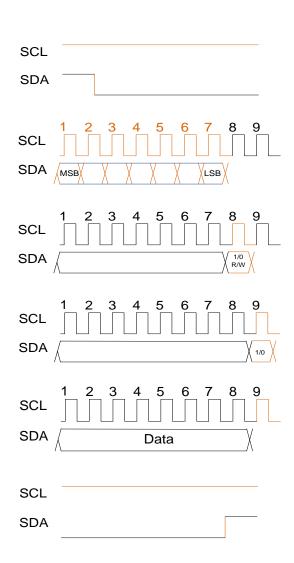When clock line (SCL) is HIGH then the data line (SDA) goes LOW to HIGH





All slaves on this bus pay attention !!!



Master wants to talk slave with this address



Master wants to read or write

0: Write cycle1: Read cycle



Slave or master:

0: I am here or data received

1: not me or data not received



Data byte


Master sends data when write cycle Slave sends data when read cycle



Master notifies the slave this is the end of transaction



Complete I²C Interface Protocol

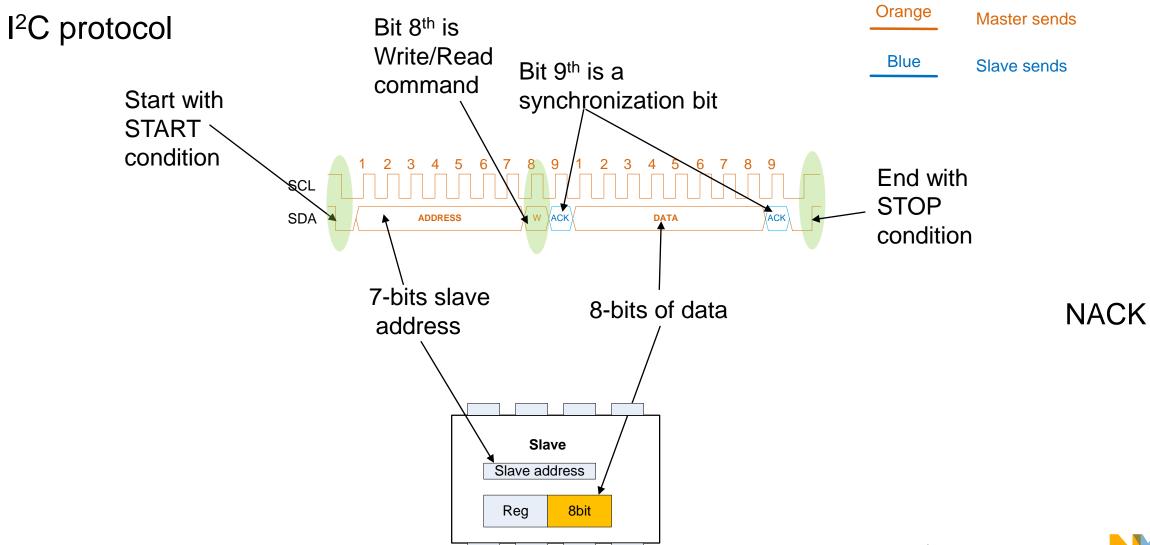








I/O (SDA & SCL) Driver Architecture

SDA and SCL are open drain/collector

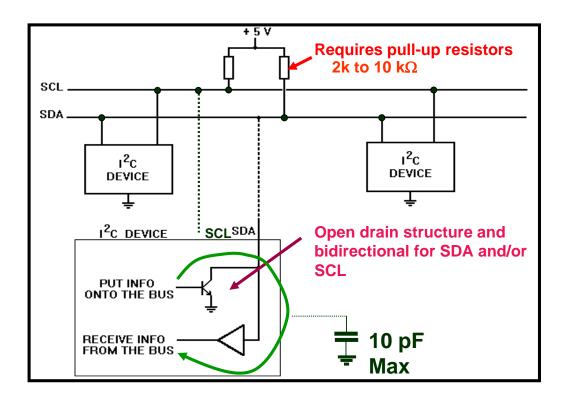
Required pull-up resistors to pull the line to logic "1"





Key Electrical Parameters

	Standard Mode	Fast Mode	Fast Mode Plus	High Speed Mode	
Bit Rate (kb/s)	0 to 100	0 to 400	0 to 1000	0 to 1700	0 to 3400
Max Load (pF)	400	400	560	400	100
Rise time (ns)	1000	300	120	160	80
Noise filter (ns)	-	50	10	10	10

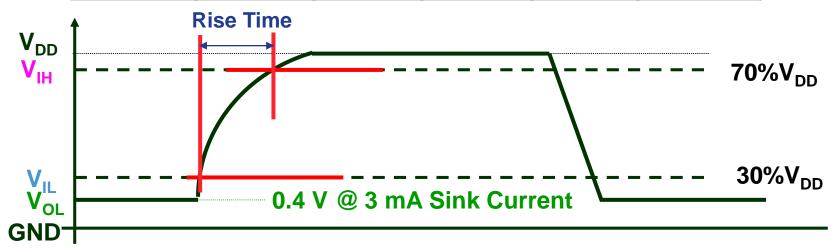



Calculating Pull-up Resistors

$$1) R_{MIN} < R_{PU} < R_{MAX}$$


2)
$$R_{MIN} = (V_{DDMAX} - V_{OLMAX}) / I_{OLMAX}$$

	V _{OLMAX}	R _{MIN}			
V _{DDMAX}		I _{OLMAX} = 3mA	I _{OLMAX} = 6mA*	I _{OLMAX} = 12mA**	I _{OLMAX} = 30mA***
2.7 V	0.6 V	700 Ω	350 Ω	175 Ω	70 Ω
3.6 V	0.6 V	1.0 kΩ	500 Ω	250 Ω	100 Ω

- * I2C Bus with a buffer
- ** EXPxxxx bus
- *** I2C Fast-mode Plus Bus

3)
$$R_{MAX} * C_{MAX} = 1.18 * t_r$$

MODE	Frequency	t _r	C _{MAX}	R _{MAX}
Standard	100 kHz	1000 ns	400 pF	2.96 kΩ
Fast Mode	400 kHz	300 ns	400 pF	885 Ω
Fast Mode Plus	1000 kHz	120 ns	560 pF	252 Ω

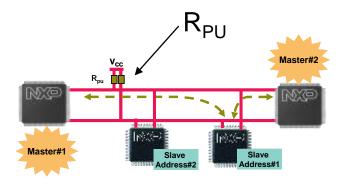

Glossary

R_{PU}: Pull-up resistor

R_{MIN}: Minimum pull-up resistor

R_{MAX}: Maximum pull-up resistor

V_{DDMAX}: Maximum supply rail

V_{OLMAX}: Maximum output voltage low

I_{OLMAX}: Maximum sink current

C_{MAX}: Maximum load capacitance

t_r: Rise time



How to Calculate the I²C-Bus Pull-up Resistors?

Minimum value

There is a minimum resistor value determined by the I²C spec limit of 3 mA

```
R = (Vdd_{max} - Vol_{max})/0.003A
```

Example: using a 5±0.5 V bus: $R = (5.5V - 0.4V)/0.003A = 1.7 k\Omega$

Maximum value

Determined by the I²C-bus rise time requirements:

$$V(t1) = 0.3*Vdd = Vdd (1-1/e^{t1/RC})$$
; then $t1 = 0.3566749*RC$

$$V(t2) = 0.7*Vdd = Vdd (1-1/e^{t2/RC})$$
; then $t2 = 1.2039729*RC$

$$t = t2-t1 = 0.8472979*RC$$

For standard-mode I²C-bus: $t = rise time = 1000ns (1 \mu s)$

so
$$RC = 1180.2 \text{ ns}$$

Example: at a bus load of 400 pF: $R_{max} = 2.95 \text{ k}\Omega$

For fast-mode:


I²C-bus rise time = 300 ns @ 400 pF: R_{max} = 885 Ω



How Does User Derive the Rise Time for I²C-Bus?

I²C-bus rise time is determined as in the following:

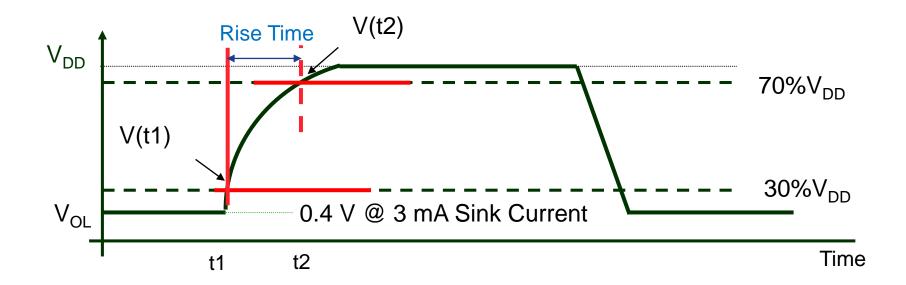- 1) $V(t1) = 0.3*V_{DD} = V_{DD} (1-1/et1/RC) \rightarrow t1 = 0.3566749*RC (EQ1)$
- 2) $V(t2) = 0.7*V_{DD} = V_{DD} (1-1/et2/RC) \rightarrow t2 = 1.2039729*RC (EQ2)$
- 3) Subtract EQ1 from EQ2 \rightarrow t _{rise time} = t2-t1 = 0.8472979*RC or R*C = 1.18*t _{rise time}





Effect of Pull-up Resistors

- Minimum pull-up resistor limits the maximum current sink that affects the voltage output low (VOL).
 - Increasing pull-up resistor above RMIN leads to decreasing VOL and higher noise margin
 - Decreasing pull-up resistor below RMIN leads to increasing VOL and lower noise margin
- Maximum pull-up resistor affects the rise time and speed
 - Increasing pull-up resistor above RMAX leads to slower/possible rise time violation or lower speed
 - Decreasing pull-up resistor below RMAX leads to faster rise time and speed



Bus Loading and Timing Relationship

The I²C bus specifications require certain bus rise times. Those times are defined with the time measured between the bus LOW and HIGH limit levels of 30% and 70% of VDD.

From the expression V (t) = VDD* $(1 - 1 / e^{t/\tau})$, and as shown on the curve at the right, the time for the bus to rise to 30%VDD is 0.357τ .

The time to rise to 70%VDD is 1.204 τ , so the I²C rise time, to rise from 30% to 70% of VDD,

is
$$(1.204 - 0.357) = 0.847^*\tau$$
.

Because $\tau = RC$, meeting the I²C rise time requirements means the pull-up "R" and bus capacitance "C" must satisfy the relationship:


0.847 RC <= I²C rise time specification

or RC \leq I²C rise time specification / 0.847

or $RC \le I^2C$ rise time specification x 1.18


For example, to meet the Fast-mode 300 ns rise requirement, the RC product must be less than

1.18 x 300 <= 354 ns.

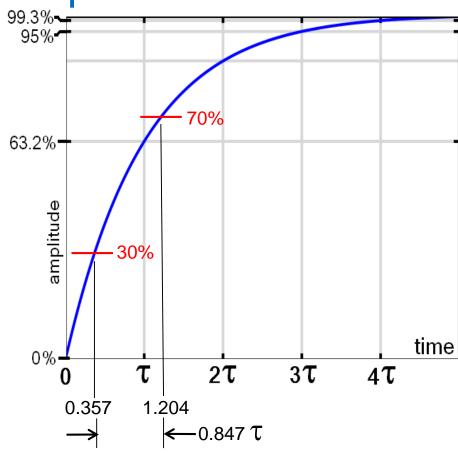

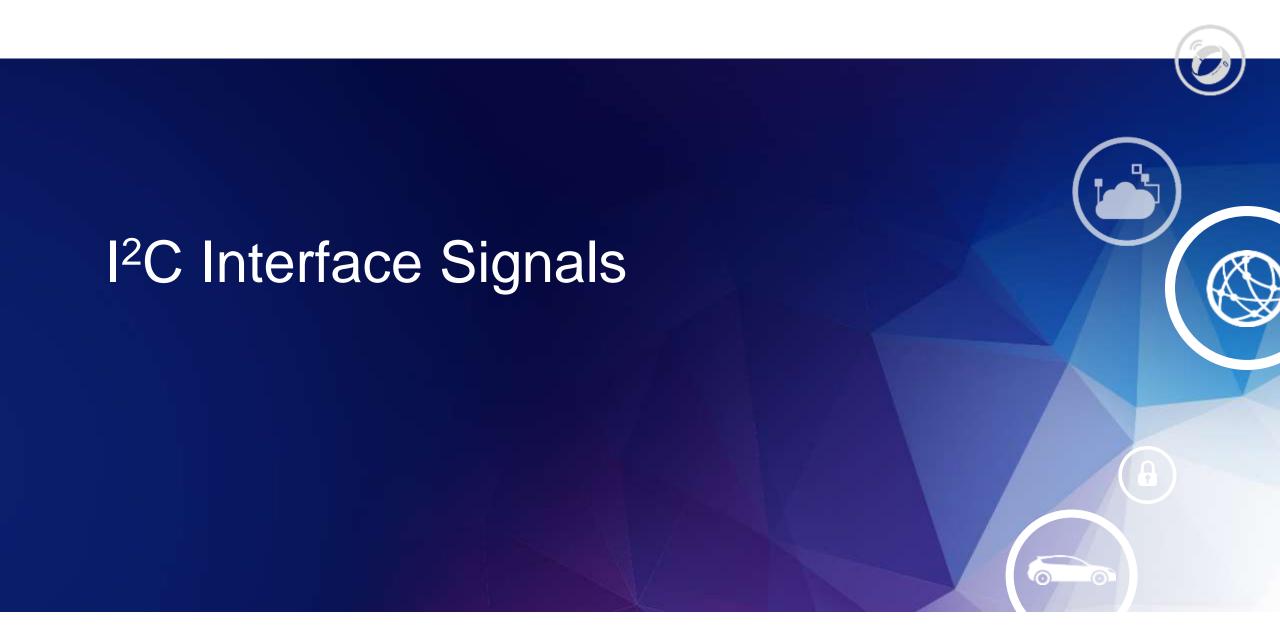
 τ = RC. R= Ohms, C= Farads, t= secs. I²C rise time requirement = 0.847RC 1/0.847 = 1.18 RC requirement < 1.18 x I²C rise time







I²C Logic Levels and Thresholds

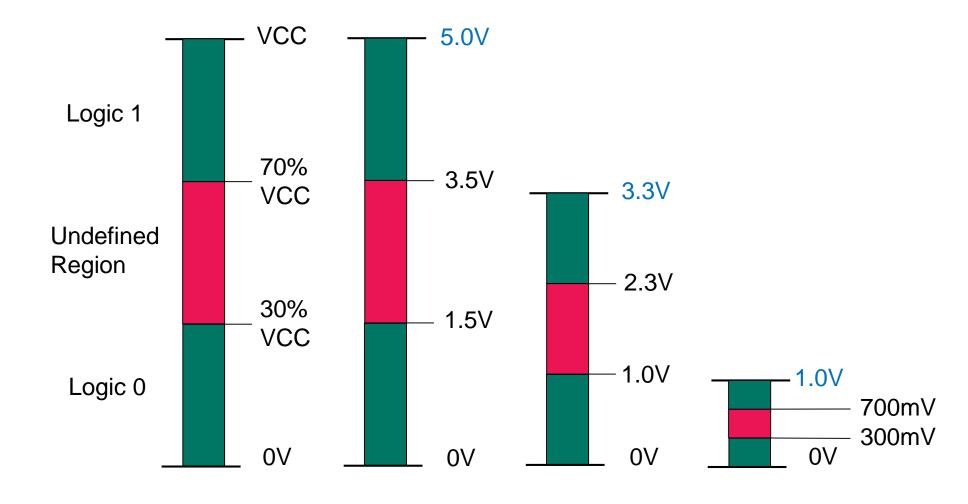







"Three Level" I²C Signals

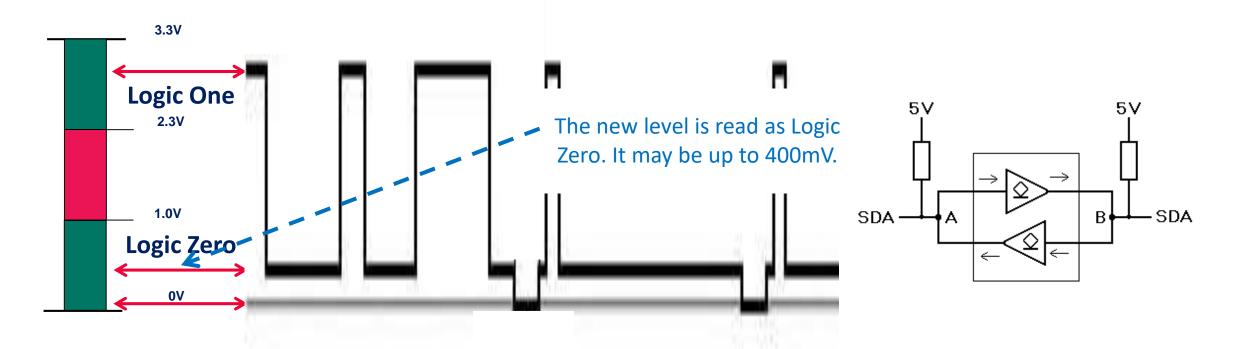- The I2C Bus has two logical levels (zero and one)
- There are now 3 signal levels, but only 2 logical levels
- This is caused by different strength Drivers, or by Bus Buffer "Offset"






I²C Signals (Oscilloscope Plot)

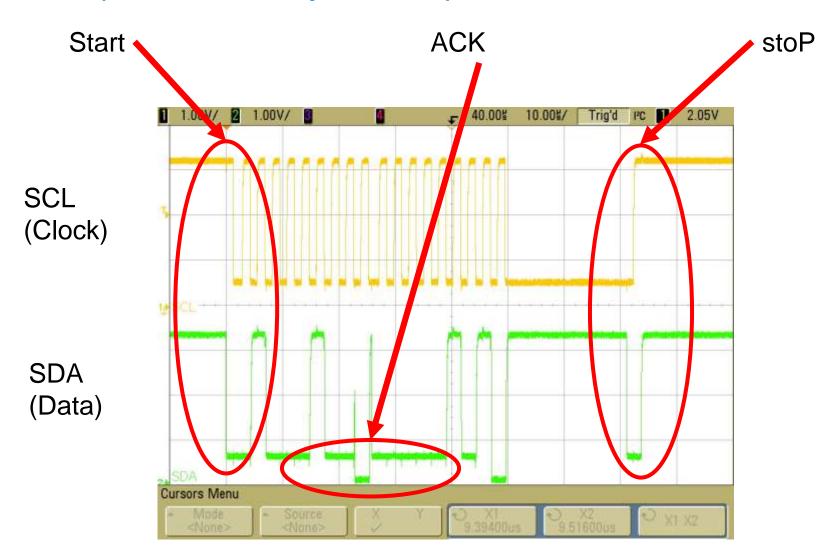




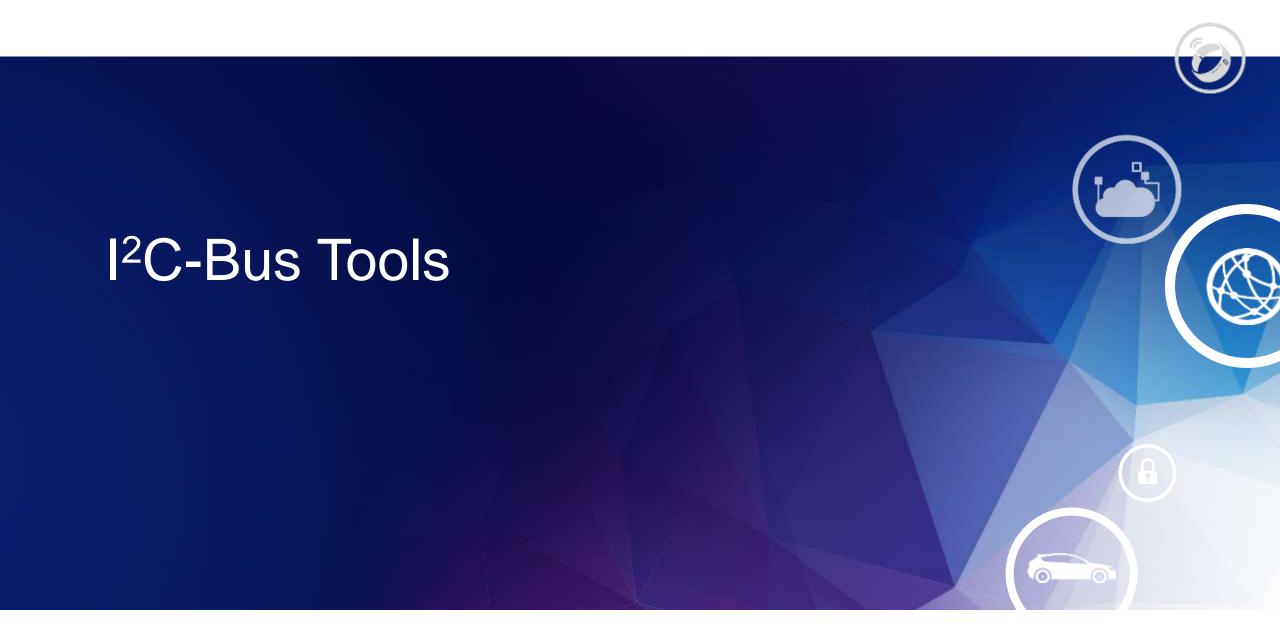




Fm+ I²C-Bus Demonstration System

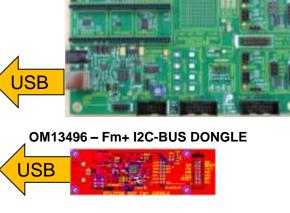PC/GUI **MASTER Total Phase Aardvark USB** The Boardshop Win-I2CUSB DLL Dongle Wire adapter OM13260 - Fm+ I2C-BUS DEVELOPMENT BOARD



SLAVE

OM13490 - DIP EVM BOARD

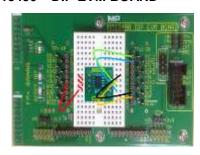

OM13303 - GPIO TARGET



OM13399 - BRIDGE BOARD



OM13488 - 16-bit GPIO **Daughter Card**



DIP ADAPTER BOARD



OM13398 - PCA9617A BUS BUFFER BASE BOARD



OM13487 - LM75 type TS **Daughter Card**





Fm+ I²C-Bus Development Board Kit (OM13320)

Box Content

OM number	12 NC Number	Description (50 Chrs max)	Description (35 Chrs max)	NXP Device Cross Reference
OM13260	9352 959 14598	FM+ I2C-bus Development Board (RoHS)	FM+ I2C-bus Dev Brd (RoHS)	PCA9665, PCA9672, PCA9901, PCA9955
OM13303	9352 959 15598	GPIO Target Board (RoHS)	GPIO Target Brd (RoHS)	none
OM13398	9353 020 74598	PCA9617A Bus Buffer Demo Brd (RoHS)	PCA9617A Bus Buffer Brd (RoH)	- Contract of the Contract of
OM13300	0353 020 75508	Bridge Board (Onin to Em+) (RoHS)	Bridge Board (Onin to Em+) (RoH	

Fm+ Development Board Kit OM13320





- Explore the I2C-Bus
- Run demonstrations of NXP's I2C Fm+ Slaves and Bus Controllers
- Develop I2C Hardware
- Expand this kit with add-on I2C Daughter Cards

BOX CONTENTS:

OM13260 Fm+ Development Board


Plu

- OM13303 GPIO Target BRD (x2)
- OM13398 PCA9617A Bus Buffer Demo Board
- OM13399 Bridge Board
- Cables and Mounting Hardware





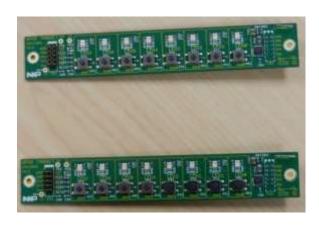Fm+ I²C-Bus Development Board Kit (OM13320)



GPIO Target Board OM13303 (2x)



Bus Buffer Board OM13398



Fm+ Development Board OM13260




Bridge Board OM13399




DIP Adapter Boards

Breakout Board (A through G)

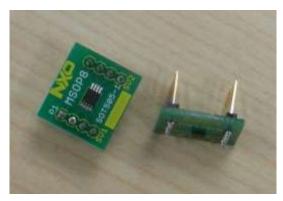
- Prepare any I²C device as a DIP module for the Fm+ I²C Bus EVM Board OM13490
- UM10754 (https://www.nxp.com/docs/en/user-guide/UM10754.pdf)




Example DIP Adapters

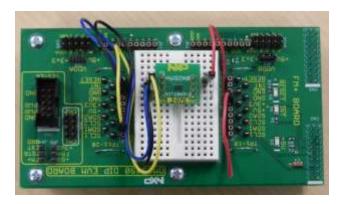

Example set up

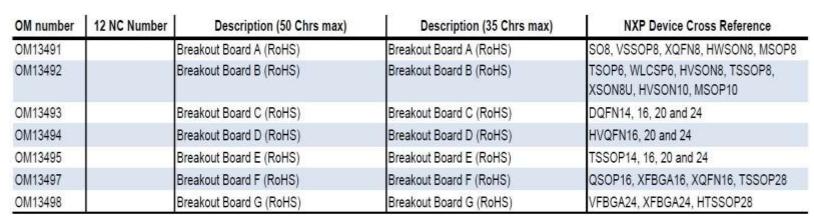

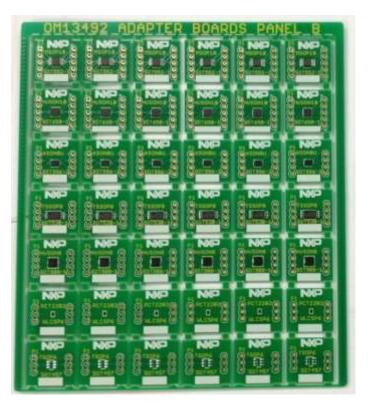




Total Phase Debugging Tools

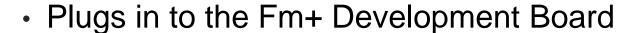- Third party, industry leading, diagnostic tools
- Aardvark (I²C Host Adapter)





Plugs in to the new Daughter Cards (allows standalone operation)








Aardvark (Master) and Beagle (Monitor)

- Third Party tools for I²C control and data logging
- Bundled software (for Win7/64, MAC, Linux)
- Not supplied by NXP (buy your own tools)

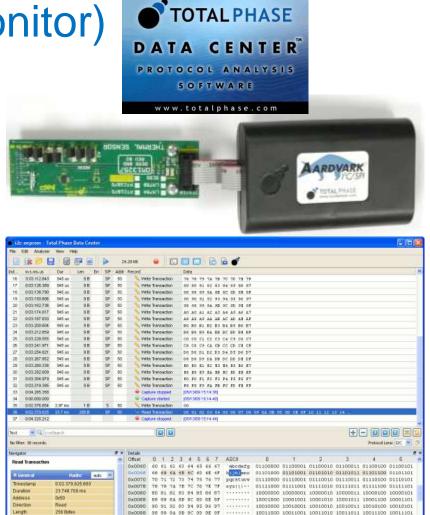http://www.totalphase.com/products/beagle_ism/





https://www.totalphase.com/products/aardvark-i2cspi/



ORODAS AS AS AS AS AC AD AE AF

0x00 0x01 0x02

End of Packet

18101600 10161001 10161018 10161611 16161100 10161101

Key NXP Contacts

- Product Marketing Director
 - Giovanni Genna
 - Office: +41 (0)44 454 7767
 - Giovanni.Genna@nxp.com
- Product Marketing Manager
 - Steve Blozis
 - Office: 408-518-5384
 - Stephen.Blozis@nxp.com
- Technical Marketing Manager
 - Emmanuel T. Nana
 - Office: 408-518-5306
 - Emmanuel.Nana@nxp.com
- Regional Marketing Manager
 - Ravi Shah
 - Office: 408-518-5309
 - Ravi.Shah@nxp.com





SECURE CONNECTIONS FOR A SMARTER WORLD