AN11184

Low Noise Fast Turn ON/OFF 5-5.9GHz WiFi LNA with BFU768F

Rev. 2 — 8 December 2015 Application note

Document information

Info	Content
Keywords	BFU768F, 5-5.9GHz LNA, WiFi (WLAN)
Abstract	This document provides circuit simulation, schematic, layout, BOM and typical EVB performance for a 5-5.9GHz WiFi (WLAN) LNA

Revision history

Rev	Date	Description
2	20151208	Updated simulation and measurement results
1	20121009	Initial publication

Contact information

For additional information, please visit: http://www.nxp.com

For sales office addresses, please send an email to: salesaddresses@nxp.com

1. Introduction

The BFU768F is a discrete HBT that is produced using NXP Semiconductors' advanced 110 GHz fT SiGe:C BiCmos process. SiGe:C is a normal silicon germanium process with the addition of Carbon in the base layer of the NPN transistor. The presence of carbon in the base layer suppresses the boron diffusion during wafer processing. This allows a steeper and narrower SiGe HBT base and a heavier doped base. As a result, lower base resistance, lower noise and higher cut off frequency can be achieved.

The BFU768F is one of a series of transistors made in SiGe:C.

BFU710F, BFU730F and BFU790F are the other types. BFU710F is intended for ultra low current applications. The BFU768F and BFU790F are high current types and are intended for application where linearity is key.

New 6th & 7th Generation Wideband transistors from NXP offer best RF noise figure / gain tradeoff at 12GHz drawing lowest current which means best signal reception at low power, enabling products to be more sensitive in noisy environments and friendlier to the environment.

Key Benefits:

- Application up to 18 GHz and higher
- Broad choice of parts for the perfect fit in the application
- Lowest current consumption meaning greener products

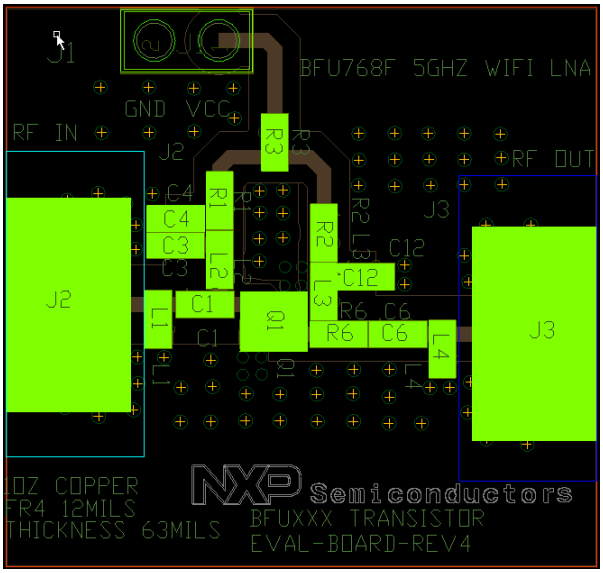

Fig 1. BFUXXX Universal Demo Board/BFU768F 5-5.9GHz WiFi LNA EVB Demo Board

- SOT343F package for high performance and easy manufacturing

2. Requirements and design of the 5-5.9GHz WiFi LNA

The circuit shown in this application note is intended to demonstrate the performance of the BFU768F in a 5-5.9 GHz LNA for e.g. 802.11a/b/g & 802.11n “MIMO” WiFi (WLAN) applications.

Key requirements for this application are:

- Frequency Band 5 – 5.9GHz
- Gain
- Input/output Match
- Linearity
- NF
- Turn ON/OFF Time

3. Design and Simulation

The 5-5.9 GHz WiFi LNA consists of one stage BFU768F amplifier. For this amplifier the minimum number of external components is used for low cost purpose:

- 1 multilayer chip inductor, lower cost comparing to wirewound type
- 4 resistors
- 4 capacitors

The design has been simulated using QUCS (version 0.0.18), and the simulation results are given in the following figures.

The LNA shows excellent match at input/output with greater than 10dB return loss and gain of greater than 10dB with superior Noise Figure of 1.19dB.

With only 10.8mA it also shows a high input P_{1dB} compression of -3.8dBm, as well as high input IP3 of +5.1dBm.

The LNA Turn ON and OFF time are 300nS and 30nS respectively.

The designed LNA is unconditionally stable at 10 MHz-20 GHz.

3.1 BFU768F 5-5.9GHz WiFi LNA Simulation

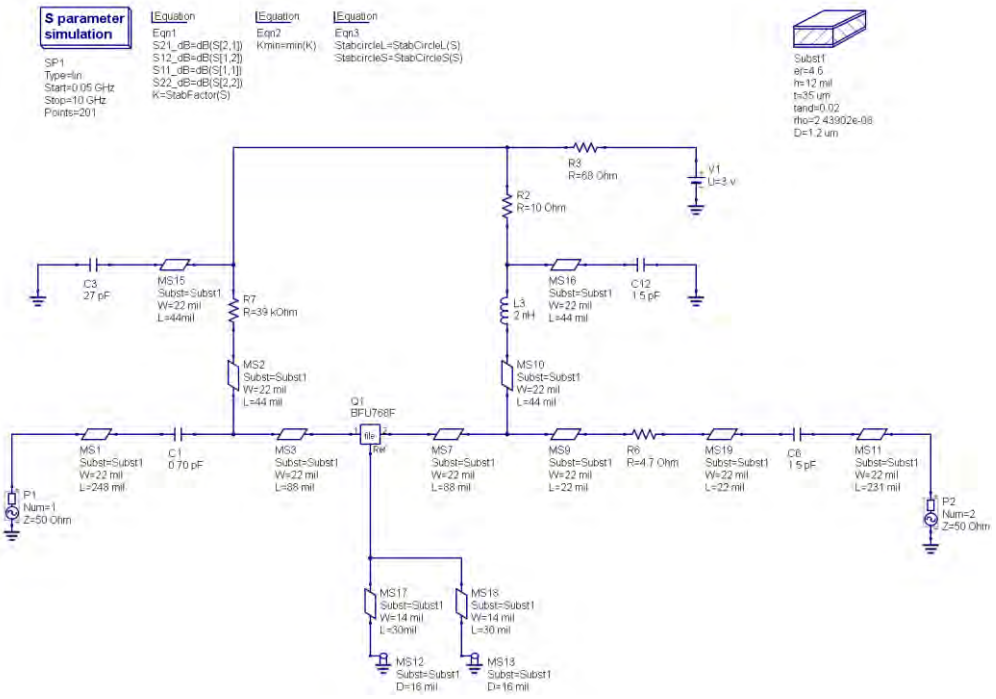

Fig 2. BFU768F 5-5.9GHz WiFi LNA Simulation: Circuit

3.2 BFU768F 5-5.9GHz WiFi LNA Simulation Result

3.2.1 Gain and Match in 5-5.9GHz Band

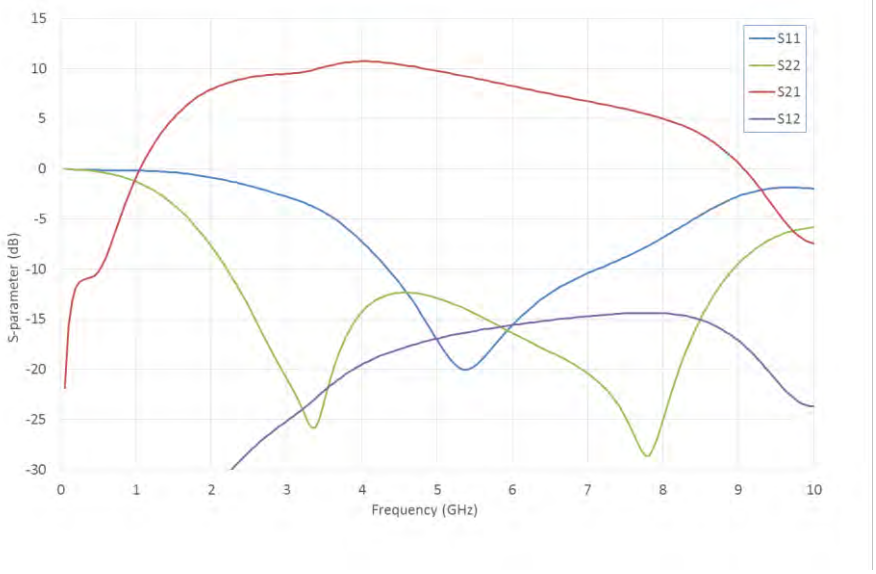

Fig 3. BFU768F 5-5.9GHz WiFi LNA Simulation: Gain and Match

3.2.2 Noise Figure in 5-5.9GHz Band

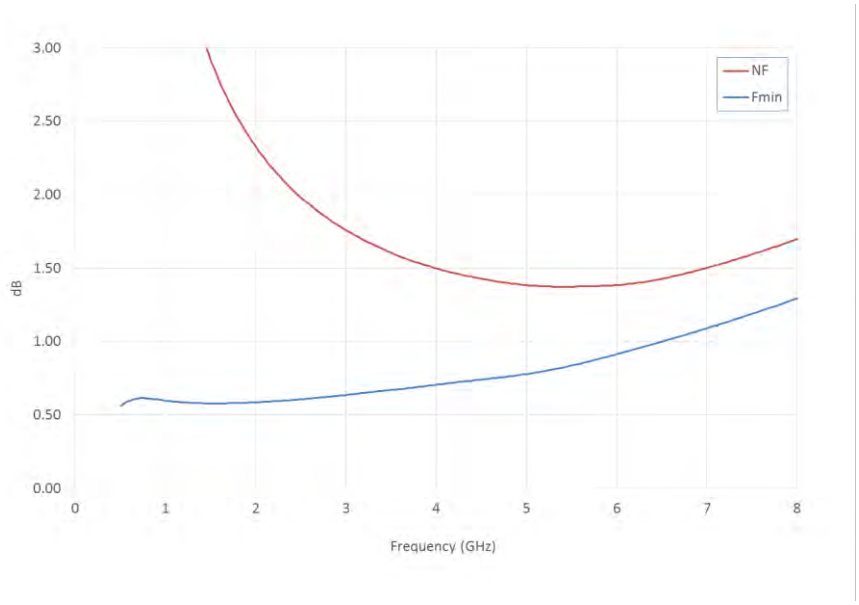

Note: the simulated NF includes the loss at input and output(no de-embedding)

Fig 4. BFU768F 5-5.9GHz WiFi LNA Simulation: Noise Figure

3.2.3 Stability

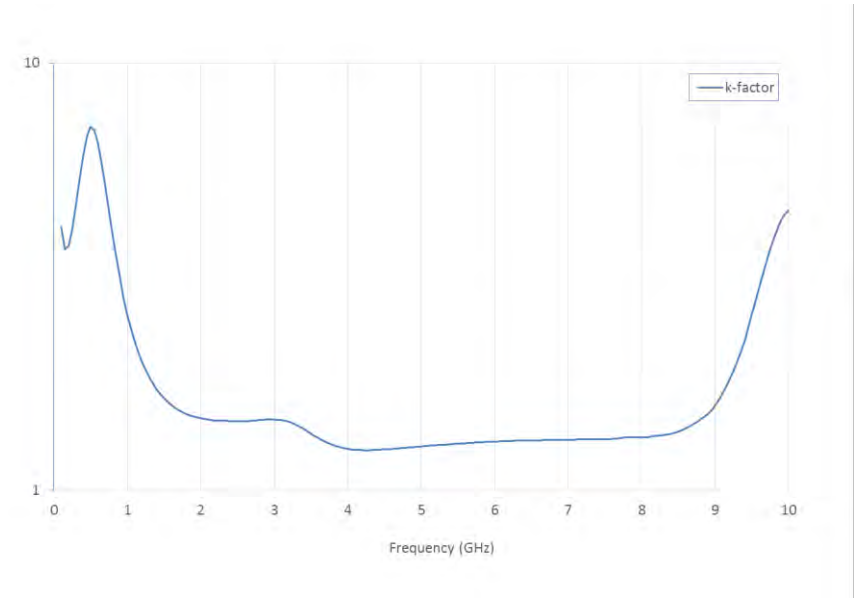

Fig 5. BFU768F 5-5.9GHz WiFi LNA Simulation: Stability

4. Application Board

The 5-5.9GHz WiFi LNA evaluation board simplifies the evaluation of the BFU768F application. The evaluation board enables testing of the device performance and requires no additional support circuitry. The board is fully assembled with the BFU768F transistor, including input and output matching components, to optimize performance.

The board is supplied with two SMA connectors for input and output connection to RF test equipment.

4.1 Application Circuit Schematic

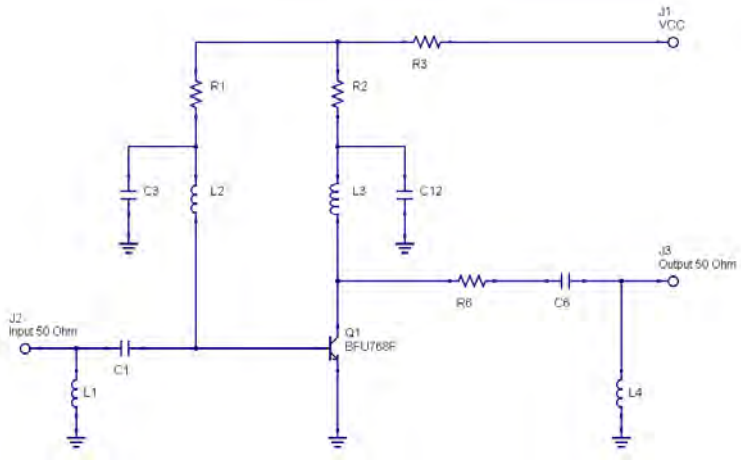

Fig 6. BFUXXX Universal Demo Board: Schematic

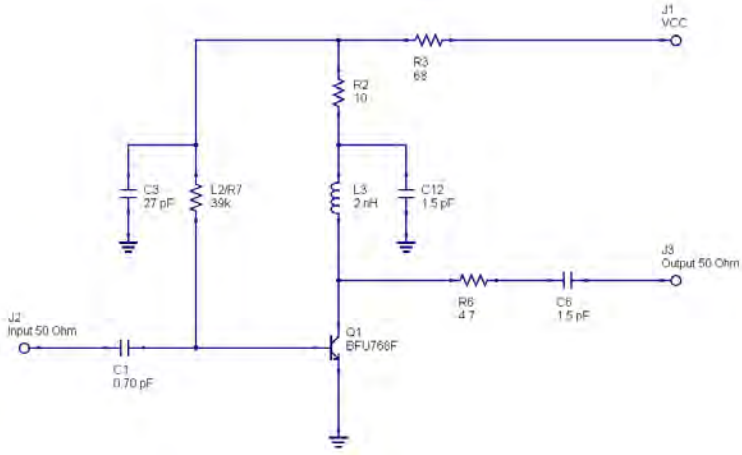

Fig 7. BFU768F 5-5.9GHz WiFi LNA: Schematic

Note: Figure 6 is the schematic for BFUXXX universal demo board, some assembly changes are made to accommodate this simplified low cost design, the revised schematic is shown in figure 7, and the changes are as following:

1. L1, L2, L4: not populated
2. Move R1 (39K) to L2 location, short two solder pads of R1 or put a 0 ohm jumper

4.2 Application Board Bill-Of-Material

Table 1. BFU768F 5-5.9GHz WiFi LNA Part List

Customer can choose their preferred vendor but should be aware that the performance could be affected.

Item	Quantity	Reference	Part Number	Value	Vendor
1	1	C1	GRM1555C1HR70BA01D	0.70pF	Murata
2	1	C3	GRM1555C1H270JZ01D	27pF	Murata
3	2	C6,C12	GRM1555C1H1R5CZ01D	1.5pF	Murata
4	1	J1	90120-0762	CON-2PIN	Molex
5	2	J2,J3	142-0701-841	CON-SMA	Johnson
6	1	L3	LQG15HS2N0S02D	2nH	Murata
7	1	Q1	BFU768F	BFU768F	NXP SEMICONDUCTORS
8	1	L2/R7	ERJ-2RKF3902X	39K	Panasonic - ECG
9	1	R2	ERJ-2RKF10R0X	10	Panasonic - ECG
10	1	R3	ERJ-2RKF68R0X	68	Panasonic - ECG
11	1	R6	ERJ-2GEJ4R7X	4.7	Panasonic - ECG

4.3 Typical Application Board Test Result

4.3.1 S-Parameter – Gain and Match (On State)

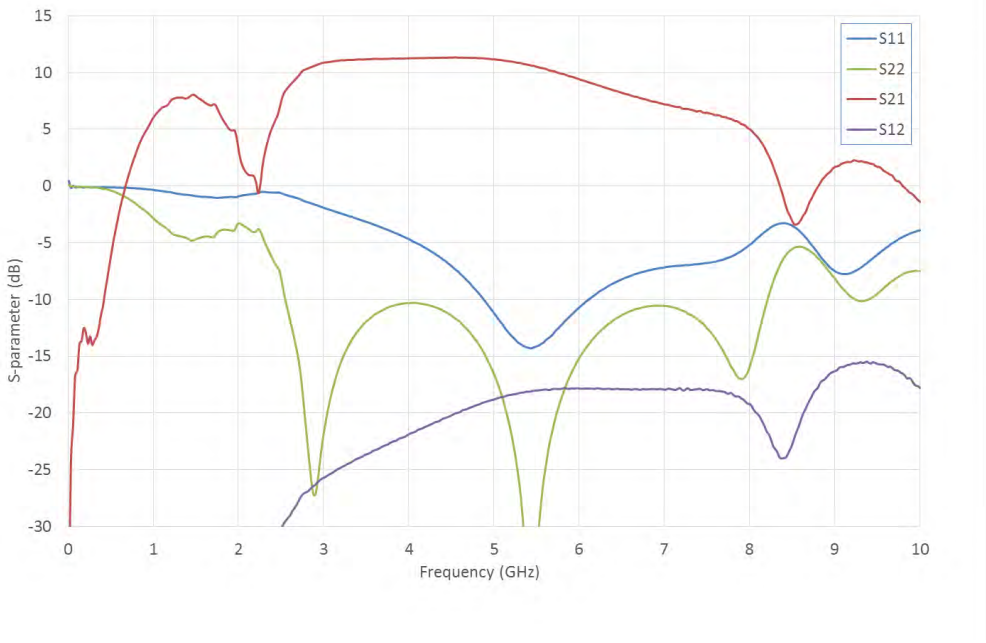

Fig 8. BFU768F 5-5.9GHz WiFi LNA: S-Parameter

4.3.2 S-Parameter – Gain and Match (Off State)

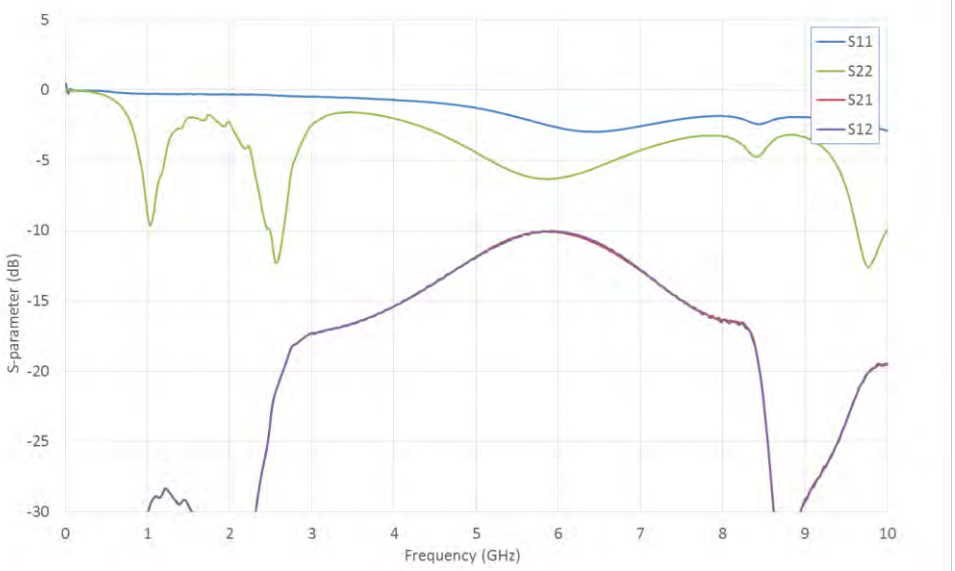

Fig 9. BFU768F 5-5.9GHz WiFi LNA: S-Parameter

4.3.3 P1dB

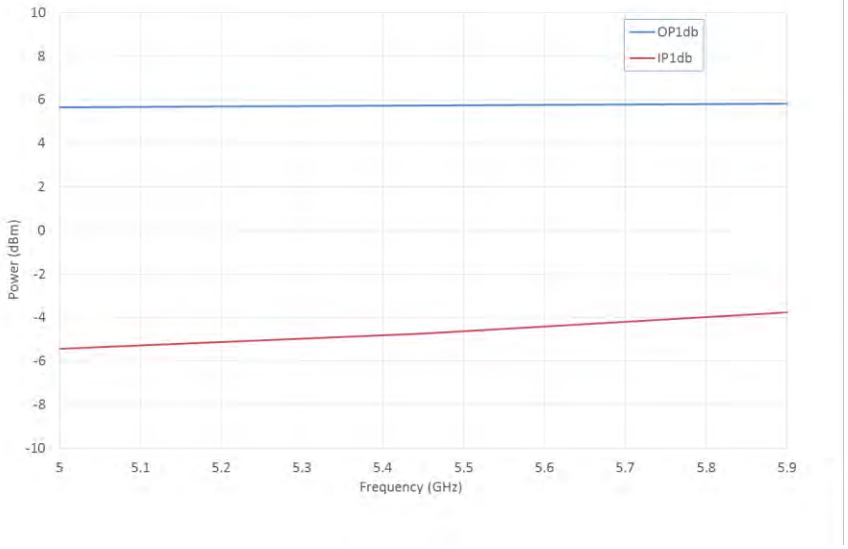

Fig 10. BFU768F 5-5.9GHz WiFi LNA: P1dB

4.3.4 Linearity/IP3

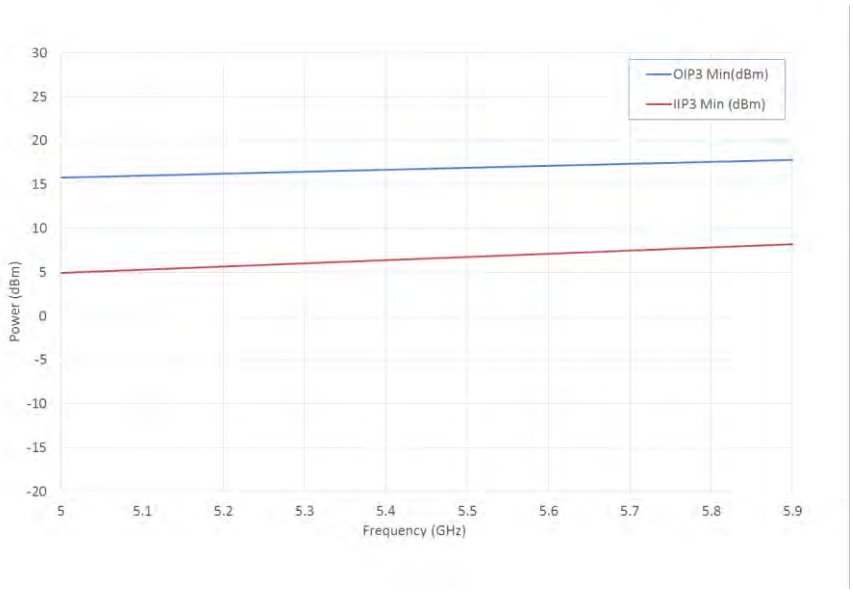

Tone spacing: 1MHz

Fig 11. BFU768F 5-5.9GHz WiFi LNA: IP3

4.3.5 Stability

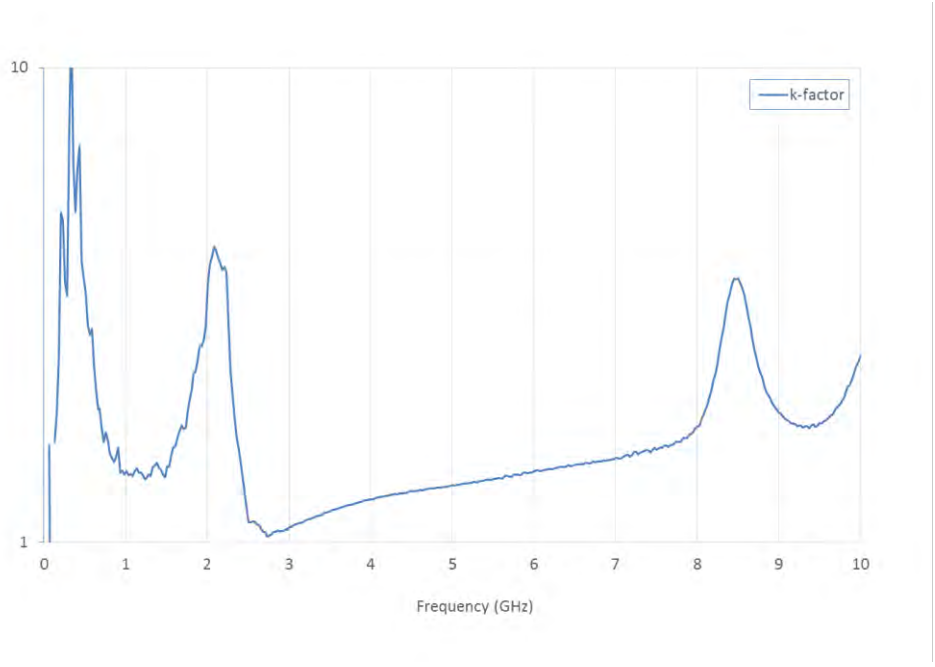

Fig 12. BFU768F 5-5.9GHz WiFi LNA: Stability

4.3.6 Noise Figure Measurement

A network analyzer is used to measure the loss between the connector input to the first matching component of the device. The measured return loss is approximately 0.4dB across the band, therefore a 0.2dB input loss must be de-embedded to get device noise figure.

The Noise figure data in the graphic below is the noise figure after de-embedding the connector and input loss.

Fig 13. BFU768F 5-5.9GHz WiFi LNA: Noise Figure

4.3.7 LNA Turn ON-OFF Time

The following diagram shows the setup to test LNA Turn ON and Turn OFF time. The LNA Turn ON and Turn OFF time are mainly determined by the R-C time constant of the biasing circuitries: on the Base bias path the τ1 = R3*C3 and on the Collector bias path τ2 = (R2+R3)*C12.

Set the waveform generator to square mode and the output amplitude at 3Vpeak (0V low) with 50Ω output impedance. The waveform generator has adequate output current to drive the LNA therefore no extra DC power supply is required which simplifies the test setup.

Set the RF signal generator output level to -20dBm at 5.5GHz and increase its level until the output DC on the oscilloscope is at 5mV on 1mV/division, the signal generator RF output level is approximately -15dBm.

It is very important to keep the cables as short (same length) as possible at input of the oscilloscope (CH1 /trigger) and Vcc of the LNA so the propagation delay difference on cables is minimized.

It is also critical to set the oscilloscope input impedance to 50ohm on channel -1 (keep Vcc at 3V, otherwise 6V on LNA Vcc) & -2 the diode detector can discharge quickly to avoid a false result on the Turn OFF time testing.

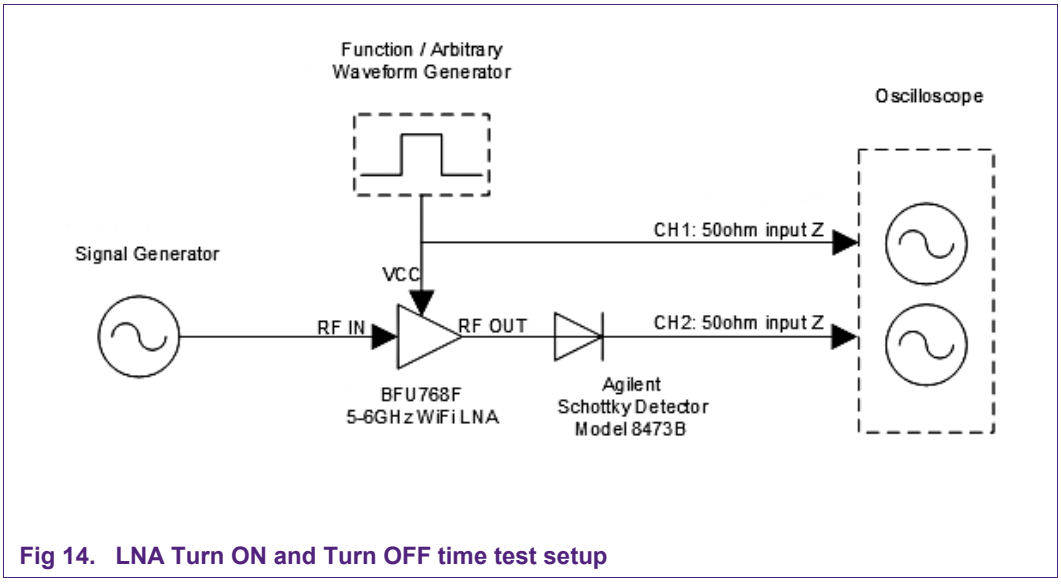

Fig 14. LNA Turn ON and Turn OFF time test setup

4.3.7.1 LNA Turn ON Time

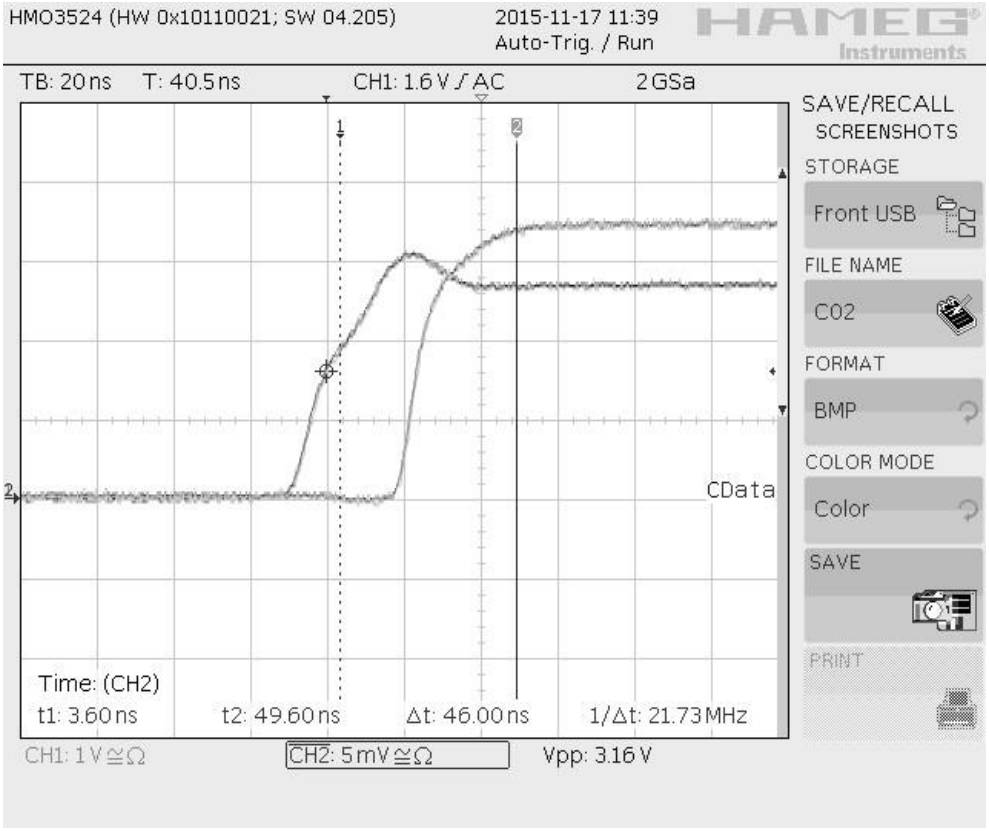

3.0Vrms, 200Hz and 50% duty cycle pulse applied on VCC pin, measured from 50% of input pulse to 90% of max. output power

Fig 15. BFU768F 5-5.9GHz WiFi LNA: Turn ON time

4.3.7.2 LNA Turn OFF Time

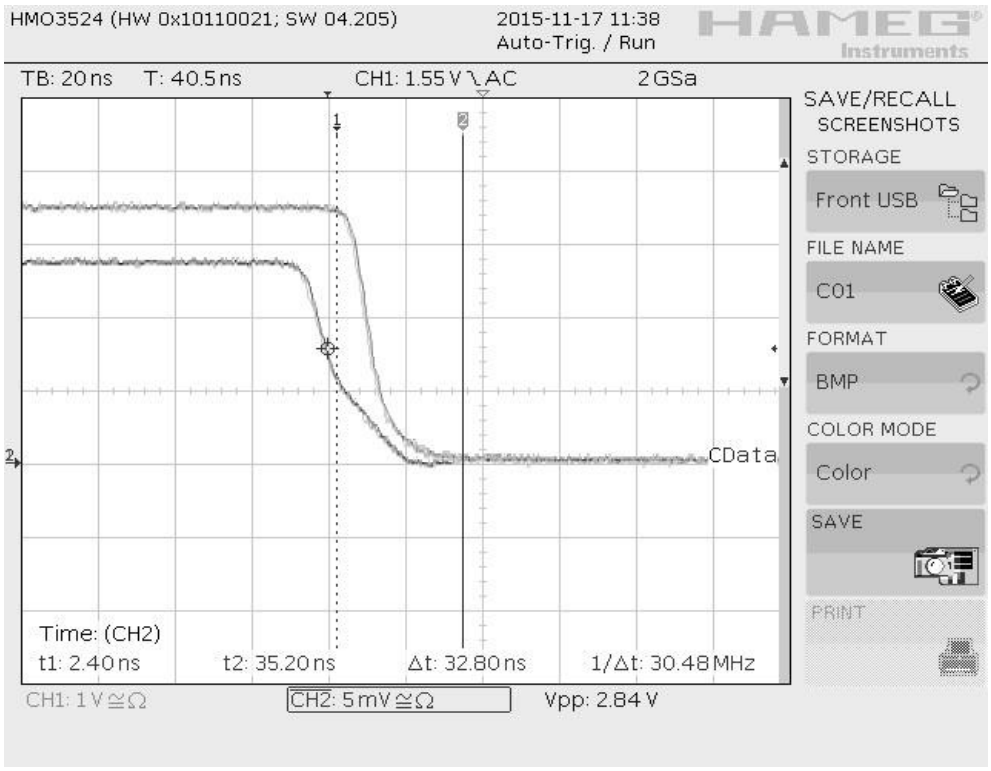

3.0Vrms, 200Hz and 50% duty cycle pulse applied on VCC pin, measured from 50% of input pulse to 10% of max. output power

Fig 16. BFU768F 5-5.9GHz WiFi LNA: Turn OFF time

4.3.8 Summary Of the Typical Evaluation Board Test Result

Table 2. Typical results measured on the BFU768F 5-5.9GHz WiFi LNA Evaluation Board

Operating frequency 5-5.9GHz, testing at 5GHz and 5.9GHz unless otherwise specified, Temp = 25°C.

Parameter		Symbol	Value	Unit
Supply Voltage		Vcc	3.0	V
Supply Current		Icc	11.0	mA
Noise Figure	@5GHz	NF	1.39	dB
	@5.9GHz	NF	1.39	dB
Power Gain	@5GHz	Gp	11.1	dB
	@5.9GHz	Gp	9.6	dB
Input Return Loss	@5GHz	IRL	11.2	dB
	@5.9GHz	IRL	11.7	dB
Output Return Loss	@5GHz	ORL	16.3	dB
	@5.9GHz	ORL	16.3	dB
Reverse Isolation	@5GHz	ISLrev	18.8	dB
	@5.9GHz	ISLrev	17.9	dB
Input 1dB Gain Compression Point	@5GHz	Pi1dB	-5.4	dBm
	@5.9GHz	Pi1dB	-3.8	dBm
Output 1dB Gain Compression Point	@5GHz	PL1dB	5.7	dBm
	@5.9GHz	PL1dB	5.8	dBm
Input Third Order Intercept Point Two Tones: f1: 5.9GHz, f2: 5.901GHz, power: -20dBm	@5.9GHz	IIP3	5.1	dBm
Output Third Order Intercept Point Two Tones: f1: 5.9GHz, f2: 5.901GHz, power: -20dBm	@5.9GHz	OIP3	15.9	dBm
Stability (0- 20GHz)		K	>1	
LNA Turn ON/OFF Time		Ton	50	ns
		Toff	30	ns

5. Legal information

5.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

5.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

5.3 Licenses

Purchase of NXP <xxx> components
<License statement text>

5.4 Patents

Notice is herewith given that the subject device uses one or more of the following patents and that each of these patents may have corresponding patents in other jurisdictions.

<Patent ID> — owned by <Company name>

5.5 Trademarks

Notice: All referenced brands, product names, service names and trademarks are property of their respective owners.

<Name> — is a trademark of NXP B.V.

6. List of figures

7. List of tables

8. Contents

For more information, visit: http://www.nxp.com
For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: 8 December 2015
Document identifier: AN11184