

BSIM4 and MOS Model 11 benchmarks for MOSFET capacitances

UPDATED PRESENTATION
using new results from STm

A.J. Scholten, R. v. Langevelde, H.M.J. Boots, D.B.M. Klaassen,
Philips Research, Eindhoven, The Netherlands
and
G. Gouget, A. Juge,
STMicroelectronics, Central R&D, Crolles, France

contents

- **simulation conditions**
 - reproduction STMicroelectronics BSIM4 results (14 Dec 2000), but without junction and overlap capacitances
 - MOS Model 11
- **additional remarks**
- **simulation results**
 - reciprocity of capacitances at $V_{DS}=0V$
 - source / drain symmetry of capacitances at $V_{DS}=0V$
 - comparison qs / nqs capacitances at low frequency
 - comparison qs / nqs Y-parameters at high frequency
 - comparison qs / nqs: fast voltage ramp in transient
- **conclusions**

simulation conditions

- **BSIM4**
 - ELDO 5.4_1.1 (Beta version)
 - NMOS default parameters used with XPART=50/50
 - no junction capacitances; no overlap capacitances
 - low frequency sim.: NMOS device: $W= 10\mu\text{m}$, $L= 0.12\mu\text{m}$
 - high frequency sim.: NMOS device: $W= 10\mu\text{m}$, $L= 2\mu\text{m}$
- **MOS Model 11**
 - no junction capacitances; no overlap capacitances
 - only intrinsic MOS capacitances
 - NQS simulations using channel segmentation
(see Scholten et al., IEDM'99)
 - low frequency sim.: NMOS device: $W= 10\mu\text{m}$, $L= 0.18\mu\text{m}$
 - high frequency sim.: NMOS device: $W= 10\mu\text{m}$, $L= 2.5\mu\text{m}$

simulation conditions

- **ac analysis (low-frequency)**

- reciprocity
- drain/source symmetry
- QS / NQS

simulations are performed at $V_D=V_S=V_B=0V$ at 1kHz

- **ac analysis (high-frequency)**

- QS / NQS

magnitude and phase of admittance parameters Y_{XG} at $V_D=V_S=V_B=0V$ and $V_G=1.2$ or $1.8V$ from 1MHz to 10GHz

- **transient analysis applying fast voltage ramp to gate**

- QS / NQS

currents for voltage ramp of 1V/s applied to gate at $V_D=1.2V$ or $1.8V$ and $V_S=V_B=0V$

additional remarks

- **MOS Model 11**

- dc and ac capacitances are equal!

- **capacitance definition**

- $i \neq j$ $C_{ij} = -\frac{\partial Q_i}{\partial V_j}$

- $i = j$ $C_{ij} = \frac{\partial Q_i}{\partial V_j}$


- **$C_{ij} > 0$ holds, except for C_{DS} and C_{SD} !!**

- see e.g. eq. (9.2.37j) of
“Operation and Modeling of the MOS Transistor”,
Y. Tsividis, Second Edition, 1999
- checked with Medici simulations


reciprocity

- at $V_{DS}=0$ V one has $C_{ij}=C_{ji}$
 - checked with Medici simulations
 - investigated for $C_{bg}=C_{gb}$ with 2 surface-potential based compact model formulations
 - charge sheet
 - Pao-Sah

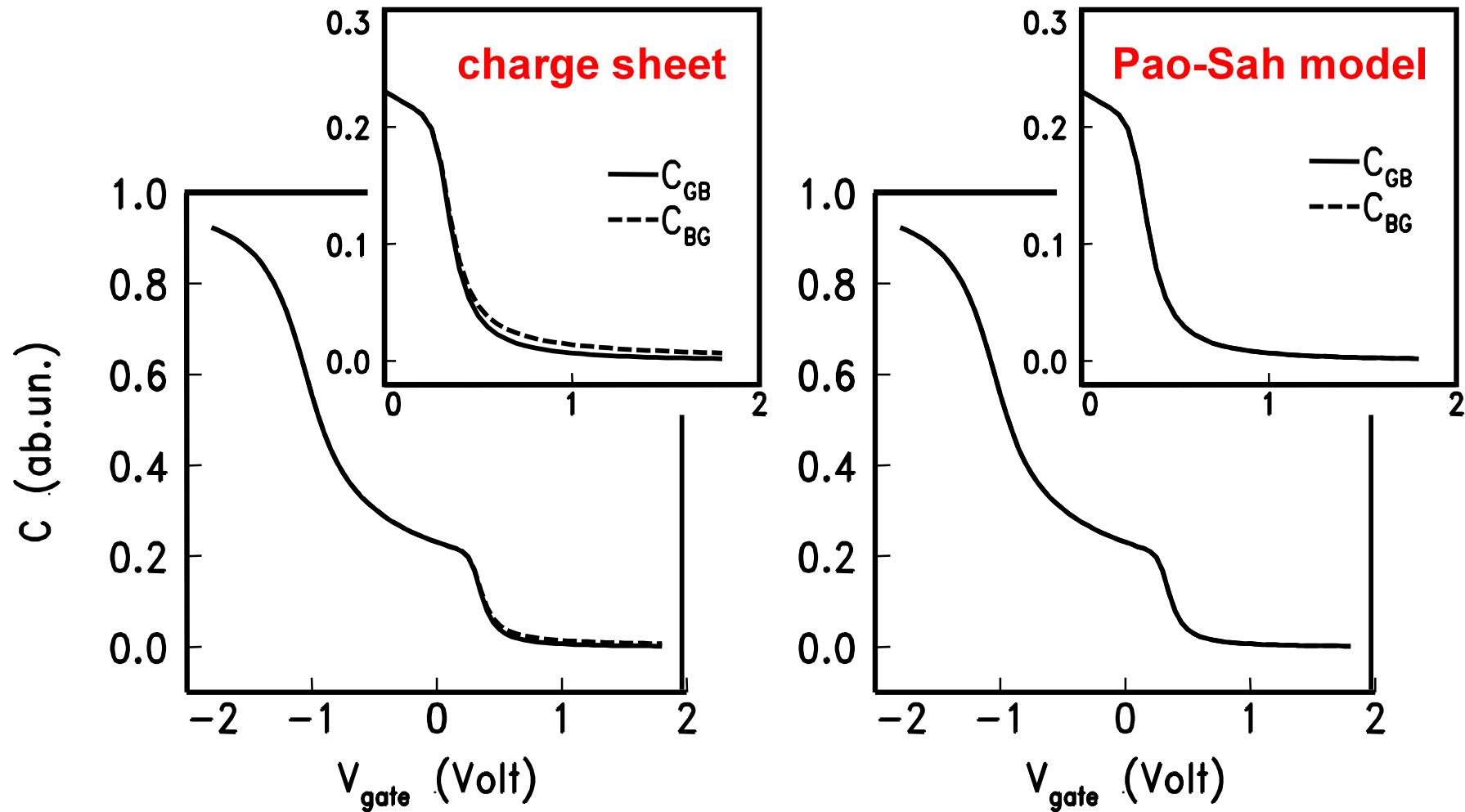
reciprocity: $C_{BG}-C_{GB}$ vs. V_G at $V_{DS}=0V$



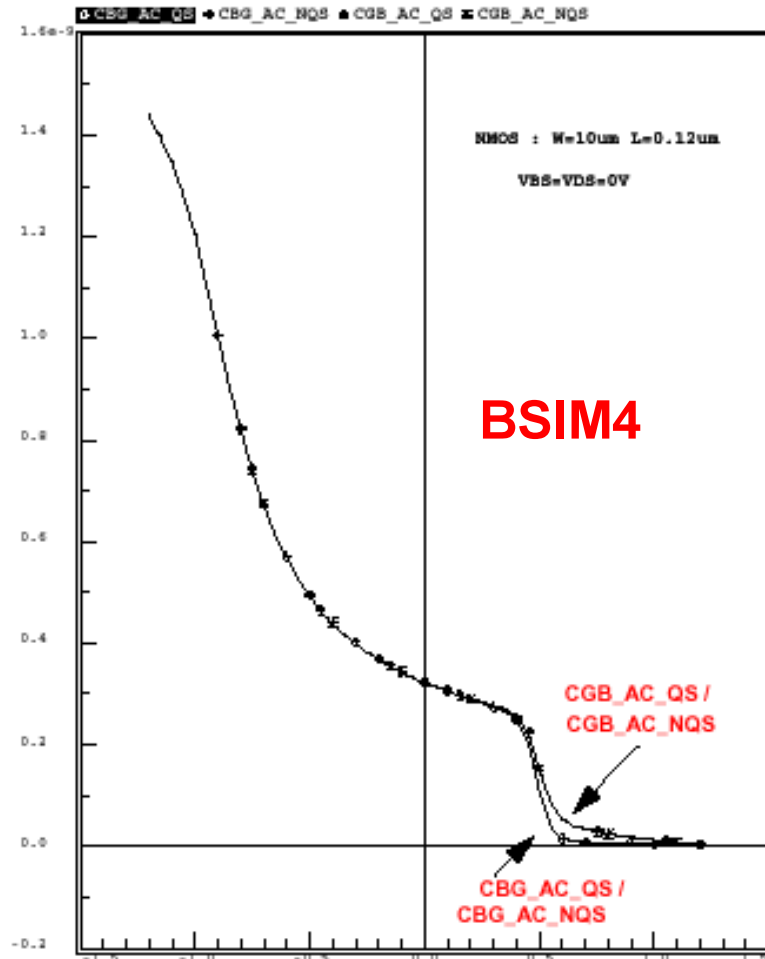reciprocity: $C_{BG}-C_{GB}$ vs. V_G at $V_{DS}=0V$




(NQS: ACNQSMOD=1)

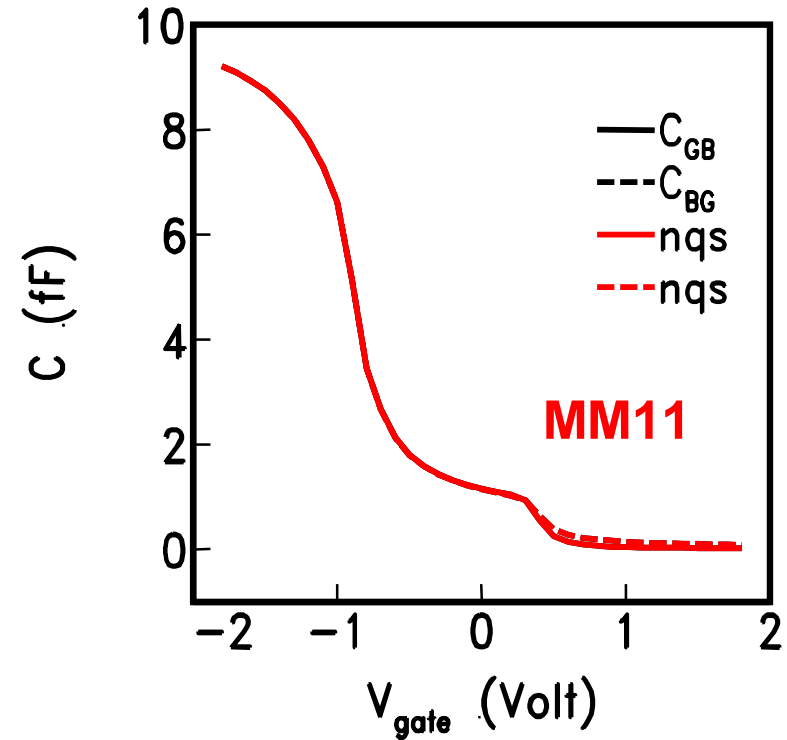


- QS=NQS
- C_{BG} and C_{GB} differ slightly

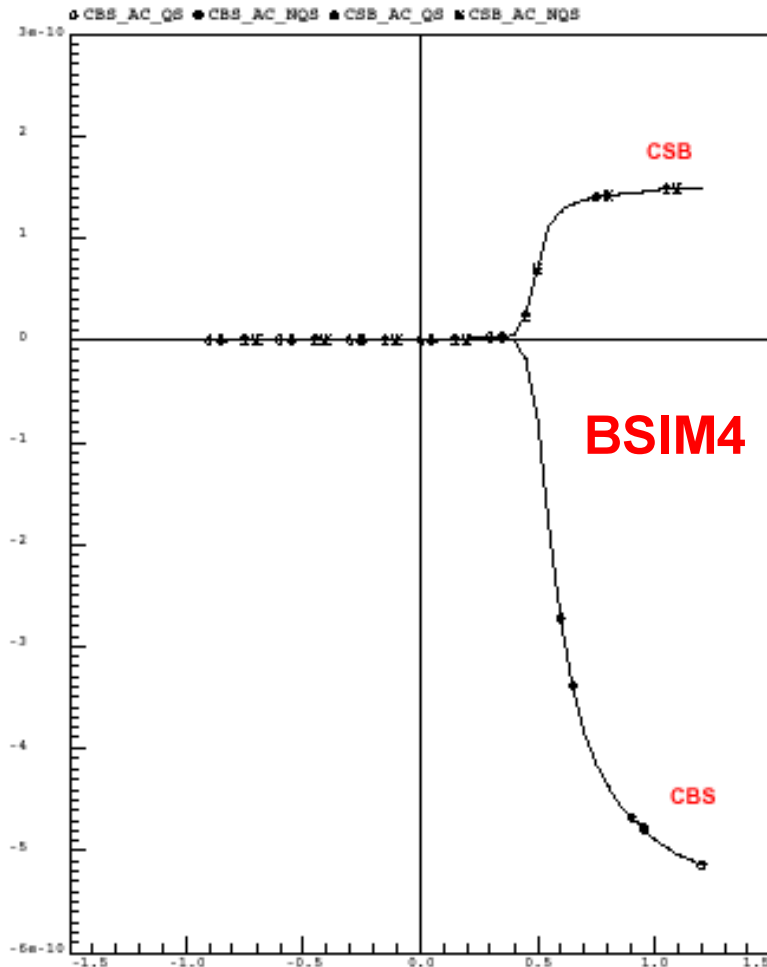reciprocity: $C_{BS}-C_{SB}$ vs. V_G at $V_{DS}=0V$





(NQS: ACNQSMOD=1)

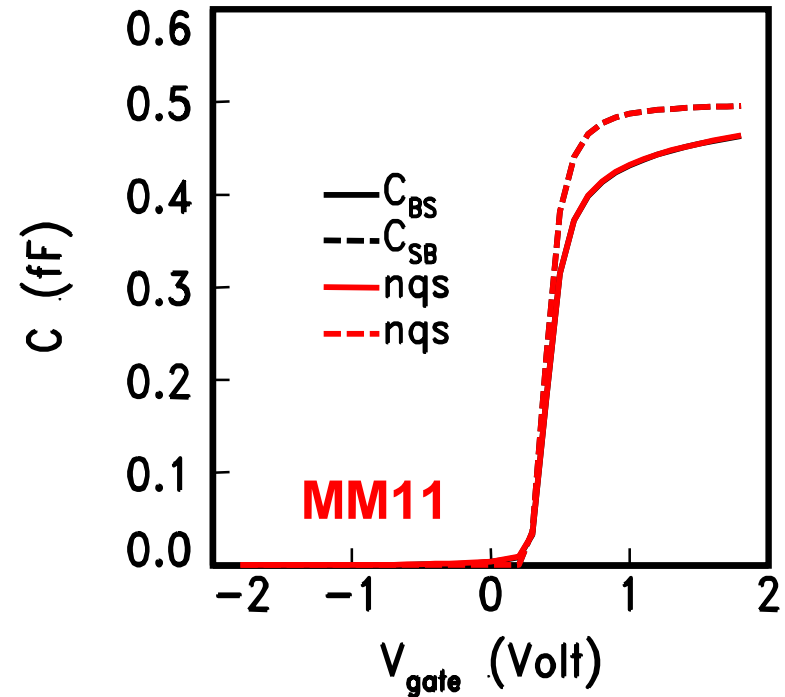



- QS=NQS
- BSIM4: $|C_{BS}|$ and C_{SB} differ factor 4
- BSIM4: C_{BS} is negative!
- MM11: C_{BS} and C_{SB} differ slightly

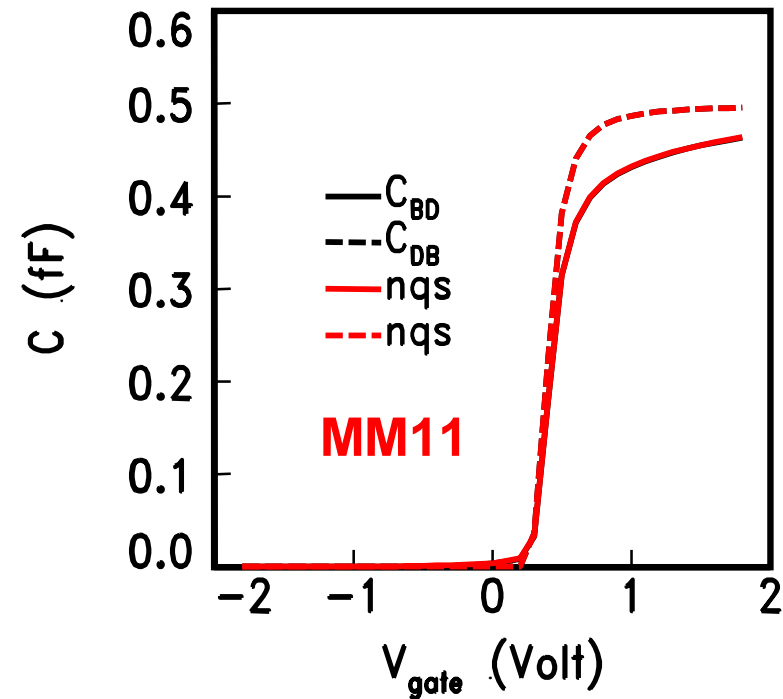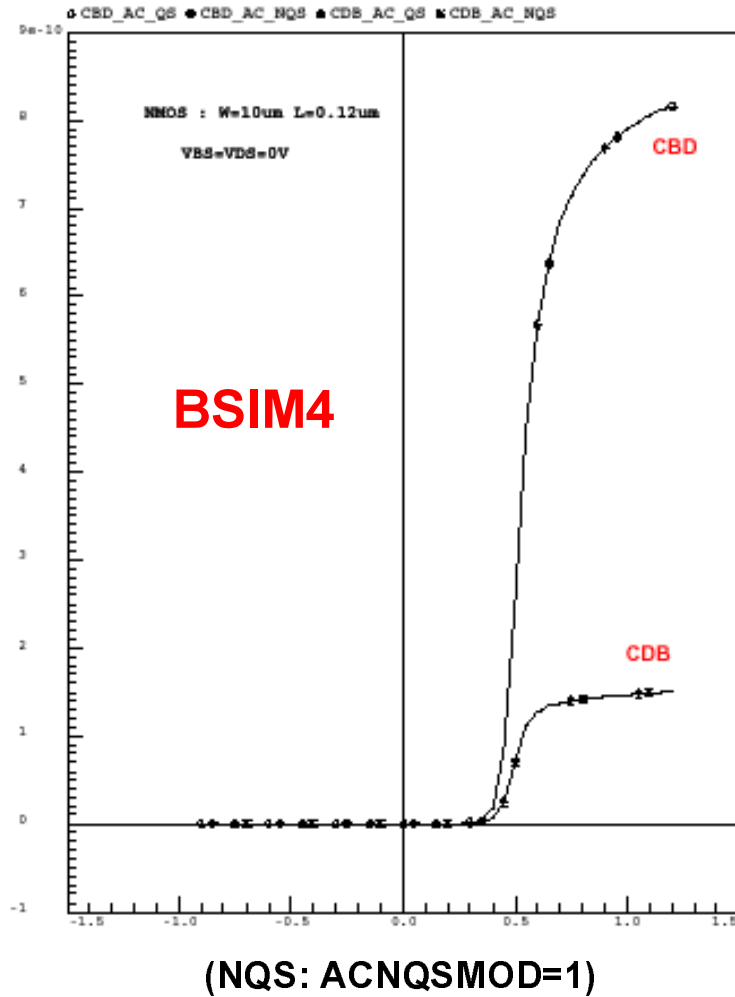reciprocity: $C_{BD}-C_{DB}$ vs. V_G at $V_{DS}=0V$




- QS=NQS
- BSIM4: C_{BD} and C_{DB} differ factor 4
- MM11: C_{BD} and C_{DB} differ slightly

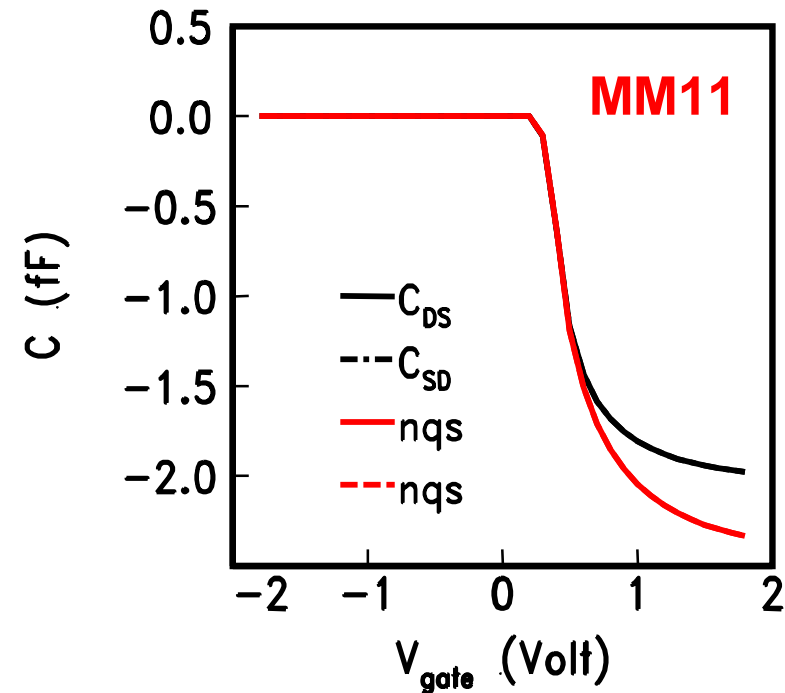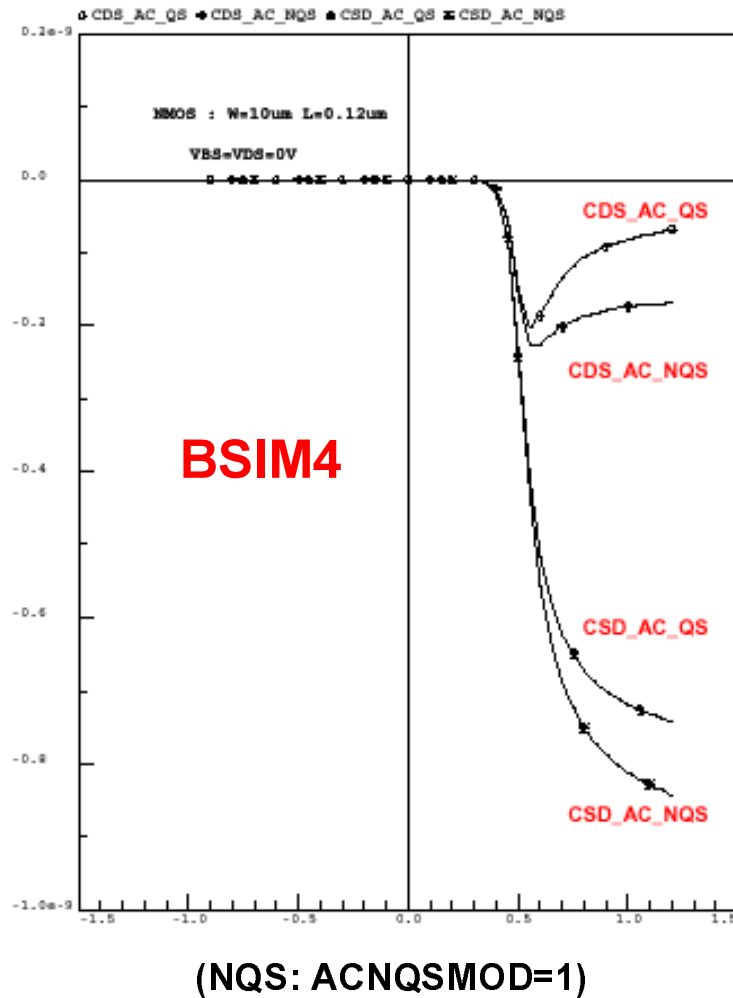reciprocity: $C_{DS}-C_{SD}$ vs. V_G at $V_{DS}=0V$




- QS and NQS differ slightly
- BSIM4: C_{DS} and C_{SD} differ factor 4
- MM11: C_{DS} and C_{SD} are equal

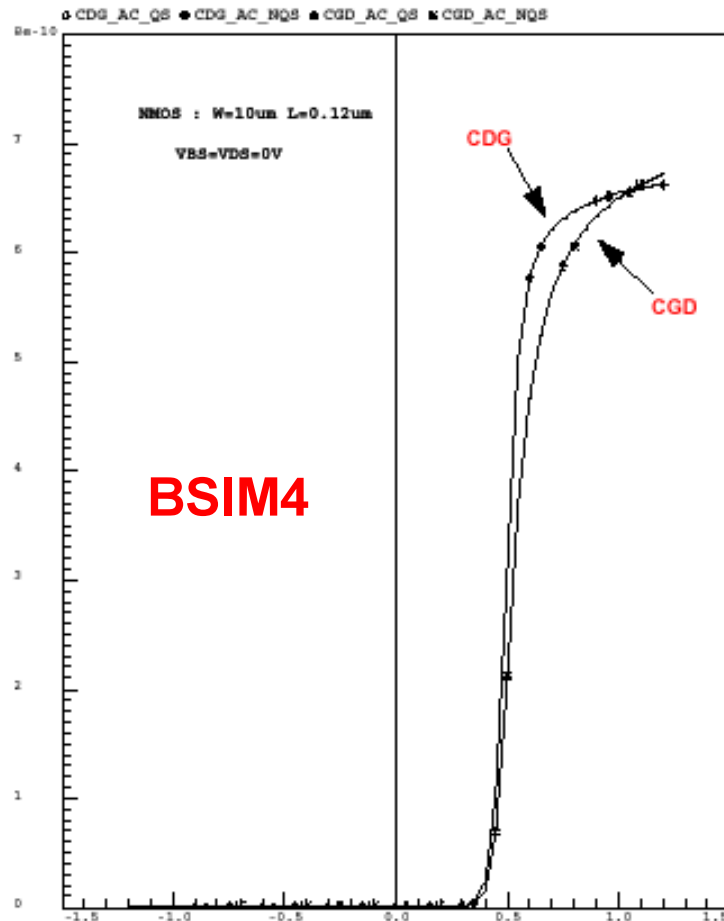reciprocity: C_{DG} - C_{GD} vs. V_G at $V_{DS}=0V$





(NQS: ACNQSMOD=1)

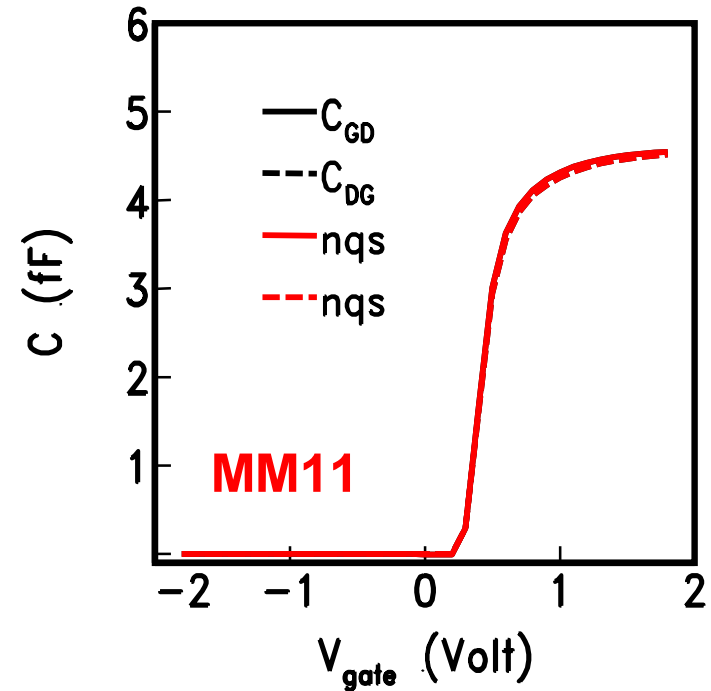

- QS=NQS
- BSIM4: C_{DG} and C_{GD} differ slightly
- MM11: C_{DG} and C_{GD} almost equal

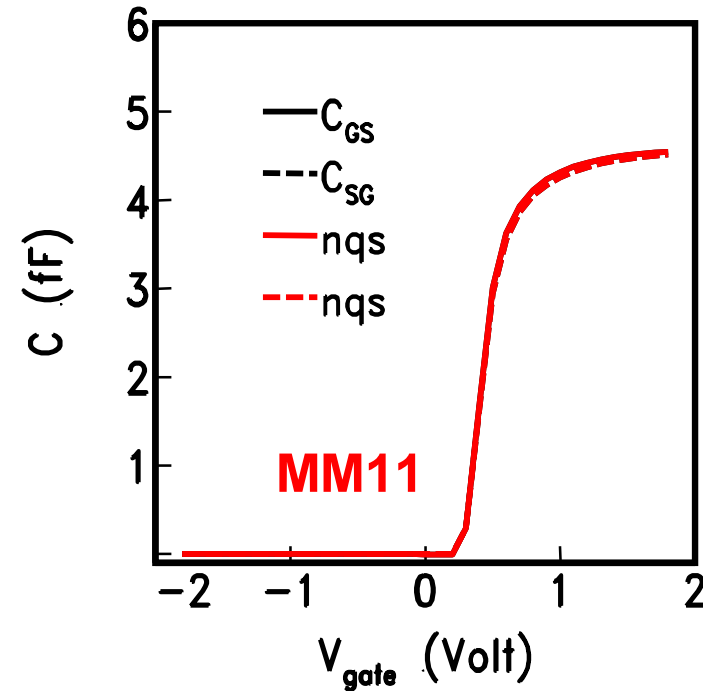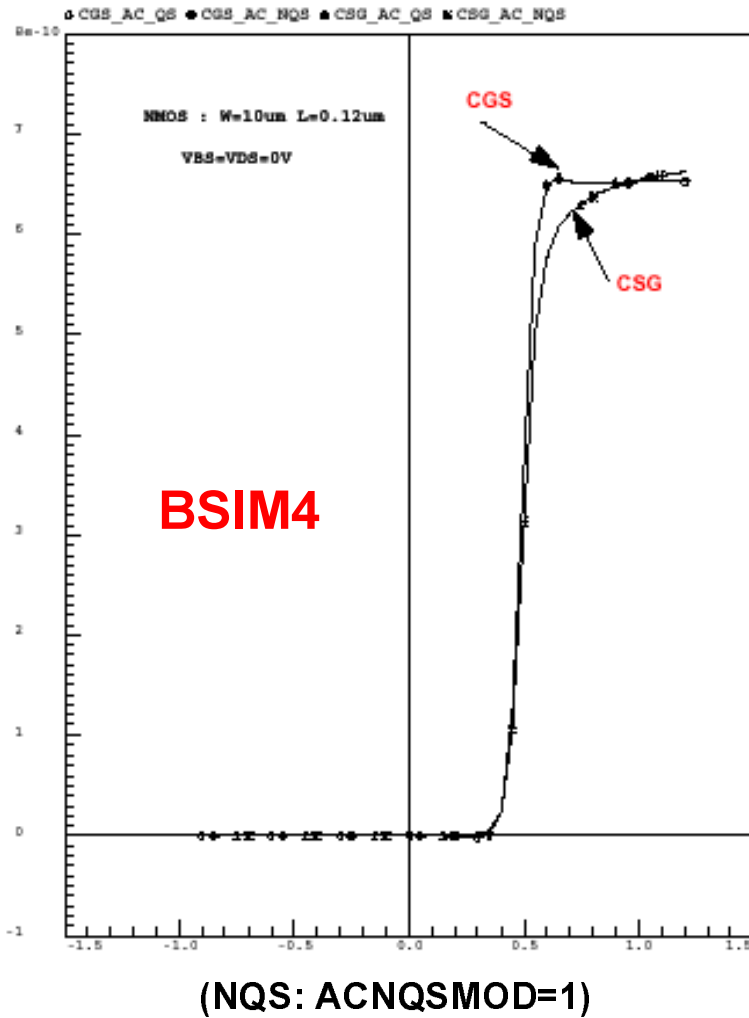reciprocity: $C_{GS}-C_{SG}$ vs. V_G at $V_{DS}=0V$




- QS=NQS
- BSIM4: C_{GS} and C_{SG} differ slightly
- MM11: C_{GS} and C_{SG} almost equal


reciprocity: summary

- **BSIM4**
 - C_{BS} / C_{SB}
 - $|C_{BS}|$ and C_{SB} differ factor 4
 - C_{BS} is negative
 - C_{BD} / C_{DB}
 - C_{BD} and C_{DB} differ factor 4
 - C_{DS} / C_{SD}
 - C_{DS} and C_{SD} differ factor 4
- **MOS Model 11**
 - almost perfect reciprocity (better than $0.01 C_{ox}$)

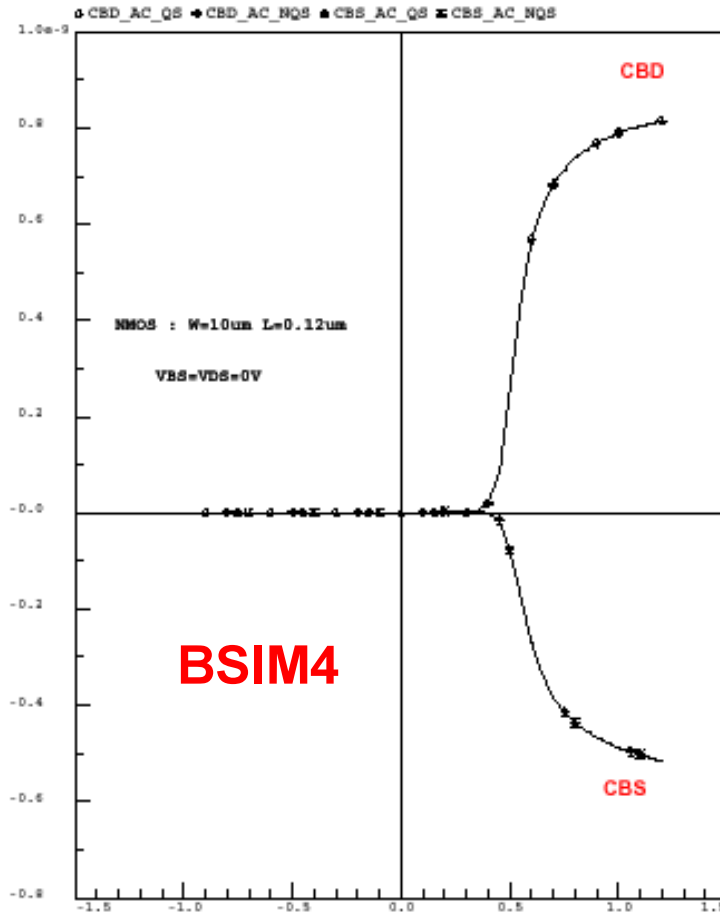symmetry: $C_{BD}-C_{BS}$ vs. V_G at $V_{DS}=0V$





(NQS: ACNQS MOD=1)

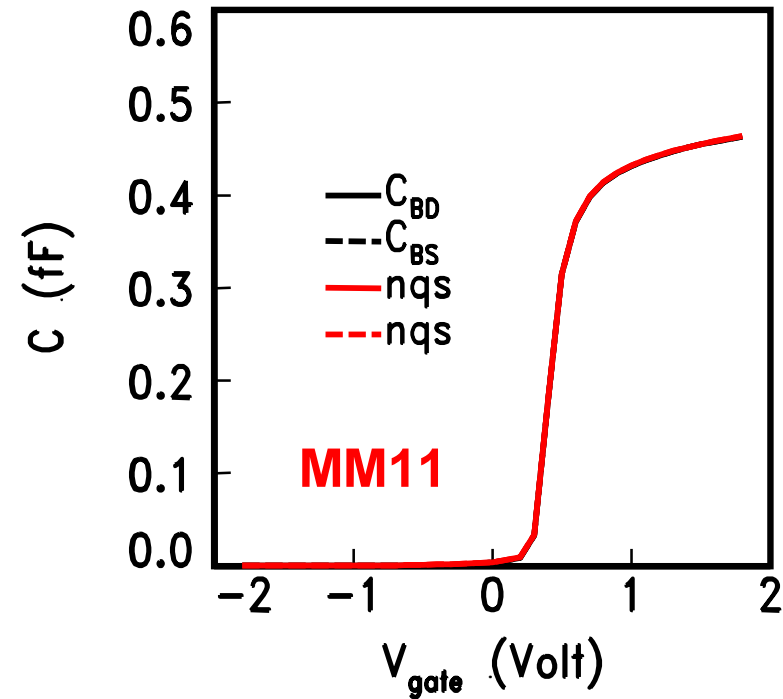


- QS=NQS
- BSIM4: C_{BS} is negative!
- MM11: C_{BD} and C_{BS} are equal

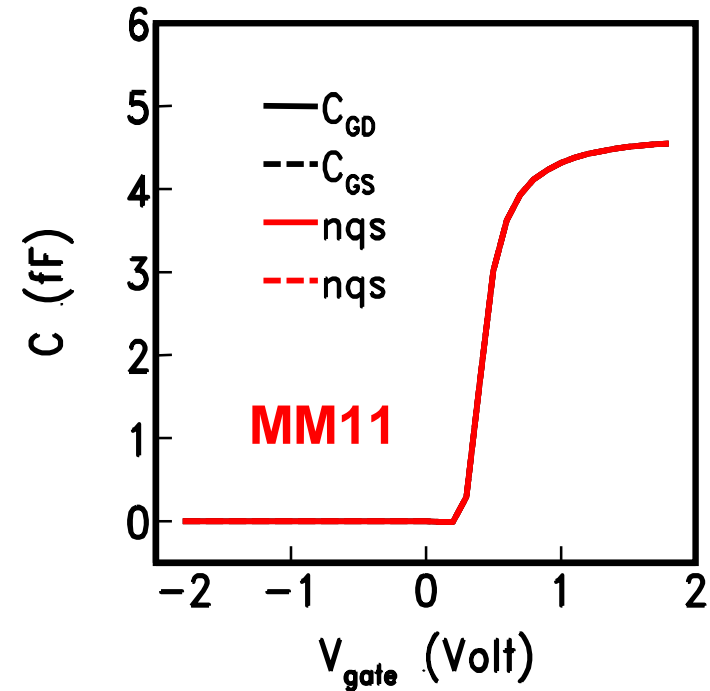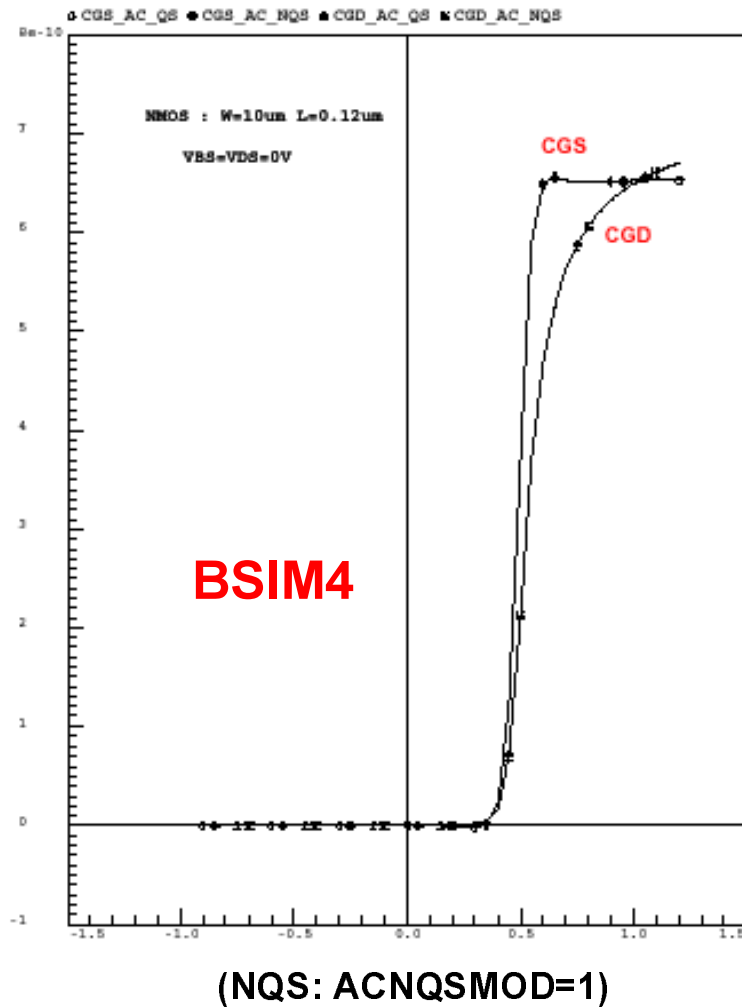symmetry: $C_{GD}-C_{GS}$ vs. V_G at $V_{DS}=0V$




- QS=NQS
- BSIM4: C_{GD} and C_{GS} differ slightly
- MM11: C_{GD} and C_{GS} are equal

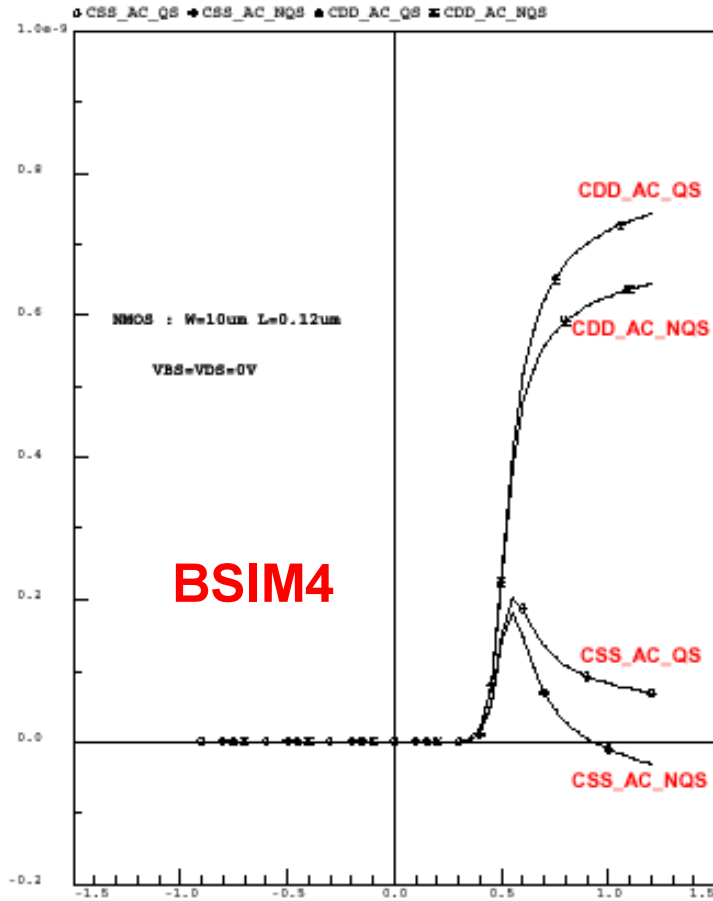symmetry: $C_{SS}-C_{DD}$ vs. V_G at $V_{DS}=0V$



(NQS: ACNQSMOD=1)


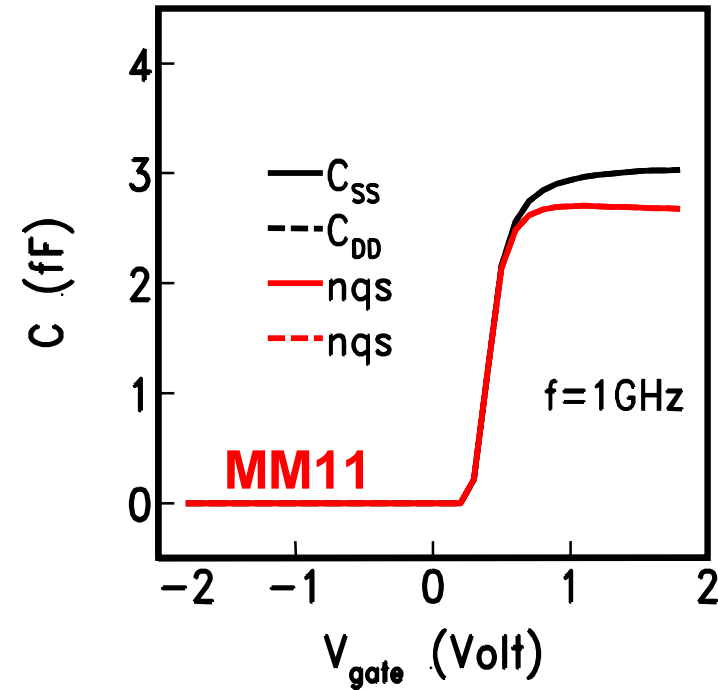


- QS and NQS differ slightly
- BSIM4: C_{SS} and C_{DD} differ factor 4
- MM11: C_{SS} and C_{DD} are equal

symmetry: summary


- **BSIM4**
 - C_{BD} / C_{BS}
 - C_{BS} is negative
 - C_{SS} / C_{DD}
 - C_{SS} and C_{DD} differ factor 4
- **MOS Model 11**
 - perfect symmetry

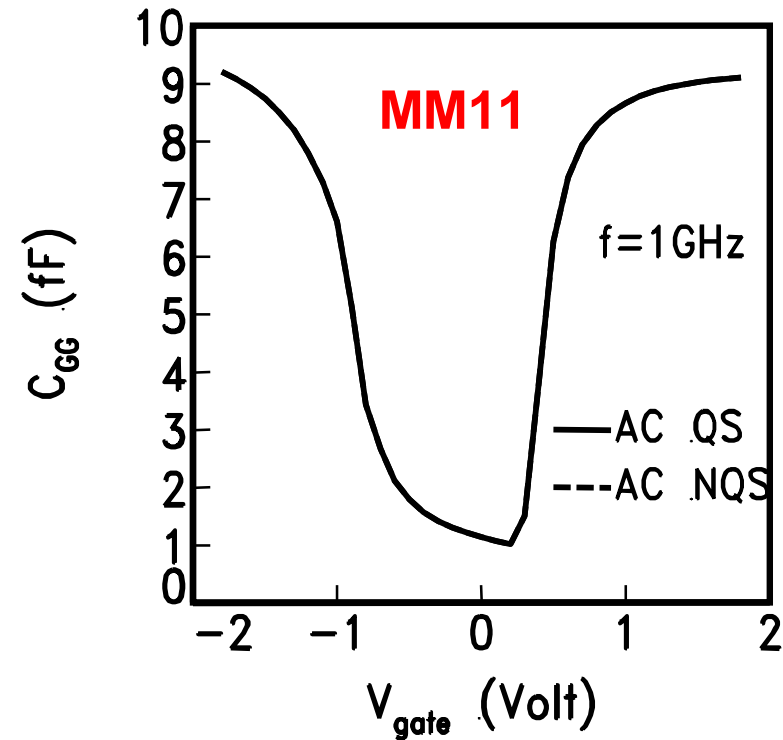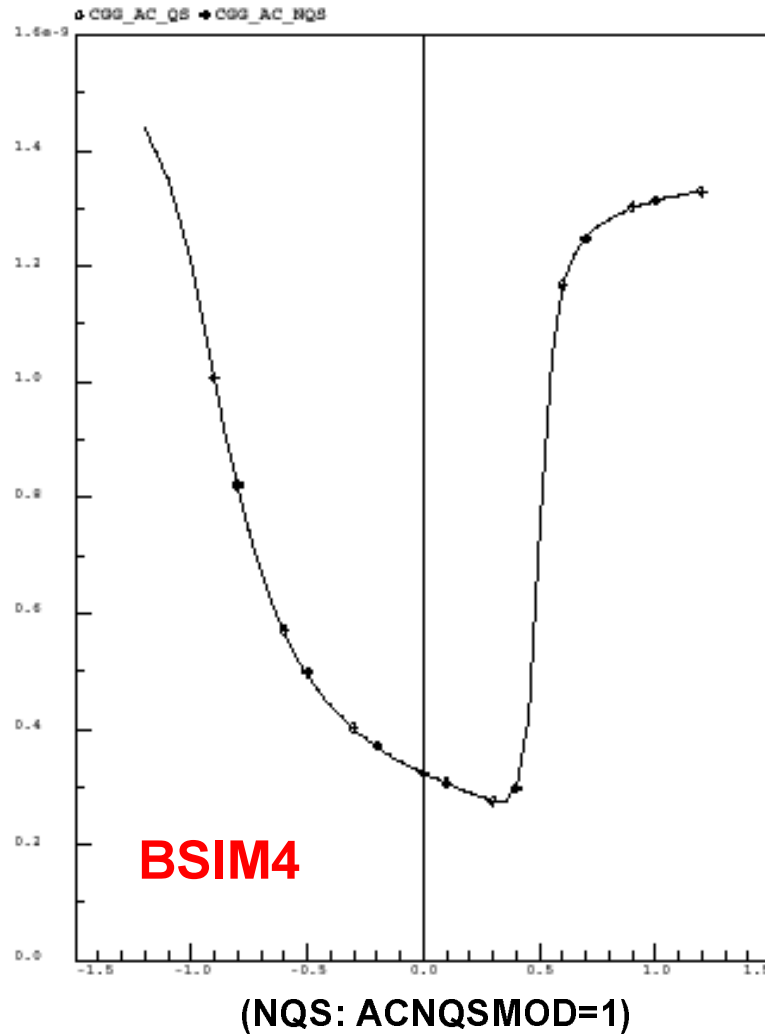qs / nqs at low frequency: C_{GG} vs. V_G at $V_{DS}=0V$




- QS and NQS are equal

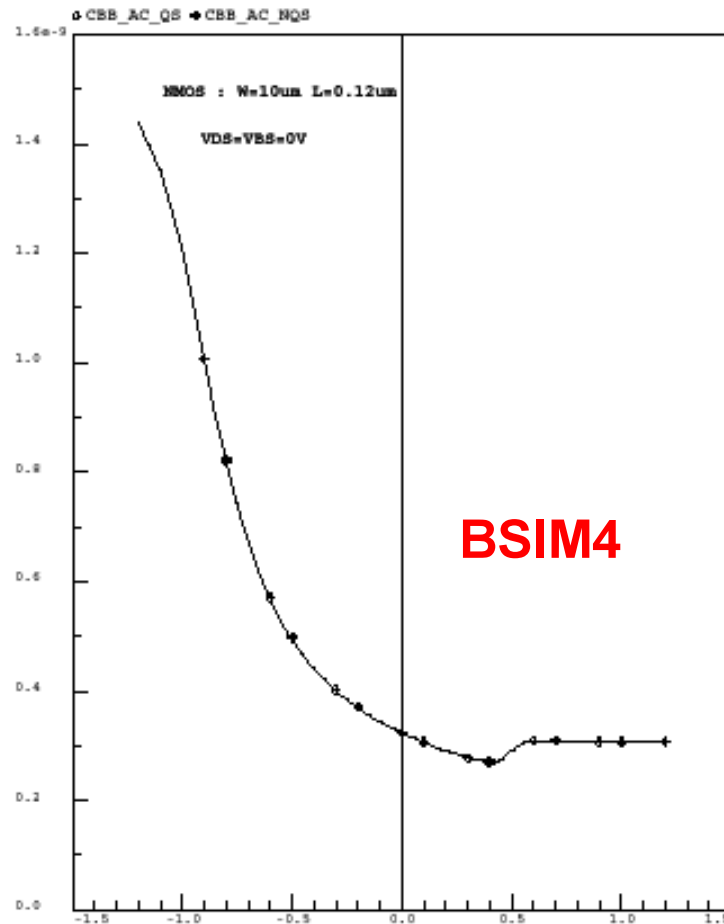qs / nqs at low frequency: C_{BB} vs. V_G at $V_{DS}=0V$



(NQS: ACNQSMOD=1)

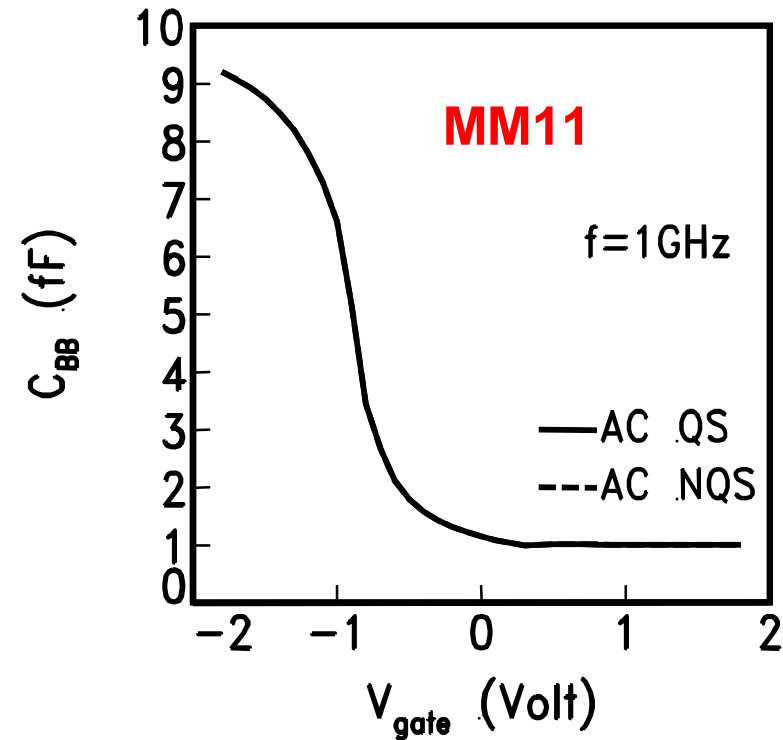

• QS and NQS are equal

comparison QS / NQS at low frequency: summary





$$C_{ij, qs} = C_{ij, nqs} ?$$

i \ j	G	D	S	B
G	ok	ok	ok	ok
D	ok	no	no	ok
S	ok	no	no	ok
B	ok	ok	ok	ok

similar results
for BSIM4
and MM11

under investigation

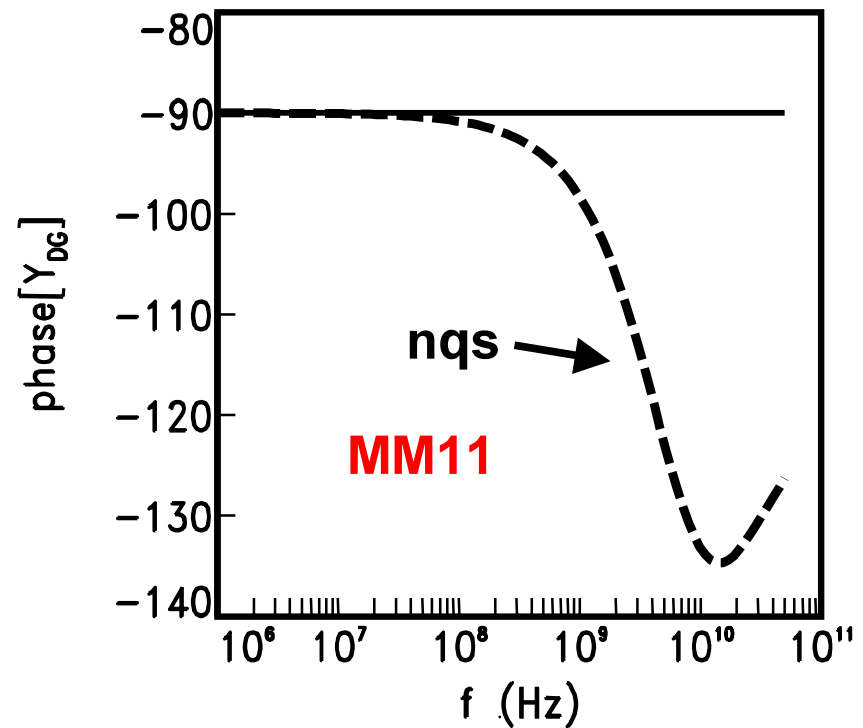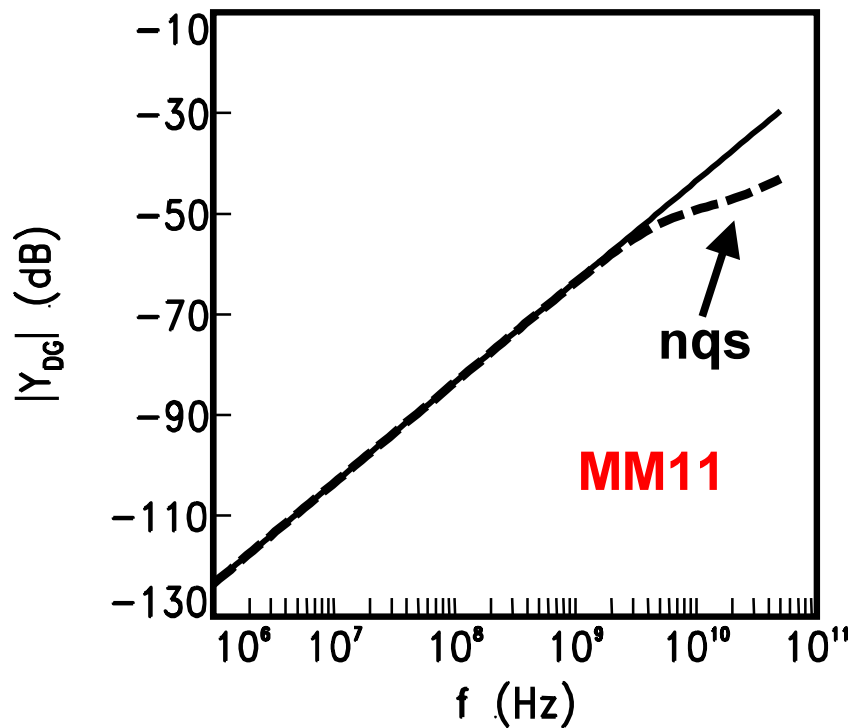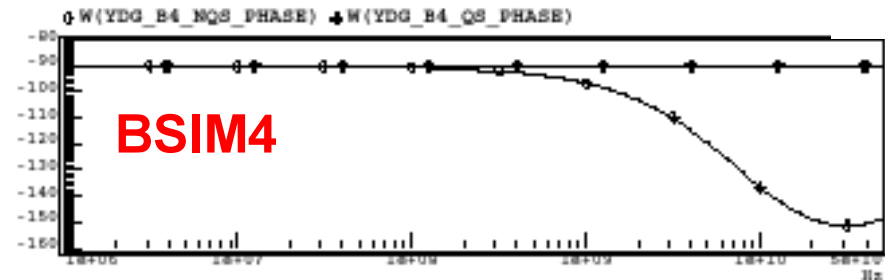
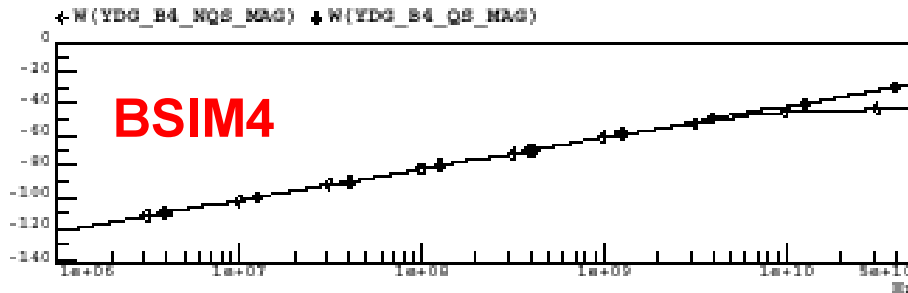
qs / nqs at high frequency: Y_{DG} vs. frequency







qs / nqs at high frequency: Y_{DG} vs. frequency

phase check:

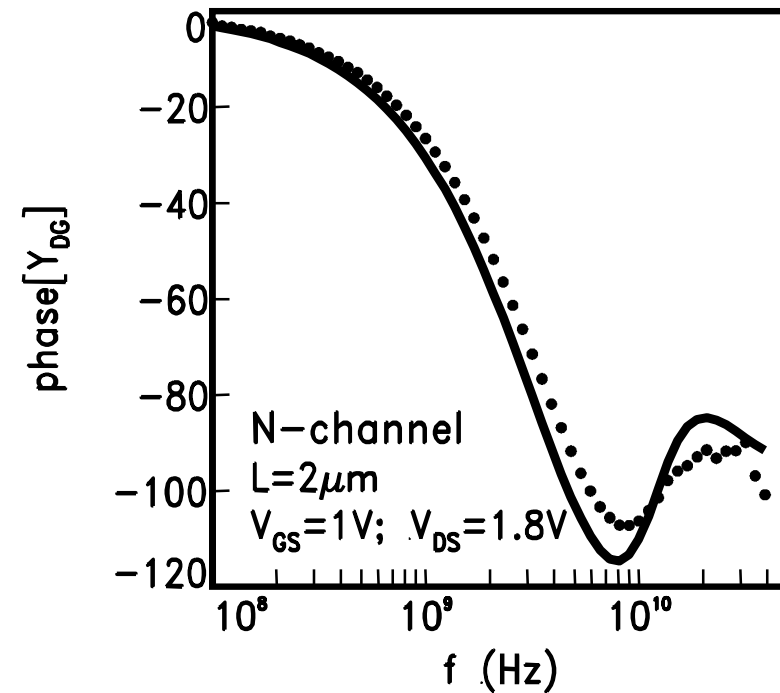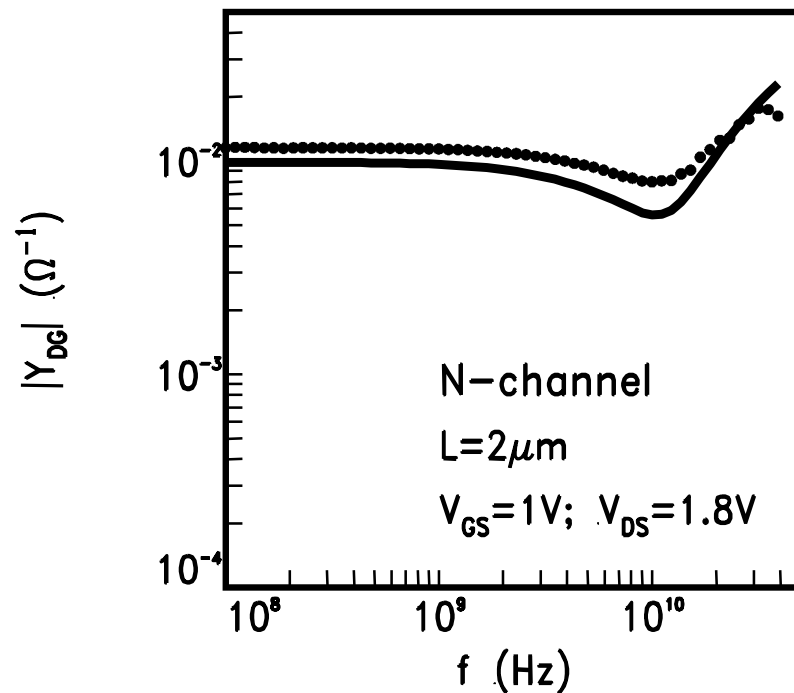- experimental data
- channel segmentation for MOS Model 9



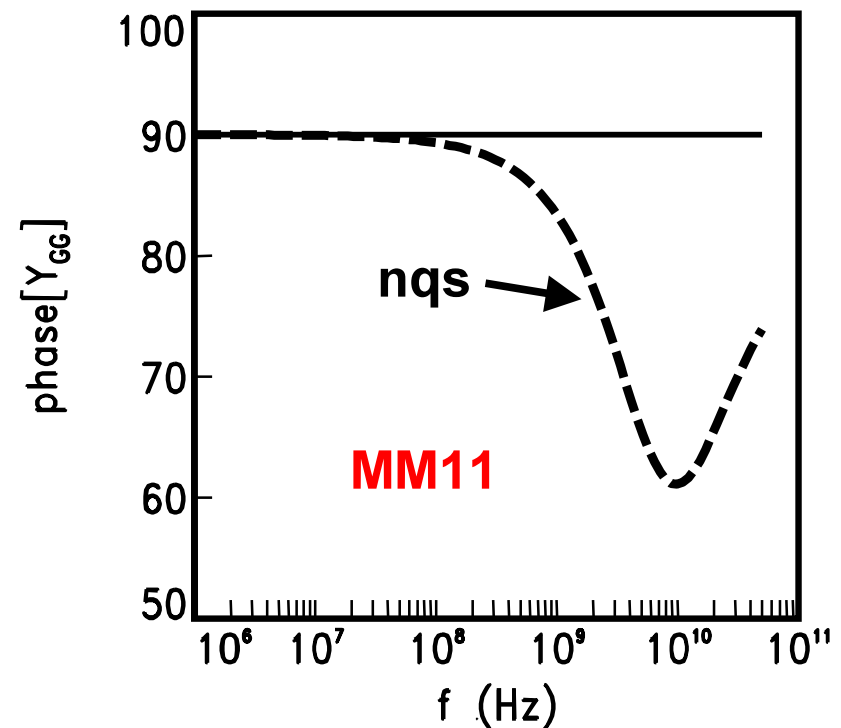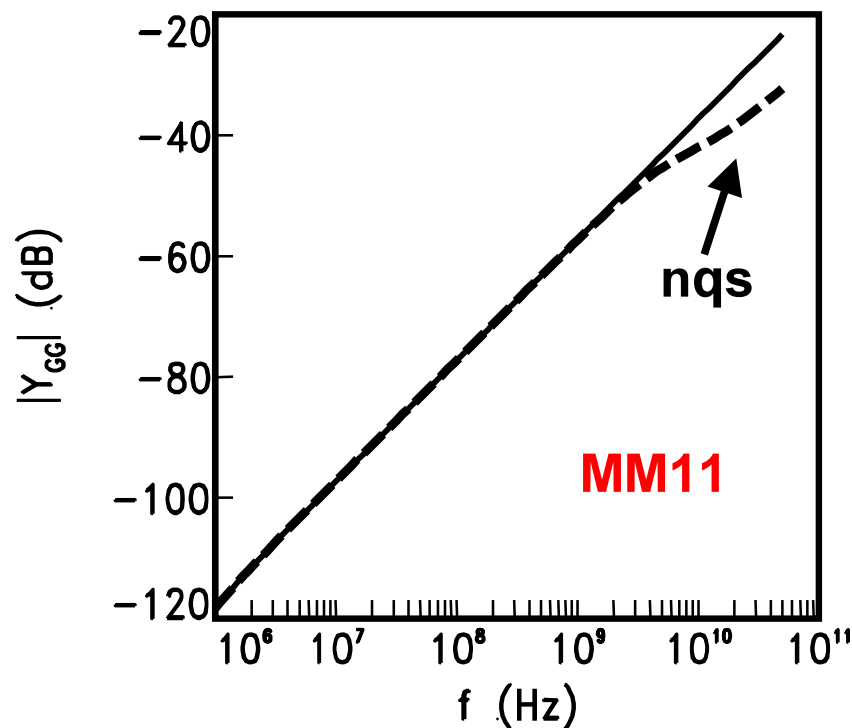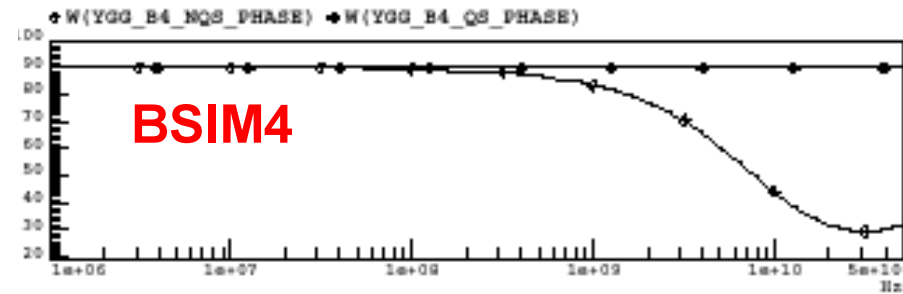
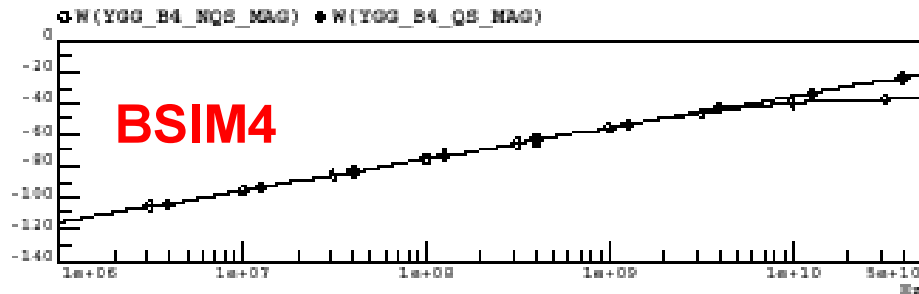
qs / nqs at high frequency: Y_{GG} vs. frequency







qs / nqs at high frequency: Y_{GG} vs. frequency

phase check:



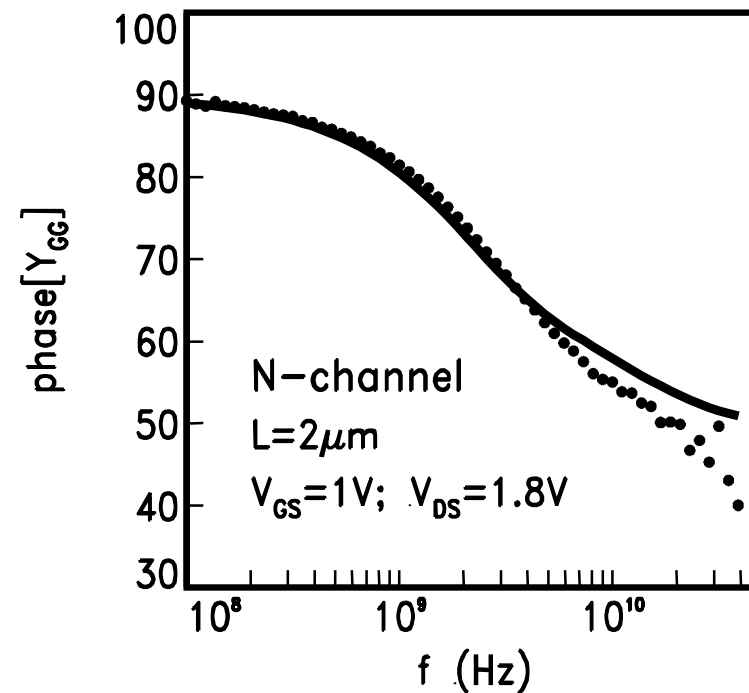
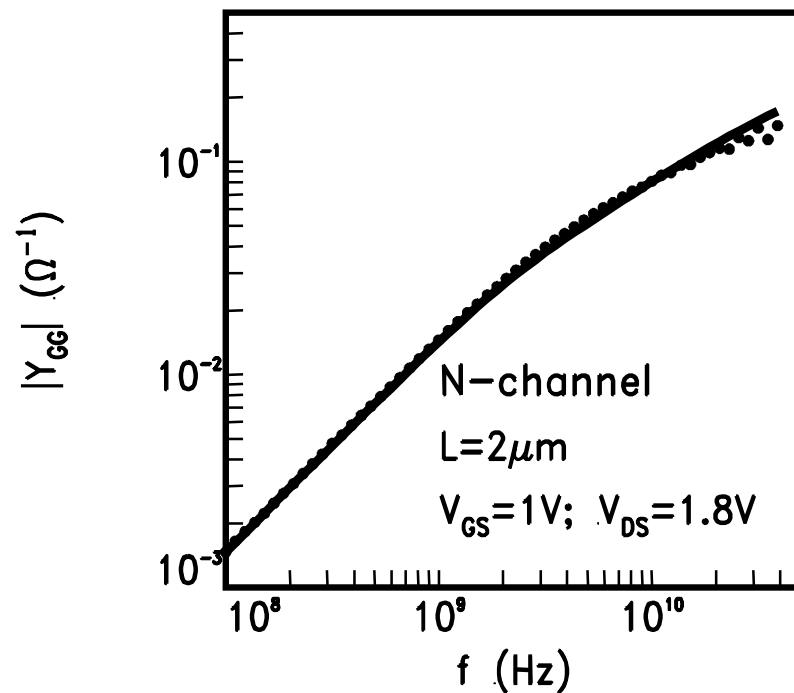
- experimental data
- channel segmentation for MOS Model 9



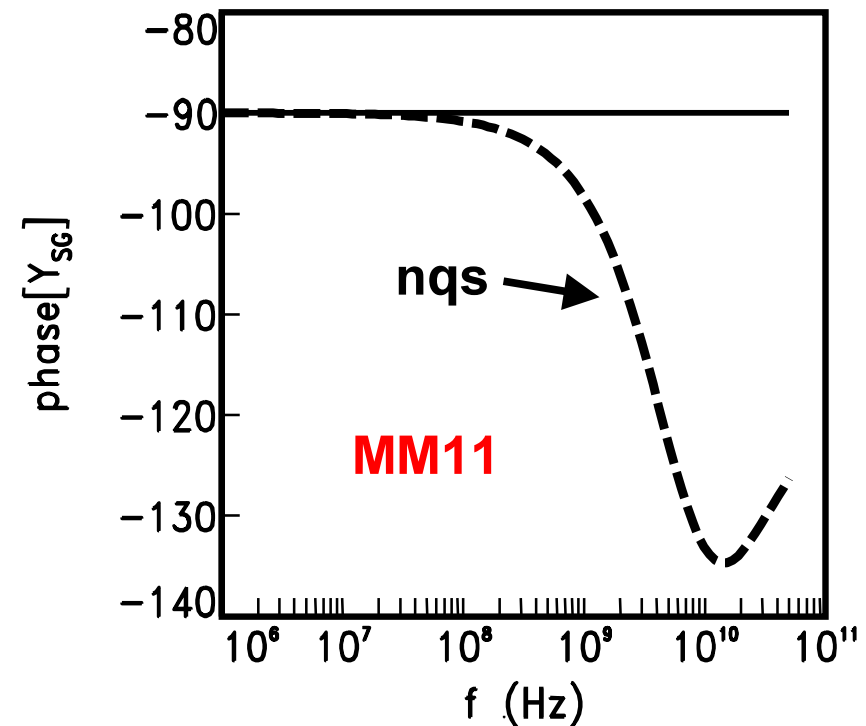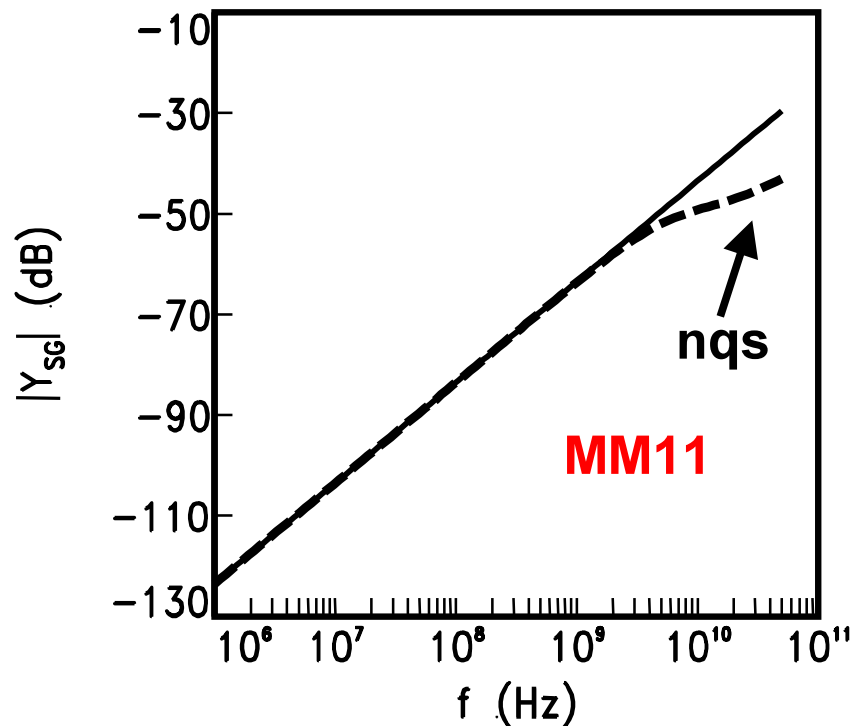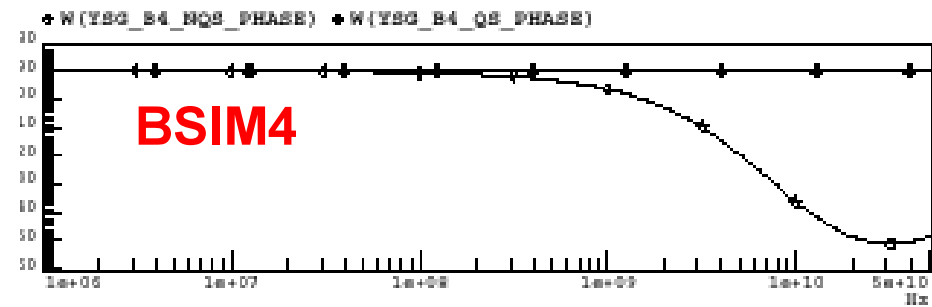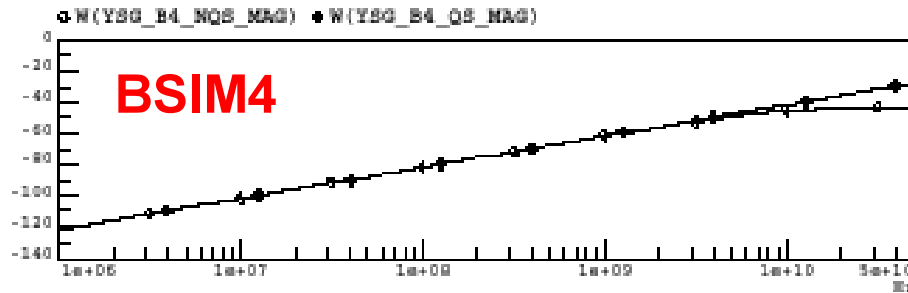qs / nqs at high frequency: Y_{SG} vs. frequency



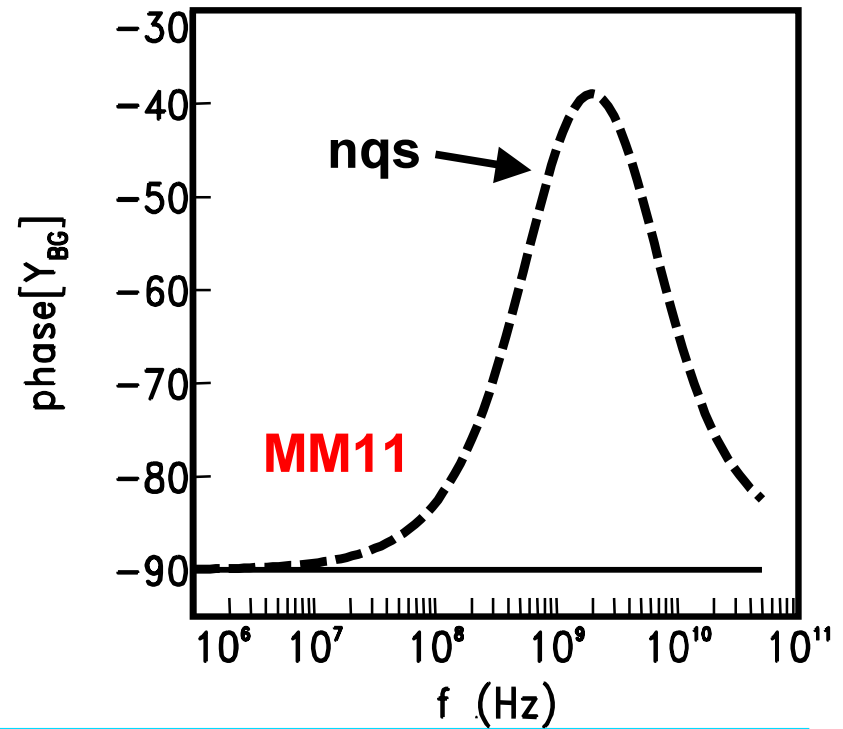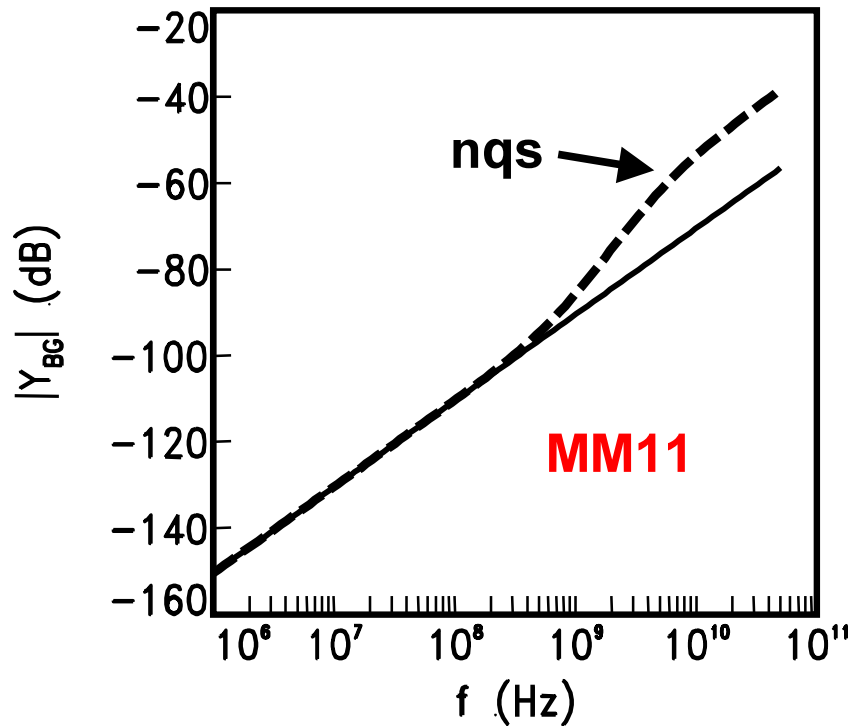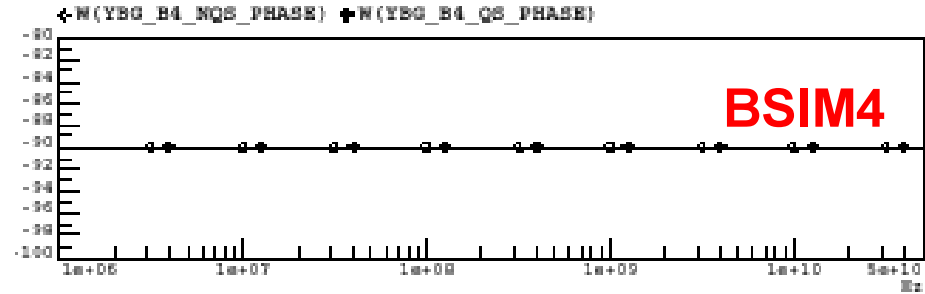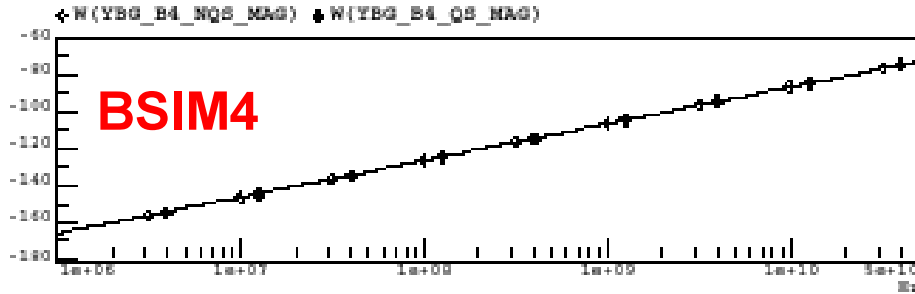qs / nqs at high frequency: Y_{BG} vs. frequency




comparison QS / NQS at high frequency: summary

- **BSIM4**
 - NQS effect on Y_{DG} , Y_{GG} and Y_{SG}
 - no NQS effect on Y_{BG}
- **MOS Model 11**
 - NQS effect on Y_{DG} , Y_{GG} , Y_{SG} and Y_{BG}





qs / nqs: fast voltage ramp in transient

- excitation on the gate




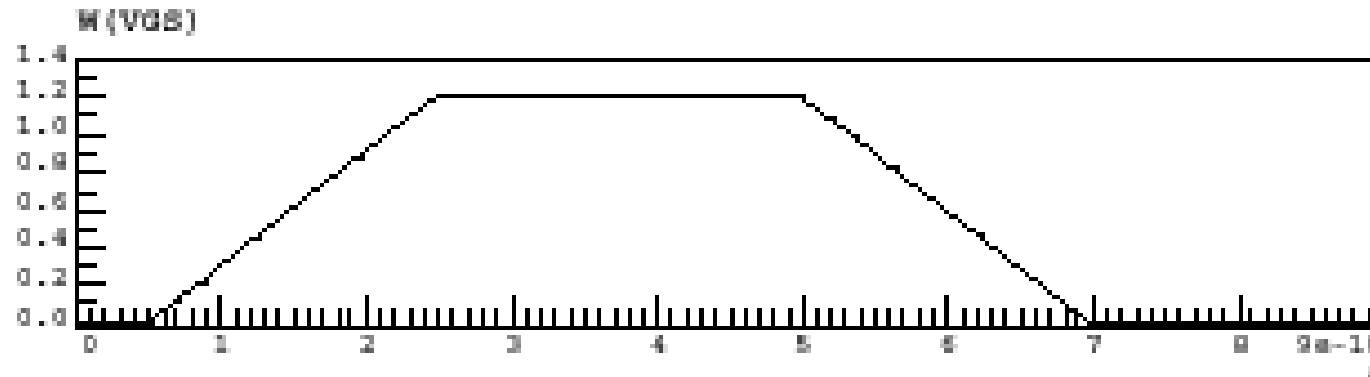


- expected results: smoother waveform in NQS mode
- MOS Model 11 simulations
 - **NQS excl:** without junction capacitances and bulk resistance
 - **NQS incl:** with junction capacitances and bulk resistance

qs / nqs: fast voltage ramp in transient

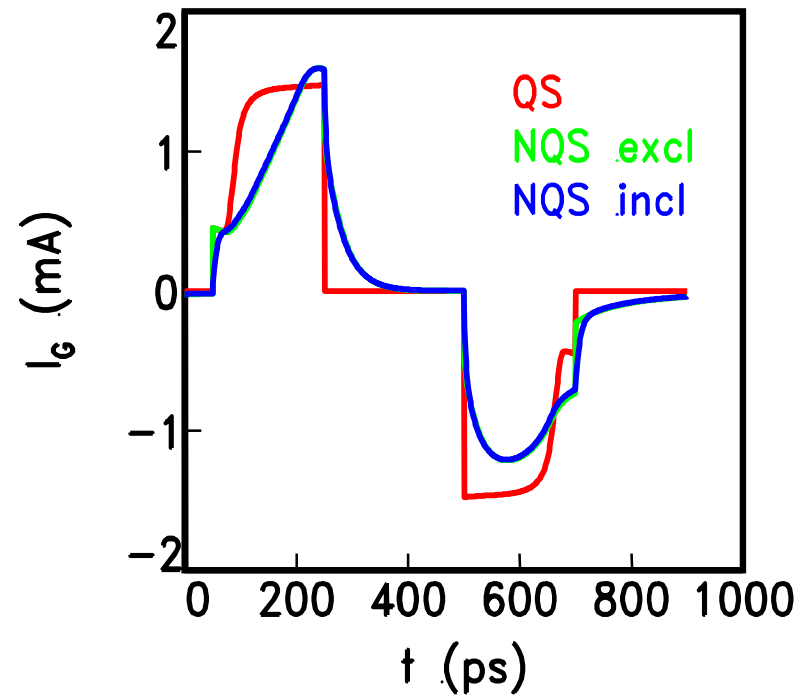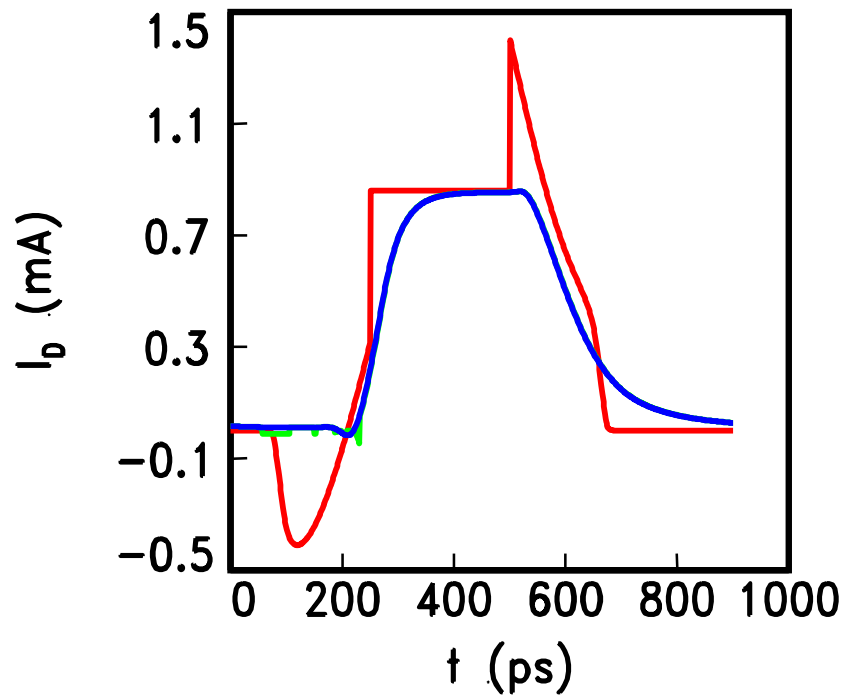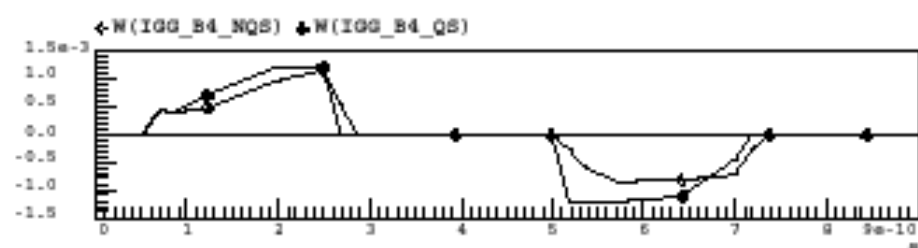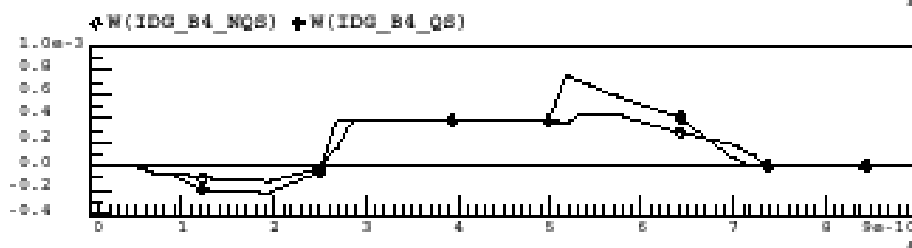

qs / nqs: fast voltage ramp in transient

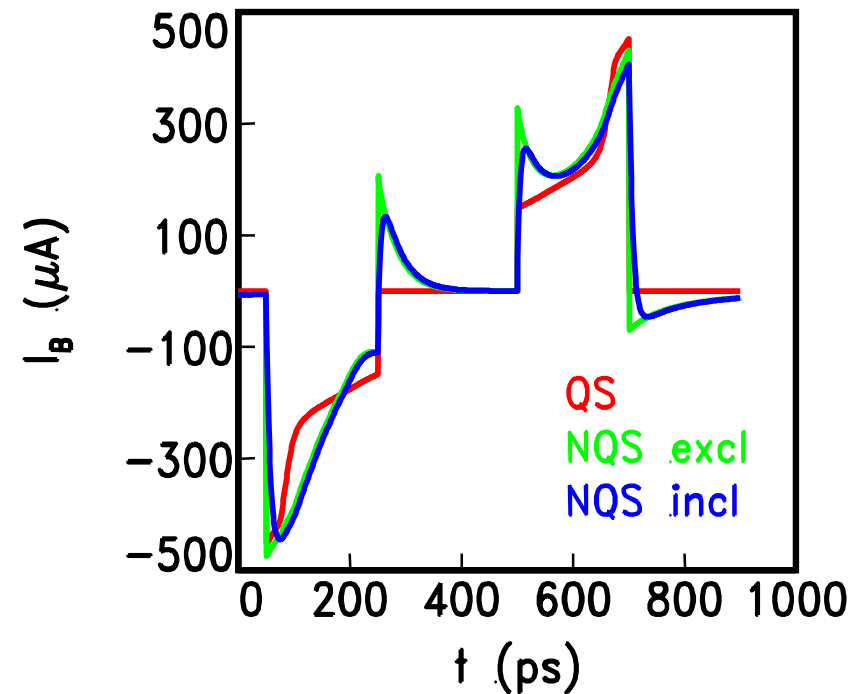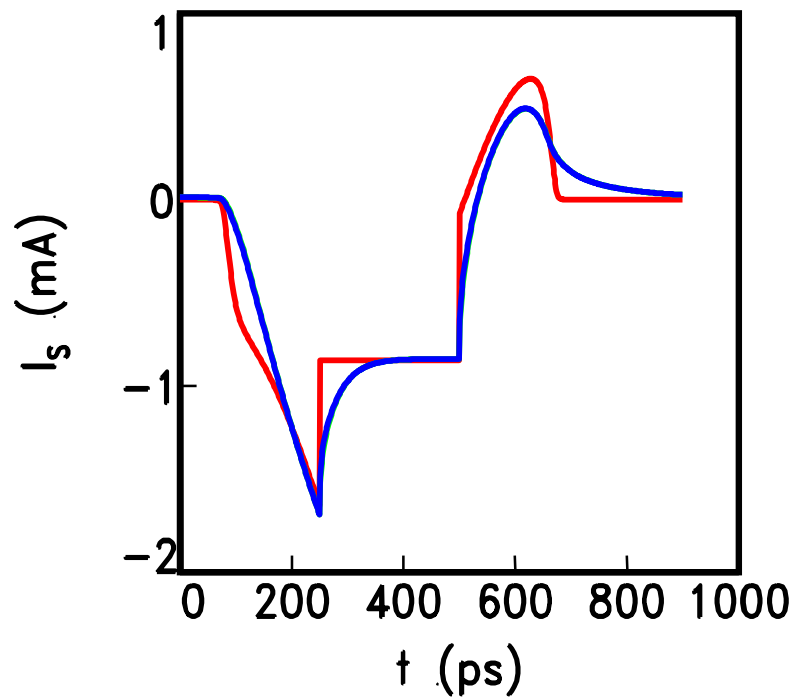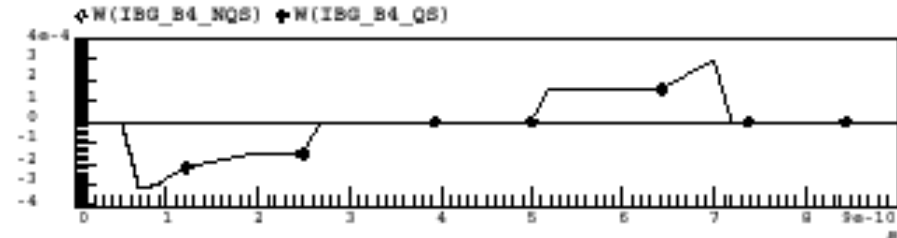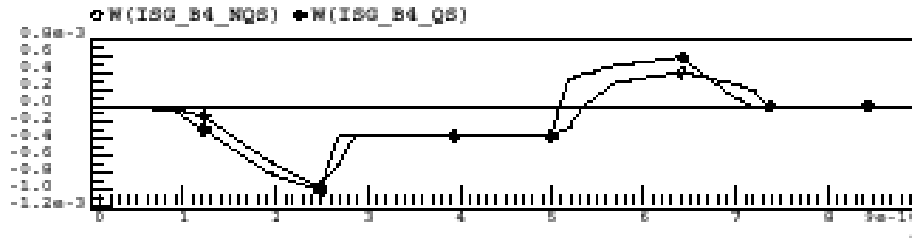

summary

- **reciprocity**
 - **BSIM4**
 - $|C_{BS}|$ and C_{SB} differ factor 4
 - C_{BS} is negative
 - C_{BD} and C_{DB} differ factor 4
 - C_{DS} and C_{SD} differ factor 4
 - **MOS Model 11**
 - almost perfect reciprocity (better than $0.01 C_{ox}$)
- **symmetry**
 - **BSIM4**
 - C_{BS} is negative
 - C_{DD} and C_{SS} differ factor 4
 - **MOS Model 11**
 - perfect symmetry

summary (cont'd)

- **comparison QS / NQS at low frequency**
 - NQS \neq QS for C_{DS} , C_{SD} , C_{SS} and C_{DD}
 - similar results for BSIM4 and MM11
- **comparison QS / NQS at high frequency**
 - **BSIM4**
 - NQS effect on Y_{DG} , Y_{GG} and Y_{SG}
 - no NQS effect on Y_{BG}
 - **MOS Model 11**
 - NQS effect on Y_{DG} , Y_{GG} , Y_{SG} and Y_{BG}